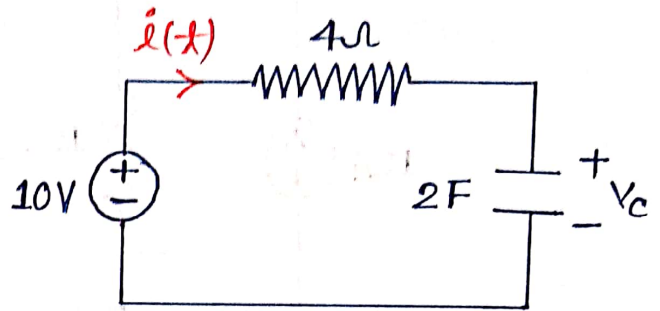


BE QUIZ-2
SOLUTION

SOL(1)÷



$$V_c(0^-) = 6V \quad (\text{Given})$$

$$\therefore V_c(0^+) = V_c(0^-) = 6V \quad (\text{Capacitor doesn't allow sudden change of voltage})$$

$$\therefore V_c(\infty) = 10V$$

$$\therefore V_c(t) = [V_c(0^+) - V_c(\infty)] e^{-t/RC} + V_c(\infty)$$

$$\text{Time constant} = \tau = RC = 4 \times 2 = 8 \text{ Sec}$$

$$\therefore V_c(t) = (6 - 10) e^{-t/8} + (+10) = (+10 - 4e^{-t/8}) V$$

$$\therefore i(t) = C \frac{dV_c(t)}{dt} = 2 \cdot \frac{d}{dt} \{ +10 - 4e^{-t/8} \}$$


$$= 2 \times (-4) \times \left(-\frac{1}{8}\right) e^{-t/8} = e^{-t/8} \rightarrow (4 \text{ POINT})$$

\therefore Energy absorbed by 4Ω resistor in $0 < t < \infty$,

$$E = \int_0^{\infty} i^2(t) \times R \, dt = \int_0^{\infty} 4 \cdot e^{-t/4} \, dt = 4 \left[\frac{e^{-t/4}}{-1/4} \right]_0^{\infty}$$

$$= -16 [e^{-t/4}]_0^{\infty} = 16 \text{ Joule} \rightarrow (2 \text{ POINT})$$

SOL(2) ÷

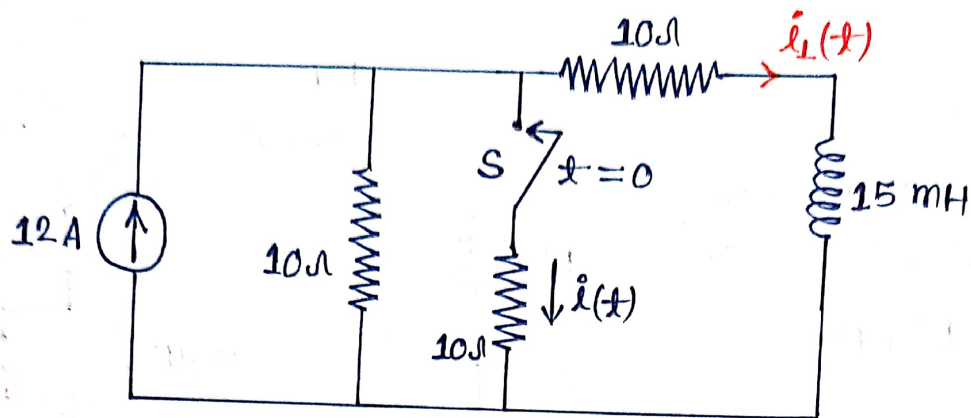

$$i_L(0^+) = i_L(0^-) = \frac{12}{2} = 6A$$

$$\therefore i(0^+) = \frac{6}{2} = 3A$$

→ (0.5 POINT)

$$\therefore i(\infty) = \frac{12}{3} = 4A$$

→ (0.5 POINT)


$$\therefore i(t) = [i(0^+) - i(\infty)] e^{-t/\tau} + i(\infty)$$

Here, Time constant (τ) = $\frac{L}{R_{eq}}$

$$= \left(\frac{15 \times 10^{-3}}{15} \right)$$

$$= 1 \text{ msec}$$

→ (0.5 POINT)

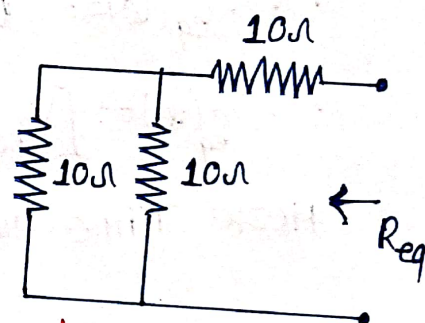

$$R_{eq} = 10 + (10 || 10) = 15\Omega$$

$$\therefore i(t) = (3 - 4) e^{-t/10^{-3}} + 4$$

$$= (4 - e^{-1000t}) A$$

→ (2.5 POINT)

SOL(3) ÷

at $t = 0^-$

$$C_{eq} = \frac{0.2 \times (0.5 + 0.3)}{0.2 + 0.5 + 0.3}$$
$$= 0.16 \mu F$$

$$V_{Ceq}(0^+) = V_{Ceq}(0^-)$$

(Capacitor doesn't allow sudden change of voltage)

Here, $V_{Ceq}(0^-) = 100 V$

$$\therefore V_{Ceq}(0^+) = 100 V \rightarrow (0.5 \text{ POINT})$$


$$\therefore V_{Ceq}(\infty) = 0 \rightarrow (0.5 \text{ POINT})$$

$$\therefore V_C(t) = [V_{Ceq}(0^+) - V_{Ceq}(\infty)] e^{-t/\tau} + V_{Ceq}(\infty)$$

Here Time constant (τ) = $RC_{eq} = 5 \times 10^3 \times 0.16 \times 10^{-6}$

$$= 0.8 \text{ msec} \rightarrow (1 \text{ POINT})$$
$$V_{Ceq}(t) = (100 - 0) e^{-t/(0.8 \times 10^{-3})} + 0$$
$$= 100 e^{-\frac{10000}{8} t}$$
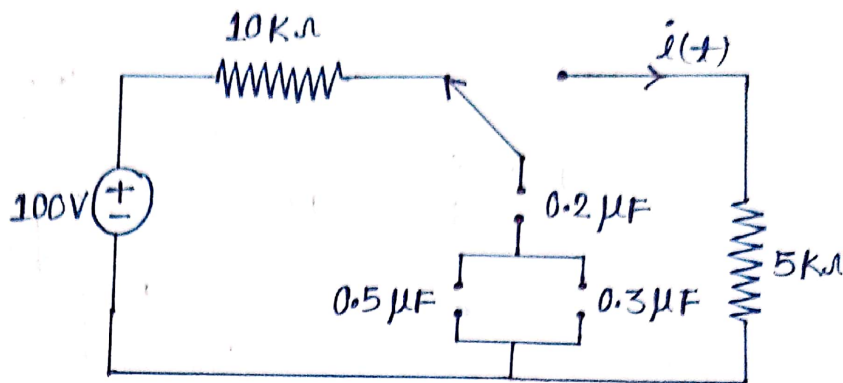
$$\therefore i(t) = -C_{eq} \cdot \frac{dV_{Ceq}(t)}{dt} = (0.16 \times 10^{-6}) \cdot \frac{d}{dt} \left\{ 100 e^{-10^4 t / 8} \right\}$$
$$= -0.16 \times 10^{-6} \times 100 \times \left(-\frac{10^4}{8} \right) e^{-1250 t}$$
$$= 20 e^{-1250 t} \text{ mA} \rightarrow (4 \text{ POINT})$$




SOL(4)÷

Step(I) at $t=0^-$

$$\therefore i_L(0^-) = \left(\frac{100}{20+20} \right) = 2.5 \text{ A}$$
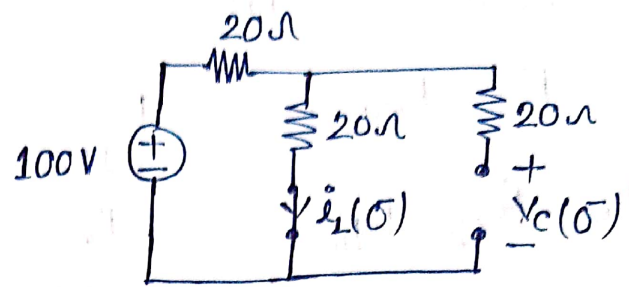
$$\therefore V_C(0^-) = 20 \times 2.5 = 50 \text{ V}$$



Step(II) at $t=0^+$

$$\therefore i_L(0^+) = i_L(0^-) = 2.5 \text{ A} \rightarrow (0.5 \text{ POINT})$$


$$\therefore V_C(0^+) = V_C(0^-) = 50 \text{ V} \rightarrow (0.5 \text{ POINT})$$

Step(III)

$$V_L = L \frac{di}{dt}$$

$$50 = 1 \times \frac{di(0^+)}{dt}$$
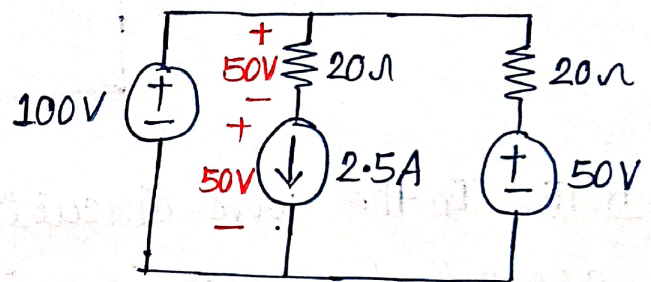
$$\therefore \frac{di(0^+)}{dt} = 50 \text{ A/sec}$$



$\rightarrow (3 \text{ POINT})$



SOL(5) :-

Here, $L = 4H$

For R_{eq} -

$$R_{eq} = R_{AB} = R_{th}$$

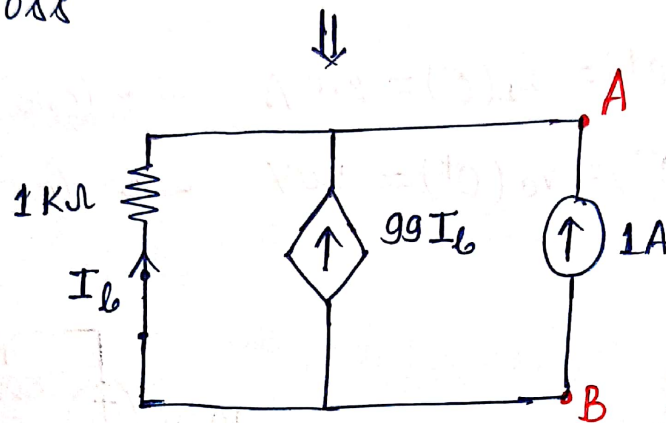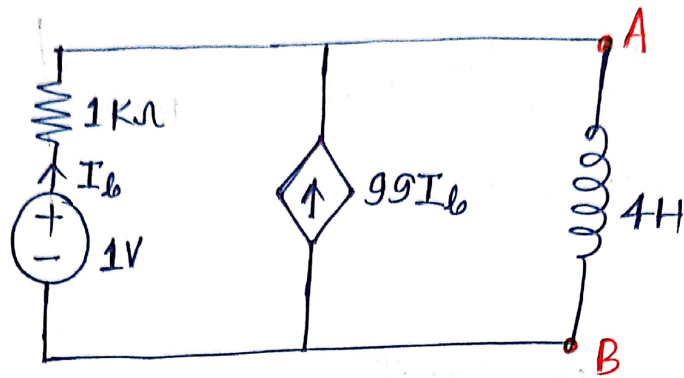NOTE: 1A external current source is connected across terminal A-B.



NOTE: In the above circuit while finding time constant, dependent source is neither replaced by open circuit or short circuit.

$$I_b + 99I_b + 1 = 0$$

$$I_b = (-1/100)$$

$$I_b = \frac{-V_A}{1 \times 10^3}$$

$$\therefore V_A = 10V = V_{AB}$$

$$\therefore R_{th} = \frac{V_{AB}}{1} = 10\Omega = R_{eq} \rightarrow (2 \text{ POINT})$$

$$\therefore \text{Time Constant} = \frac{L}{R_{eq}} = \frac{4}{10} = 0.4 \text{ Sec} \rightarrow (1 \text{ POINT})$$