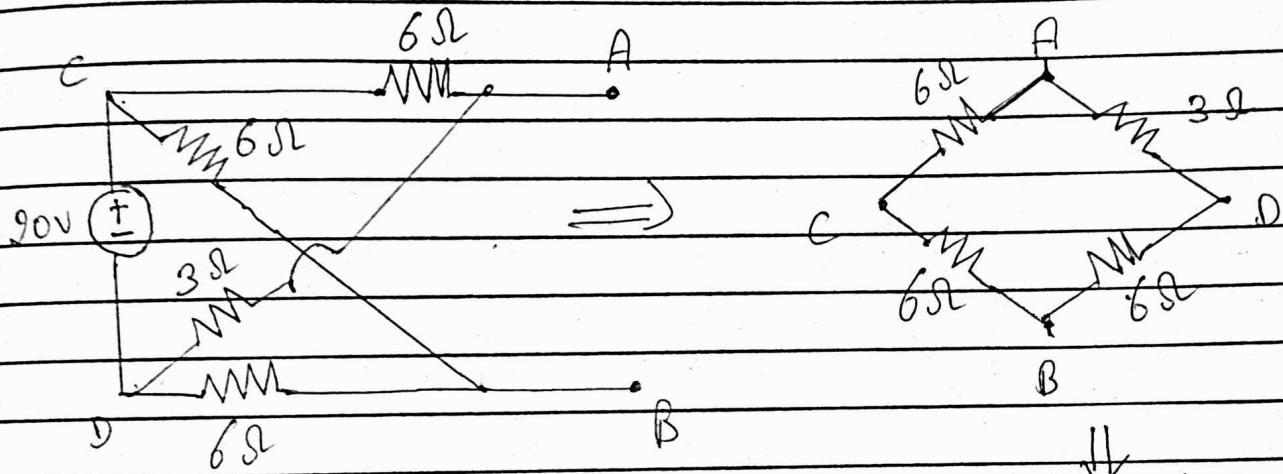


1st Question

First find Source V_{TH} & R_{TH} using Thevenin Theorem



↓
Apply Nodal Analysis

Using Nodal Analysis

$$\frac{V_A - 20}{6} + \frac{V_A}{2} = 0 \quad \rightarrow (1)$$

$$\frac{V_B - 20}{6} + \frac{V_B}{6} = 0 \quad \rightarrow (2)$$

$$V_A - 20 + 2V_A = 0$$

$$V_A = 20/3 \text{ Volt}$$

$$2V_B = 20$$

$$V_B = 10 \text{ Volt}$$

$$V_A = 20/3 \text{ Volts}$$

$$V_B = 10 \text{ Volts}$$

$$\text{so, } V_A - V_B = \frac{20}{3} - 10 \Rightarrow \left(-\frac{10}{3} \text{ Volts} \right) = V_{TH}$$

Teacher's Signature:


~~Across Load~~

P across $200\Omega \Rightarrow -\frac{5}{3} \times \frac{5}{3} \times \frac{1}{200} = \frac{1}{24} \text{ W } [V^2/R = P]$

P across $50\Omega \Rightarrow I_2^2 \times 50 = 169/32 = 5.281 \text{ W } [P=I^2R]$


P across $V_a \Rightarrow I_2 \times V_a = \frac{195}{3 \times 200} \times 14.58 = 4.738 \text{ W } [P=VI]$

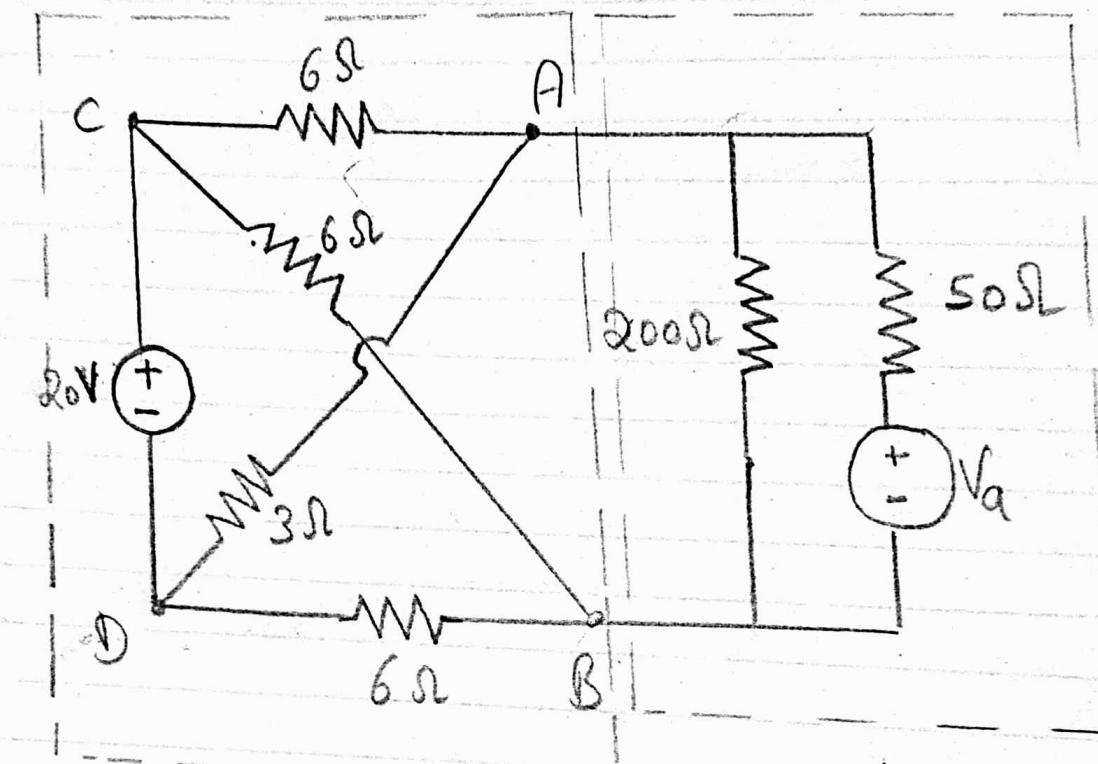P across $V_{TH} = V_{TH} \times I = -\frac{10}{3} \times (-1/3) = \frac{10}{9} = 1.11 \text{ W } [P=V^2/R]$



Source

Load

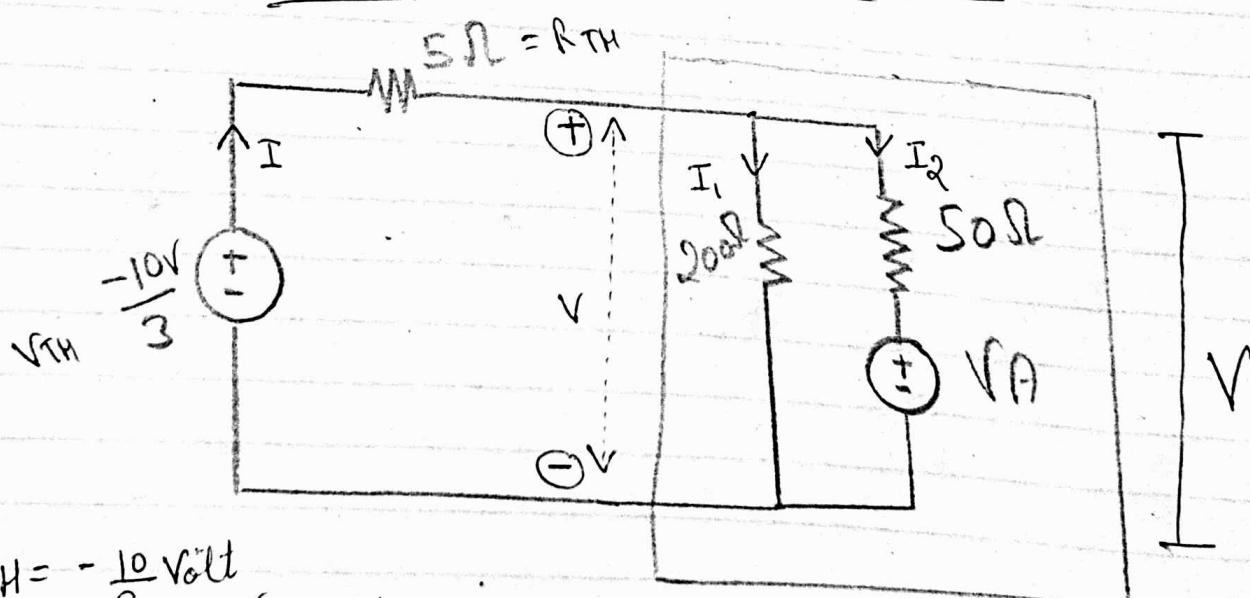


$$V_{TH} = -\frac{10}{3} \text{ Volt}$$

Eg. Theremin

$$R_{TH} = 5\Omega$$

load

Answer

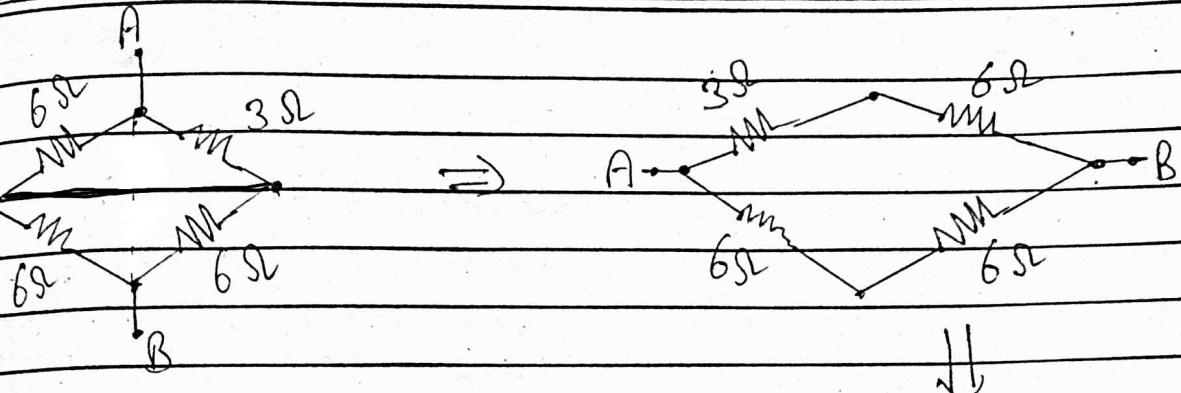


$$(5\Omega) = \frac{18}{2} + 3$$

$$\Rightarrow (3 \parallel 6) \text{ series } (6 \parallel 6)$$

$$= \frac{3 \times 6}{3+6} + \frac{6 \times 6}{6+6}$$

$$R_{TH} = 5\Omega$$

So, eq. Thenen

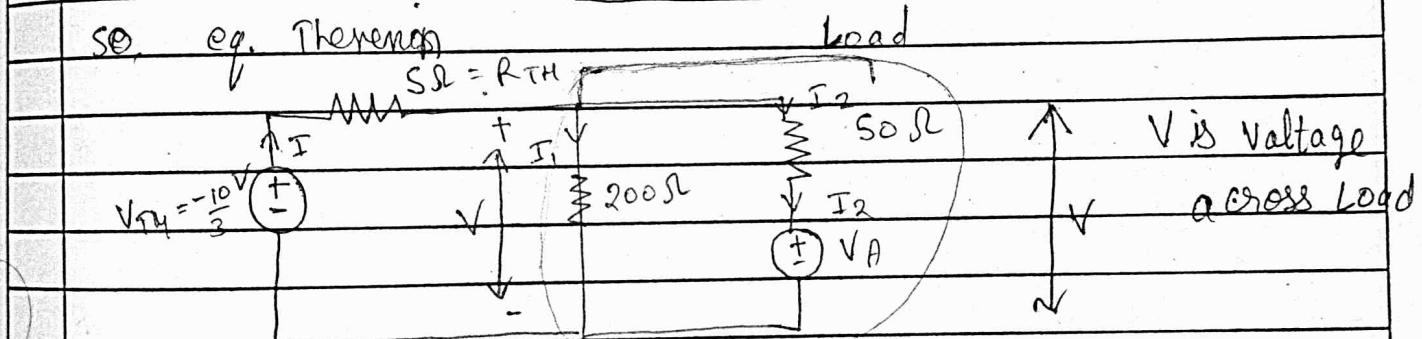

$$V_{TH} = -10/3 \text{ Volt}$$

$$\& R_{TH} = 5\Omega$$

\therefore When max power is transferred to a load.

$$\Rightarrow V = V_{TH} - IR_{TH}$$

Power going into load. $\Rightarrow P_L = V_{TH}I - I^2R_{TH}$

$$\Rightarrow \text{To Maximize } P_L \Rightarrow \frac{\partial P_L}{\partial I} = 0$$

$$\Rightarrow V_{TH} - 2IR_{TH} = 0 \Rightarrow I = \frac{V_{TH}}{2R_{TH}}$$

\therefore Let V be voltage across load

$$\Rightarrow V = \frac{V_{TH}}{2}$$

\therefore Max Power is transferred when half of source voltage appears across Load.

Teacher's Signature : _____

Date _____

Expt. No. _____

Page.No. _____

$$S_o \quad V = -\frac{10}{3} \times \frac{1}{2} = -\frac{5}{3} \text{ Volt}$$

$$\Rightarrow I = -\frac{10}{3} - \left(-\frac{5}{3}\right) = -\frac{5}{3} \text{ Volt} = -\frac{1}{3} \text{ Amp} \\ \approx -0.333 \text{ Amp}$$

$$I_1 = -\frac{5}{3} \times \frac{1}{200} = -\frac{5}{3 \times 200} \text{ Amp} \approx 0.00833 \text{ Amp}$$

$$I_2 = -\frac{1}{3} - \left(-\frac{5}{3}\right) = \left(-\frac{1}{3} + \frac{5}{3}\right) \text{ Amp} \\ \approx 0.325 \text{ Amp}$$

$$\text{Now, } V = S_o I_2 + V_A$$

$$V_A = V - S_o I_2$$

$$= 10 - \frac{5}{3} - S_o \left(-\frac{1}{3} + \frac{5}{3}\right)$$

$$V_A \Rightarrow 14.5833 \text{ Volt} = V_A = 14.58 \text{ Volts}$$

\therefore Max power when $R_{load} = R_{eq}$

\therefore Max power transferred when Half of source voltage appears across load

$$R_{eq} = [R_{TH} = 5\Omega] \text{ Answer}$$

$$V_A = 14.5833 \text{ Volts} \text{ Answer}$$

Teacher's Signature: _____

2nd Question

<u>V_1 (Volt)</u>	<u>V_2 (Volt)</u>	<u>V_3 (V)</u>	<u>I (Amp)</u>
2	0	0	1
0	4	0	5
0	0	5	-6

\Rightarrow 1st Method

\therefore We can use superposition theorem to solve this linear Bidirectional circuit & OHM's Law. $V = IR$

\Rightarrow The current I can be split in three parts, $I = I_1 + I_2 + I_3$

$\Rightarrow V_1$ Active, $V_2 \& V_3 = 0$, Then find I_1 .

V_2 Active, $V_1 \& V_3 = 0$, Then find I_2

V_3 Active, $V_1 \& V_2 = 0$, Then find I_3

Then $I_1 + I_2 + I_3 = I$

Here $V_1 = 2, I = 1$ then as $V = IR \Rightarrow R_1 = 2 \Omega$

$$V_2 = 4 \& I = 5 \Rightarrow$$


$$4 = 5R_2 \Rightarrow R_2 = 4/5 \Omega$$

$$V_3 = 5 \& I = -6 \Rightarrow$$

$$5 = -6R_3 \Rightarrow R_3 = -5/6 \Omega$$

Teacher's Signature: _____

2nd question

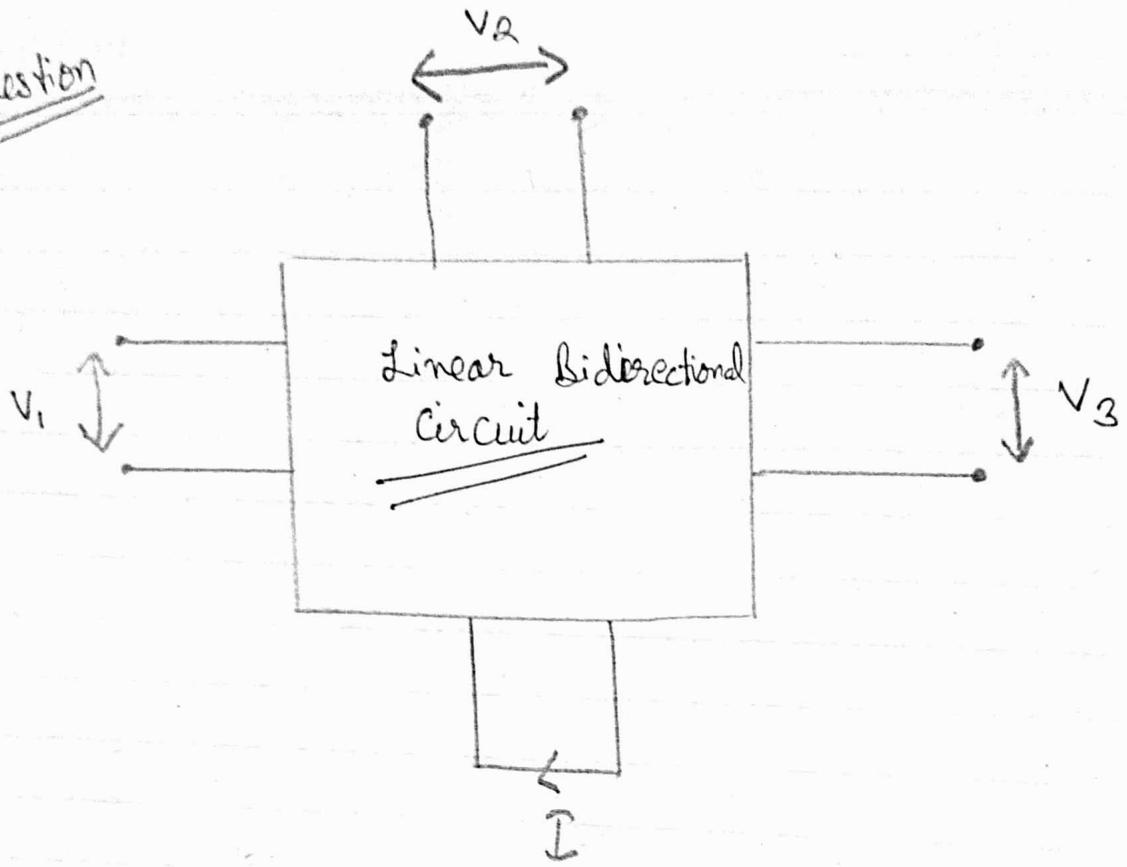

So, if $V_1 = 25V$, $V_2 = 15V$, $V_3 = 20V$

$$\text{Then, } I_1 = \frac{25}{R_1} = \frac{25}{2} = 12.5 \text{ Amp}$$

$$\therefore R_1 = 2\Omega$$

$$\because R_2 = 4\Omega \quad I_2 = \frac{15}{R_2} = \frac{15}{4} = 3.75 = 18.75 \text{ Amp}$$

$$\therefore R_3 = 5\Omega$$

$$I_3 = \frac{20}{R_3} = \frac{20}{5} = -4 \text{ Amp}$$

$$I = I_1 + I_2 + I_3 = (12.5 + 18.75 - 4)A$$

$$I = 25 \text{ Amp} \quad \boxed{\text{Answer}}$$

(OR) we can say, using linearity, if $V = IR$
then $aV = aIR$.

$$\text{Then, } 2 = 1 \times R_1 \Rightarrow 25 = \frac{25}{2} R_1$$

$$4 = 5 \times R_2 \Rightarrow 15 = \frac{15}{4} R_2$$

$$5 = -6R_3 \Rightarrow 20 = -24R_3$$

$$\text{So, } I = \frac{25}{2} + \frac{15}{4} - 4$$

$$\Rightarrow 25.5 \quad \boxed{\text{25.5 Amp is R}}$$

$$I = 25.5 \text{ Amp} \quad \boxed{\text{Answer}}$$

Teacher's Signature : _____

Method 2

\therefore As system is linear, we can also

~~do~~ do by making three eq.

$$\left. \begin{array}{l} ax_1 + by_1 + cg_1 = d_1 \\ ax_2 + by_2 + cg_2 = d_2 \\ ax_3 + by_3 + cg_3 = d_3 \end{array} \right\} a, b, c, d_1, d_2, d_3 \rightarrow \text{Variables}$$

$$a(2) + 0 + 0 = 1 \Rightarrow a = 1/2$$

$$0 + b(4) + 0 = 5 \Rightarrow b = 5/4$$

$$0 + 0 + c(5) = -6 \Rightarrow c = -6/5$$

Now, $\frac{1}{2}(2s) + \frac{5}{4}(1s) - \frac{6}{5}(20) = 7.25 \text{ Amp}$ Answer

Teacher's Signature : _____

Question - 3

~~Sol.~~

Date _____

Expt. No. _____

Page.No. _____

Question 3 : ~~As Question was given in the question paper~~

~~solutions~~

~~Sol.~~ ~~where~~ ~~eg. 2 volt~~ ~~2 volt~~
∴ The given electronic device seems to be a
volt Linear Voltage Regulator (IC - 7805)

$$\therefore \text{As, } (V_{in} - V_{out}) \geq 2$$

∴ So at least 2 volt is necessary for functioning
of this voltage regulator.

∴ Reference Node / Quiescent current (I_0) is Negligible
so, $I_0 \approx 0$.

$$\therefore (V_{out} - V_{reference}) = 5V$$

∴ Current source will deliver 0.25 current to 45Ω , ^{100W}
Regist. Resistor

$$\therefore \Rightarrow P = \frac{V^2}{R}$$

$$\therefore P = 100W, R = 45\Omega$$

$$\Rightarrow 100 = \frac{V^2}{45} \Rightarrow V^2 = 45 \times 100 \quad \boxed{0}$$

$$\Rightarrow V = \sqrt{45 \times 100} = 67.08V$$

∴ Max voltage that can appear $R = 45\Omega = 67.08V$
across


Now Designing current source :

Using ~~IC - 7805~~ IC - 7805 linear Voltage Regulator

Teacher's Signature : _____

Question 3

Sol: Linear Voltage Regulator IC - 7805

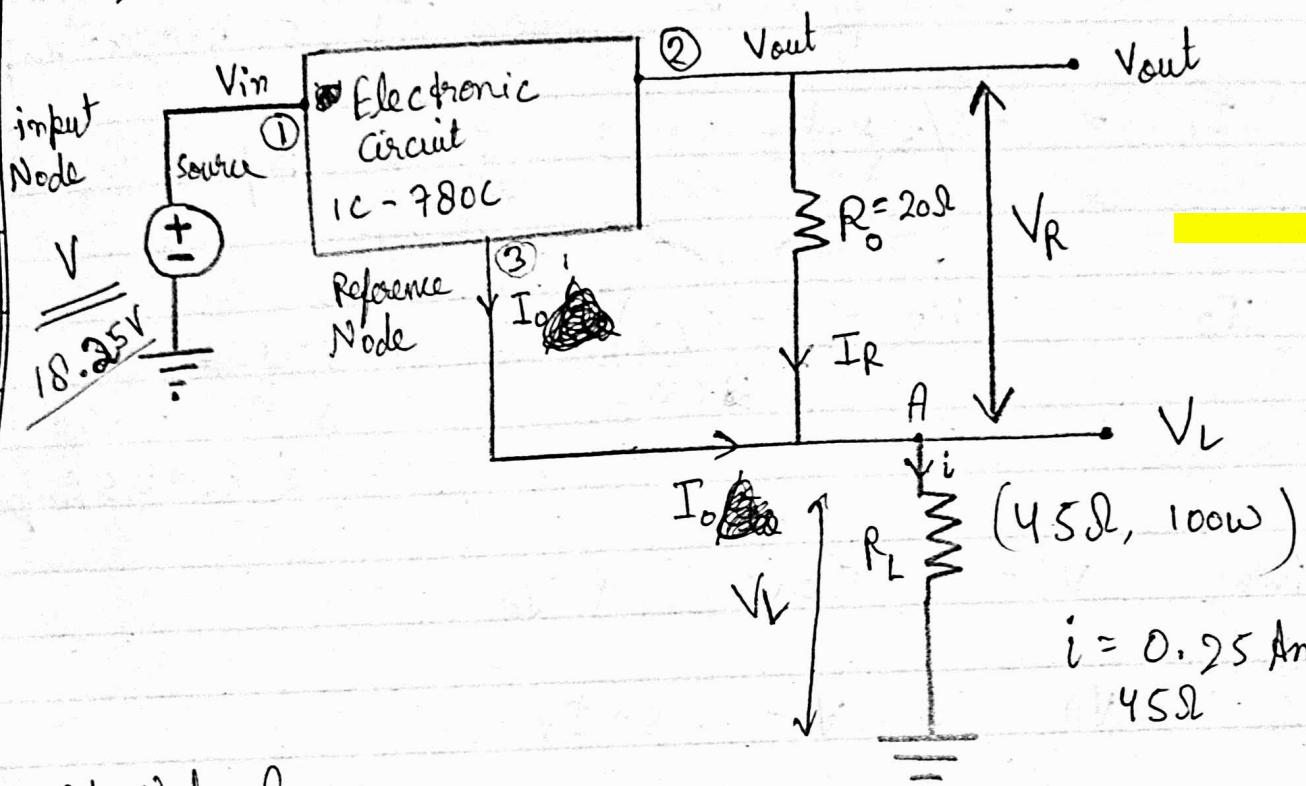

$$i = 0.25 \text{ Amp across } 45\Omega$$

At Node A

Use Nodal Analysis at A

$$\begin{cases} \text{Power} = i^2 R_L \Rightarrow \frac{1}{4} \times \frac{1}{4} \times 45 \\ = 2.0125 \text{ W} \end{cases}$$

~~i = IR + I_o~~

$$i = IR + I_o \quad \because I_o \approx 0 \text{ (given)}$$

$$i = IR + 0 \quad \because V_R = V_{23} = V_2 - V_3 = V_{out} - V_{reference}$$

$$i = IR = \frac{V_R}{R}$$

$$\therefore V_R = V_{23} = 5 \text{ Volt}$$

$$i = \frac{5}{R_o} = 0.25 = \frac{1}{4}$$

$$\Rightarrow R_o = 20\Omega$$

$$\therefore i = 0.25 \text{ Amp (given)}$$

$$\therefore \boxed{R_o = 20\Omega}$$

So, $R_o = 20\Omega$ for $i = 0.25$ across 45Ω

V_{across R_o} Load R_L ~~= 11.25~~

$$\text{V}_{\text{across } 45\Omega} = i \times R_L = \frac{1}{4} \times 45 = 11.25 \text{ V}$$

$$\text{as } 11.25 \text{ V} < 67.08 \text{ V}$$

$\therefore 67.08$ Max allowed voltage

$$\begin{aligned}\text{Output Voltage } V_{\text{out}} &= V_R + V_L \\ &= 5 + 11.25 \\ &= 16.25 \text{ V}\end{aligned}$$

$$\text{Also, } (V_{\text{in}} - V_{\text{out}}) \geq 2 \quad \because \text{given}$$

$$V_{\text{in}} \geq V_{\text{out}} + 2$$

$$V_{\text{in}} \geq 16.25 + 2$$

$$V_{\text{in}} \geq 18.25 \text{ V}$$

so, Min voltage input voltage, $V_{\text{in}} \geq 18.25 \text{ Volt}$

source referred for Ques 3

<https://www.circuitstoday.com/fixed-positive-voltage-regulators>

