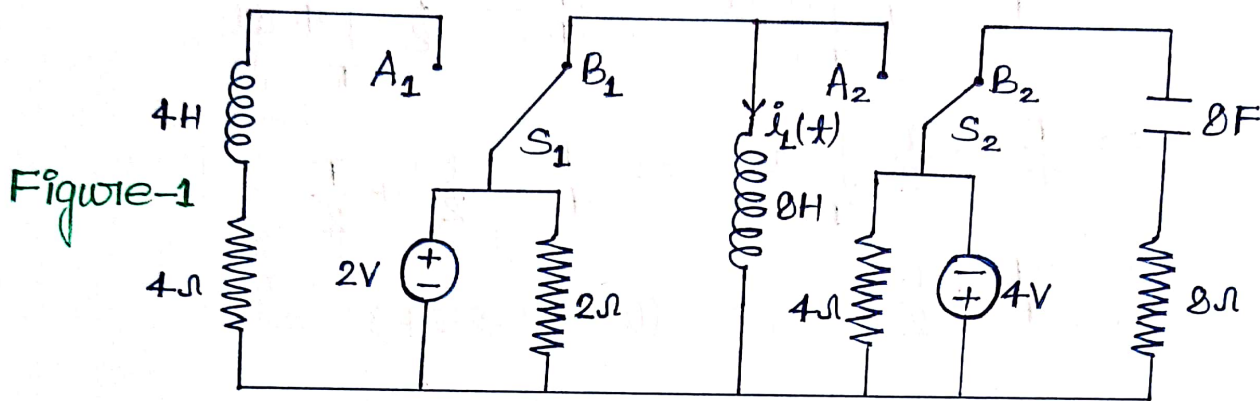


ASSIGNMENT-2 SOLUTION

SOL(1)

Case(I) : $0 \leq t < T$; switch S_1 is connected to position B_1 & switch S_2 is connected to position B_2 .



initial current through inductor = $i_L(0^-) = 0A$ (Given)

$$\therefore i_L(0) = i_L(0^+) = i_L(0^-) = 0A$$

Here inductor start charging by 2 volt source.

$$L = 8H, V = 2 \text{ volt}$$

$$\therefore i_L(t) = \frac{1}{L} \int_0^t V \cdot dt = \frac{1}{8} \int_0^t 2 \, dt = \frac{1}{4} \int_0^t dt = \left(\frac{t}{4} \right)$$

$$\therefore \text{at } t = T; i_L(T) = \frac{T}{4}$$

— (a)
(2.25 P)

Case(II) : $T \leq t < 2T$; switch S_1 is connected to position A_1 & switch S_2 is connected to position A_2 .

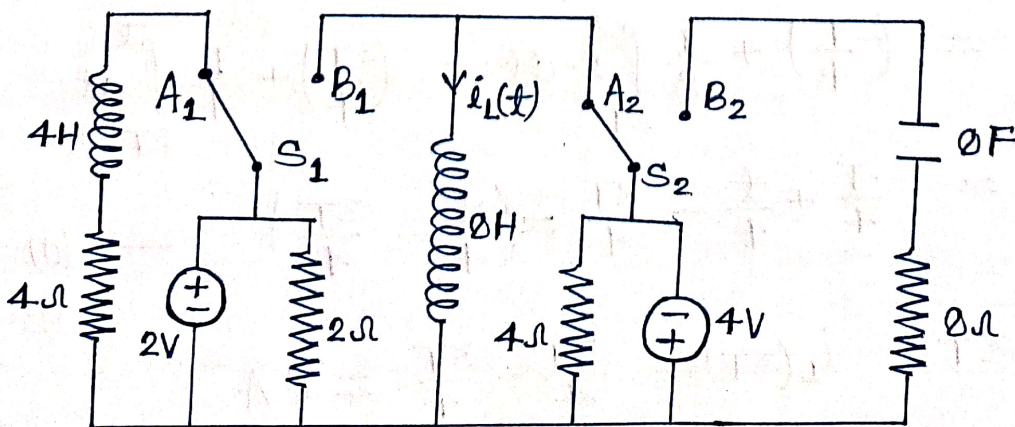


Figure-2

initial current through inductor = $i_L(t) = \frac{T}{4}$

Here inductor start charging in opposite direction by 4V source.

$$L = 8H, \quad V = 4 \text{ volt}$$

$$\begin{aligned} \therefore i_L(t) &= \frac{T}{4} - \frac{1}{L} \int_T^t V \cdot dt = \frac{T}{4} - \frac{1}{8} \int_T^t 4 \, dt \\ &= \frac{T}{4} - \frac{1}{2} \int_T^t dt = \frac{T}{4} - \frac{t}{2} + \frac{T}{2} \\ &= \left(\frac{3T}{4} - \frac{t}{2} \right) \quad \text{--- (b) (2.25 P)} \end{aligned}$$

$$\therefore \text{at } t = 2T; \quad i_L(2T) = \frac{3T}{4} - \frac{2T}{2} = \left(-\frac{T}{4} \right)$$

Case (III) : $2T \leq t < 3T$; switch S_1 is connected to position B_1 & switch S_2 is connected to position B_2 .

By using Figure-1,

initial current through inductor = $i_L(2T) = \left(-\frac{T}{4} \right)$

Here inductor start charging by 2V source.

$$L = 8H, \quad V = 2 \text{ volt}$$

$$\begin{aligned} \therefore i_L(t) &= i_L(2T) + \frac{1}{L} \int_{2T}^t V \, dt \\ &= \left(-\frac{T}{4} \right) + \frac{1}{8} \int_{2T}^t 2 \cdot dt = \left(-\frac{T}{4} \right) + \frac{1}{4} \int_{2T}^t dt \\ &= -\frac{T}{4} + \frac{t}{4} - \frac{2T}{4} = \left(\frac{t}{4} - \frac{3T}{4} \right) \quad \text{--- (c) (2.25 P)} \end{aligned}$$

$$\therefore \text{at } t = 3T; \quad i_L(3T) = \frac{3T}{4} - \frac{3T}{4} = 0A$$

Case(IV) $\div 3T \leq t < 4T$; switch S_1 is connected to position A_1 & switch S_2 is connected to position A_2 .

By using Figure-2,

initial current through inductor $= i_L(3T) = 0 \text{ A}$

Here inductor start charging by 4V source in opposite direction.

$$L = 8 \text{ H}, V = 4 \text{ Volt}$$

$$\therefore i_L(t) = i_L(3T) - \frac{1}{L} \int_{3T}^t V dt$$

$$= 0 - \frac{1}{8} \int_{3T}^t 4 dt = -\frac{1}{2} \int_{3T}^t dt$$

$$= -\frac{1}{2}(t - 3T) = \frac{3T}{2} - \frac{t}{2} \quad \text{--- (d) (2.25 P)}$$

$$\therefore \text{at } t = 4T; i_L(4T) = \frac{3T}{2} - \frac{4T}{2} = \left(-\frac{T}{2}\right)$$

Case(V) $\div 4T \leq t < 5T$; switch S_1 is connected to position B_1 & switch S_2 is connected to position B_2 .

By using Figure-1,

initial current through inductor $= i_L(4T) = \left(-\frac{T}{2}\right)$

$$L = 8 \text{ H}, V = 2 \text{ Volt}$$

$$\therefore i_L(t) = i_L(4T) + \frac{1}{L} \int_{4T}^t V dt = \left(-\frac{T}{2}\right) + \frac{1}{8} \int_{4T}^t 2 dt$$

$$= -\frac{T}{2} + \frac{1}{4} \int_{4T}^t dt = -\frac{T}{2} + \frac{t}{4} - T = \frac{t}{4} - \frac{3T}{2} \quad \text{--- (e)}$$

$$\therefore i_L(5T) = \frac{5T}{4} - \frac{3T}{2} = \left(\frac{T}{4}\right)$$

Now, $\hat{i}_L(t) = eq^n(a) + eq^n(b) + eq^n(c) + eq^n(d) + eq^n(e) + \dots$

$$\therefore \hat{i}_L(t) = \frac{1}{4} \pi(t) - \frac{1}{2} \pi(t-T) + \frac{1}{4} \pi(t-2T) - \frac{1}{2} \pi(t-3T) + \frac{1}{4} \pi(t-4T) - \frac{1}{2} \pi(t-5T) + \dots$$


$$= \frac{1}{4} \left\{ t u(t) + (t-2T) \cdot u(t-2T) + (t-4T) u(t-4T) + \dots \right\} \\ - \frac{1}{2} \left\{ (t-T) u(t-T) + (t-3T) u(t-3T) + (t-5T) u(t-5T) + \dots \right\}$$

$$= \frac{1}{4} \sum_{n=0}^{\infty} (t-2nT) \cdot u(t-2nT) \\ - \frac{1}{2} \sum_{n=0}^{\infty} [t-(2n+1)T] \cdot u[t-(2n+1)T]$$

$\rightarrow (1 P)$

SOL(2):

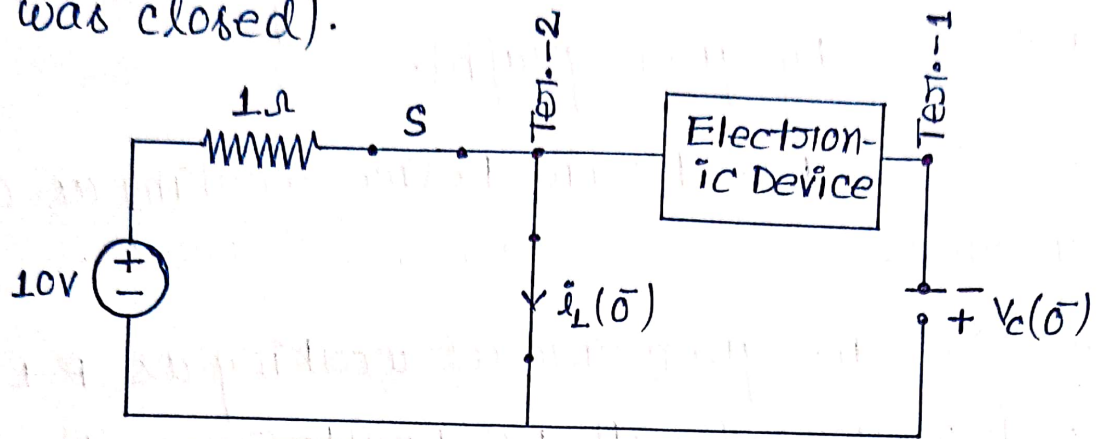Step(I): Analysis of circuit at $t=0^-$ (when switch was closed).




at $t=0^-$ (steady state),
Inductor behave as a Short Circuit, Hence—

$$i_L(0^-) = \left(\frac{10}{1}\right) = 10A \quad \rightarrow (1P)$$

Capacitor behave as a Open Circuit, Hence—
 $V_C(0^-) = 0$ volt

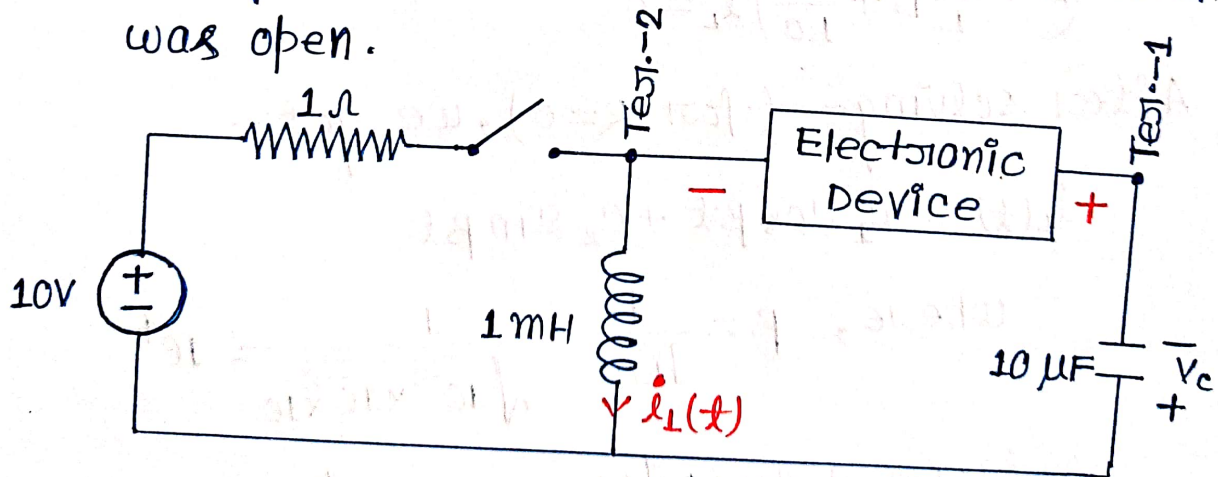Step(II): Analysis of circuit at $t>0$ (when switch was open).



at $t=0^+$ (Transient state)

$$i_L(0^+) = i_L(0^-)$$

$$i_L(0^+) = 10A$$

[Inductor does not allow sudden change of current] $\rightarrow (1P)$

When Terminal-1 of Electronic Device is positive & Terminal-2 of Electronic Device is Negative then Electronic Device working as a Short Circuit (By given graph).

at $t > 0$, Electronic Device working as a Short Circuit.

at $t > 0$, the given circuit working as R-L-C series circuit with DC Excitation. where —

$R = 0$ (Undamping condition)

General differential eqⁿ for series R-L-C circuit —

$$\frac{d^2 i_L}{dt^2} + \frac{R}{L} \frac{di_L}{dt} + \frac{i_L}{LC} = 0$$

$$D^2 i_L + \frac{R}{L} D i_L + \frac{i_L}{LC} = 0$$

$$\left(D^2 + \frac{R}{L} D + \frac{1}{LC}\right) i_L = 0$$

After solving — (for $R = 0$), we get —

$$i_L(t) = C_1 \cos \beta t + C_2 \sin \beta t$$

$$\text{where, } \beta = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{10^{-3} \times 10^{-6} \times 10}} = 10^4$$

$$\therefore i_L(t) = C_1 \cos(10^4 t) + C_2 \sin(10^4 t) \quad \text{--- (1)}$$

$$\therefore \text{at } t = 0^+, i_L(0^+) = i_L(0) = 10A$$

$$\text{at } t = \infty, i_L(\infty) = 0A$$

IVE

$$\therefore C_1 = 10 \text{ \& } C_2 = 0$$

$$\text{Hence, } i_L(t) = 10 \cos(10^4 t) \text{ A} \quad \rightarrow (5P)$$

$$\therefore \text{Voltage across capacitor, } V_C(t) = \frac{1}{C} \int i_L(t) \cdot dt$$
$$V_C(t) = \left(\frac{1}{10 \times 10^{-6}} \right) \int 10 \cdot \cos(10^4 t) dt = 100 \cdot \sin(10^4 t) \text{ V}$$
$$\rightarrow (2P)$$

$$\therefore \text{Steady state magnitude voltage across capacitor } (t \rightarrow \infty) = 100 \text{ volt} \quad \rightarrow (1P)$$