

Assignment-2

Winter 2024

Basic Electronics (ECE113)

Instructions

- **Institute Plagiarism Policy Applicable.** This will be subjected to strict plagiarism check.
- This assignment should be attempted individually.
- A maximum point for this assignment is **20**. All questions are compulsory.
- **File Submission:** Only a *.pdf* file are acceptable, which you have to submit on Google Classroom. Use A4 size sheets only (ruled or blank) to solve your assignment and scan it to create a *.pdf* file. Attempt each question on a different sheet. Do not start a new question at the back of the previous one. Do not forget to mention Page Number (bottom center) clearly on each sheet of the assignment. Submit a *.pdf* file named *A1_RollNo.pdf* (e.g., *A1_PhD22100.pdf*), which containing the quality scan copy of your solved assignment.
- **Submission Policy:** Turn-in your submission as early as possible to avoid late submissions. In case of multiple submissions, the latest submission will be evaluated. Expect **No Extensions**. Late submissions will not be evaluated and hence will be awarded zero marks strictly.
- **Clarifications:** Symbols have their usual meaning. Assume the missing information & mention it in the report. Use Google Classroom for any queries. In order to keep it fair for all, no email queries will be entertained.
- There could be multiple ways to approach a question. Please justify your answers. Questions without justification will get zero marks.

[CO3] Q1: [10 Points] Two voltage sources are used to charge the inductor **8 H** alternately as indicated in the circuit shown in Figure-1. The switches **S₁** and **S₂** are mechanically coupled and connected as follows:

- For time interval $2nT \leq t < (2n+1)T$, where $n=0,1,2,3,\dots$ switch **S₁** is connected to position **B₁** and switch **S₂** is connected to position **B₂**
- For time interval $(2n+1)T \leq t < (2n+2)T$, where $n=0,1,2,3,\dots$ switch **S₁** is connected to position **A₁** and switch **S₂** is connected to position **A₂**

Assume that the inductor has zero initial current. Find the value of current across inductor $i_L(t)$ for all time interval.

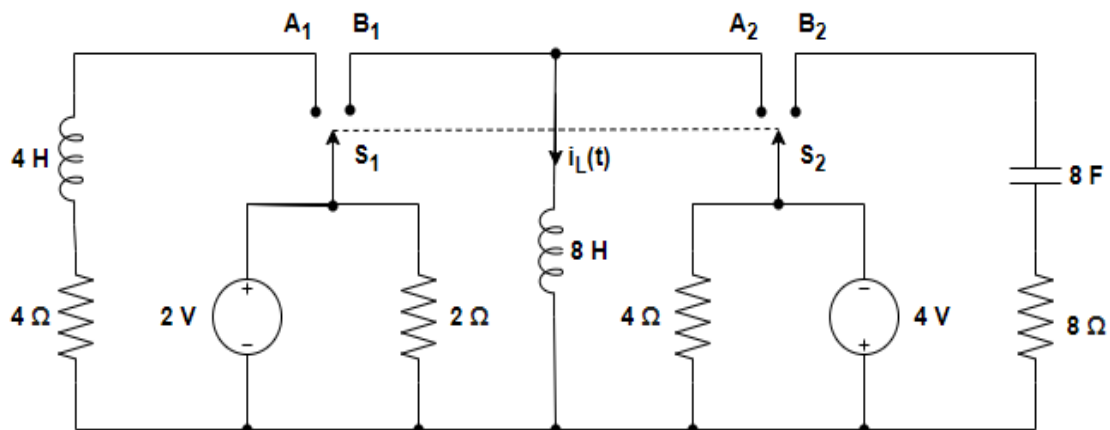


Figure 1

[CO3] Q2: [10 Points] In the given following circuit (Figure-2), the switch **S** was closed for a long time. The switch **S** is opened at time $t=0$. An electronic device **V – I** characteristic is given in Figure-3 with respect to its assigned terminal (Terminal-1 and Terminal-2). Do-

- Find the capacitor voltage $V_c(t)$ for $t \geq 0^+$
- Find the steady state magnitude of the capacitor voltage V_c (in volts).

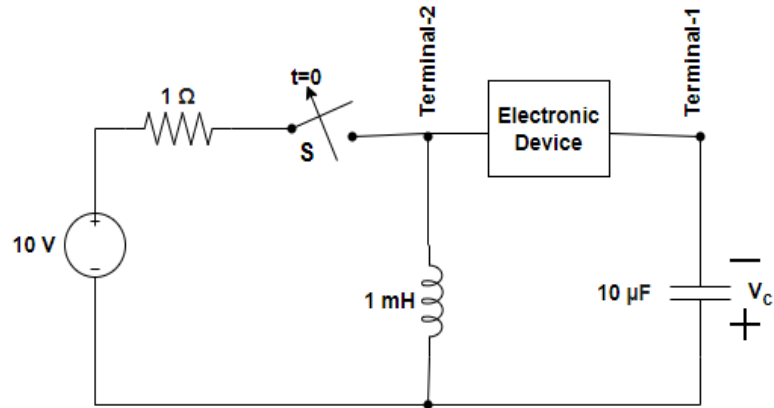


Figure 2

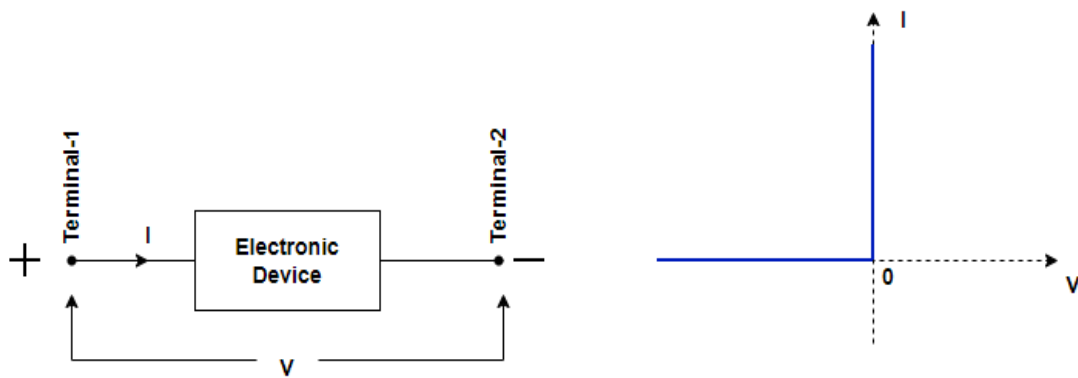


Figure 3

Note: At $t=0^-$, current through electronic device is 0 A.