

2024 - BE END SEMESTER EXAM.

SOLUTION

SOL(1) $\frac{0}{0}$

(a) For const current through 'a', op-amp must be in saturation.
Set-A:

For non-inverting op-amp,

$$V_o = \left(1 + \frac{R_F}{R_1}\right) V_{in}$$

$$\pm 12 = \left(1 + \frac{a}{1}\right)_2$$

$$\therefore a = 5\text{ k}\Omega, -7\text{ k}\Omega \rightarrow (2 \text{ POINT})$$

Hence, for const current through 'a', $a \leq 5\text{ k}\Omega$
 $\rightarrow (2 \text{ POINT})$

Set(B):

For non-inverting op-amp,

$$V_o = \left(1 + \frac{R_F}{R_1}\right) V_{in}$$

$$\pm 15 = \left(1 + \frac{a}{1}\right)_3$$


$$\therefore a = 4\text{ k}\Omega, -6\text{ k}\Omega \rightarrow (2 \text{ POINT})$$

Hence, for const current through 'a', $a \leq 4\text{ k}\Omega$
 $\rightarrow (2 \text{ POINT})$

Set(B) :-

Forward Voltage (V_f) & Forward resistance (R_f) will be same as Set(A).

Given circuit can be redrawn as -

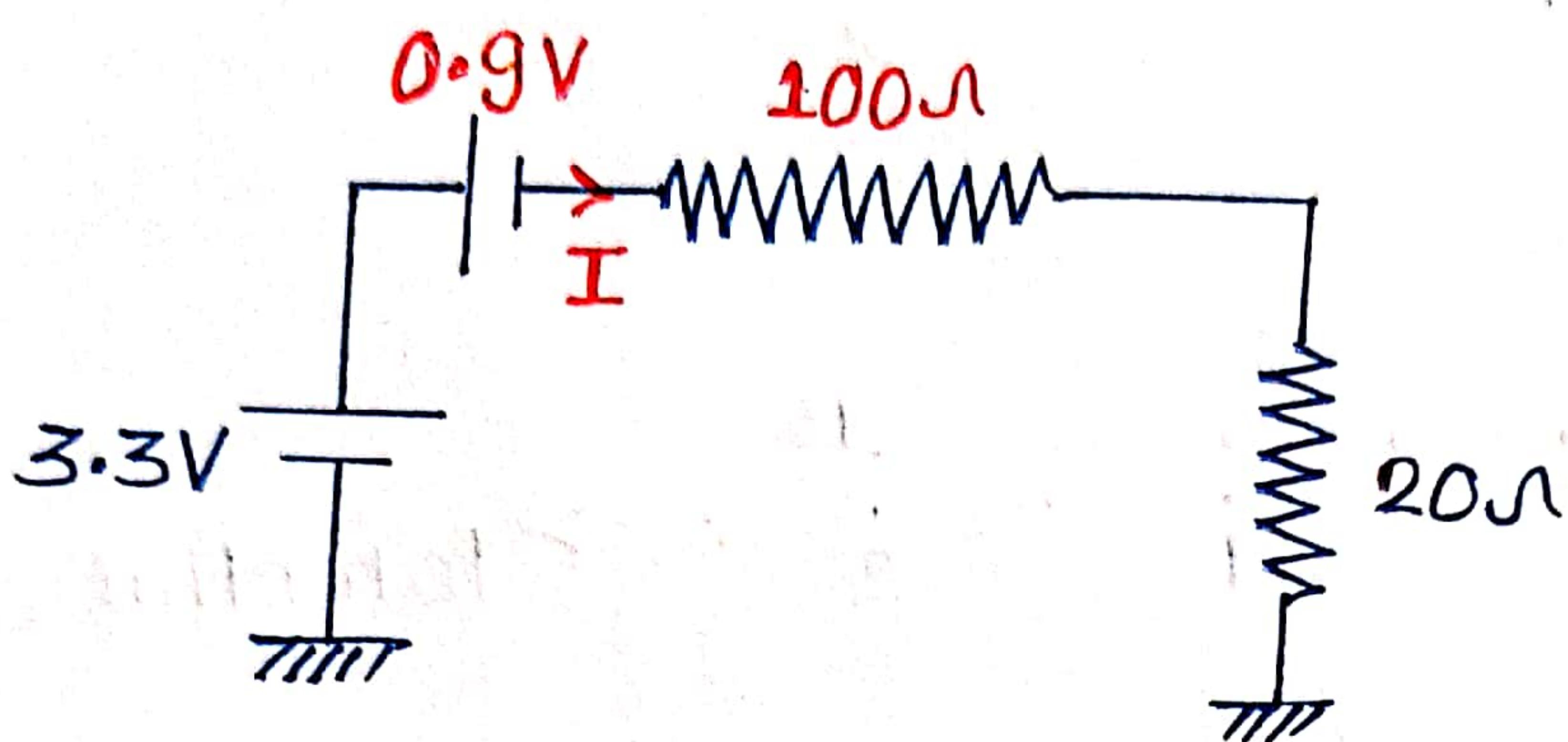


$$\therefore \text{Current, } I = \frac{(3.3 - 0.9)}{(100 + 20)} = 0.02 \text{ A} = 20 \text{ mA}$$

$\rightarrow (2 \text{ POINT})$

SOL(5) :-

Set(A) :-

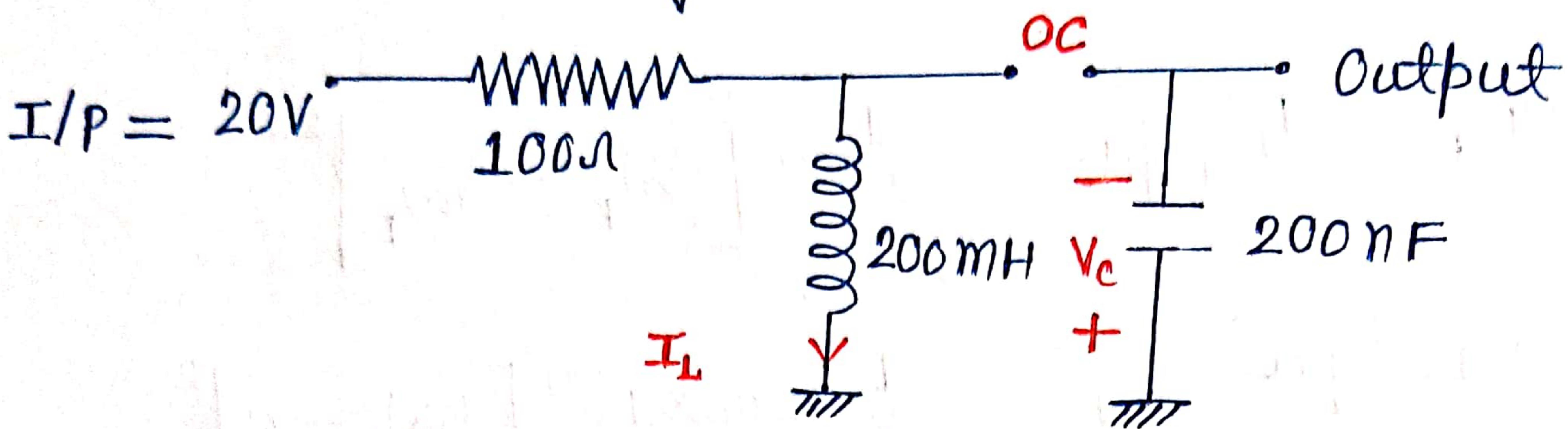Case-I : When 20V voltage source applied at the input.




At Steady state -

$$\text{Initial Current through inductor}, (I_L)_{\text{initial}} = \frac{20}{100} = 0.2 \text{ A}$$

$$\text{Initial voltage across capacitor}, (V_c)_{\text{initial}} = 0 \text{ V}$$

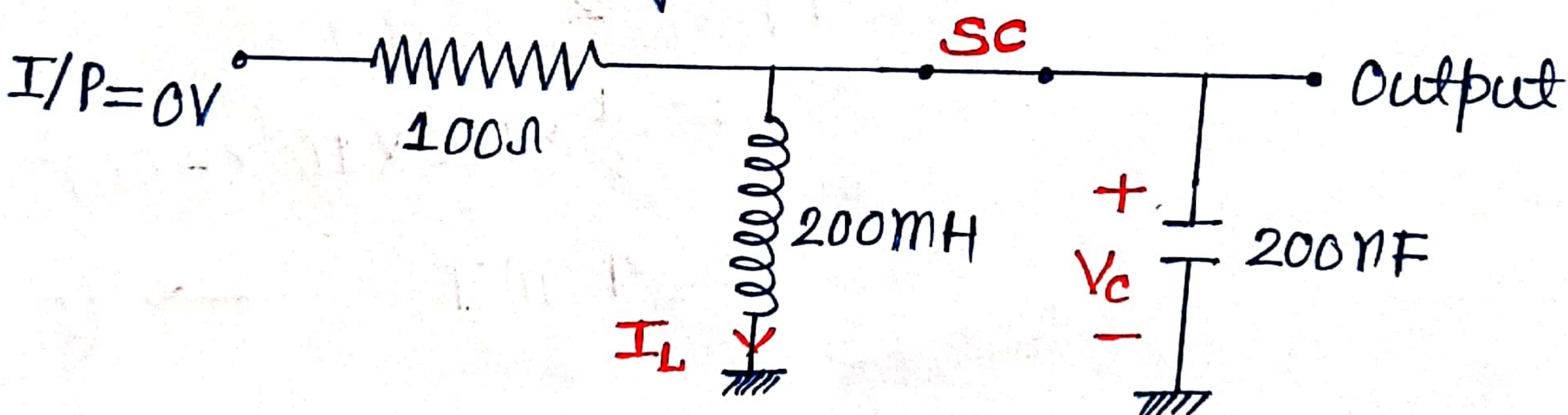Case-II : When suddenly source was removed



At steady state -

$$\text{Final current through inductor}, (I_L)_{\text{final}} = 0 \text{ A}$$

$$\text{Final voltage across capacitor}, (V_c)_{\text{final}} = (V_c)_F$$

NOTE : In Case-II, diode will work as short circuit, until capacitor fully charged by the initial value of inductor current. After that diode will work as open circuit & there will be no flow of current. (apply for both sets)

Here,

$$\left(\begin{array}{l} \text{(Energy transferred by} \\ \text{Inductor} \end{array} \right) = \left(\begin{array}{l} \text{(Energy received by} \\ \text{Capacitor} \end{array} \right)$$

$$\frac{1}{2} L \left[(I_L)_F - (I_L)_I \right]^2 = \frac{1}{2} C \left[(V_C)_F - (V_C)_I \right]^2$$

$$\frac{1}{2} \times 200 \times 10^{-3} [0 - 0.2]^2 = \frac{1}{2} \times 200 \times 10^9 [(V_C)_F - 0]^2$$

$$\therefore (V_C)_F = 200 \text{ Volt}$$

\therefore Voltage at the output after long time (steady state),
 $= -(V_C)_F = (-200) \text{ Volt}$ → (4 POINT)

\therefore Amount of stored energy $= \frac{1}{2} C V^2$

$$= \frac{1}{2} \times 200 \times 10^9 \times (200)^2$$

$$= 4 \text{ mJ} \quad \rightarrow (2 \text{ POINT})$$

Set(B) :-

Case-I: When 10V voltage source applied at the input for long time.

At steady state,

Initial current through inductor, $(I_L)_I = \frac{10}{100} = 0.1 A$

Initial voltage across capacitor, $(V_C)_I = 0 V$

Case-II: When suddenly source was removed.

At steady state,

Final current through inductor, $(I_L)_F = 0 A$

Final voltage across capacitor, $(V_C)_F = ?$

Here,

$$\left(\begin{array}{l} \text{Energy transferred by} \\ \text{Inductor} \end{array} \right) = \left(\begin{array}{l} \text{Energy received by} \\ \text{Capacitor} \end{array} \right)$$

$$\frac{1}{2} L [(I_L)_F - (I_L)_I]^2 = \frac{1}{2} C [(V_C)_F - (V_C)_I]^2$$

$$\frac{1}{2} \times 200 \times 10^{-3} [0 - 0.1]^2 = \frac{1}{2} \times 200 \times 10^{-9} [(V_C)_F - 0]^2$$

$$\therefore (V_C)_F = 100 \text{ Volt}$$

∴ Voltage at the output after long time (steady state),
 $-(V_C)_F = -100 \text{ Volt}$ → (4 POINT)

∴ Amount of stored energy = $\frac{1}{2} CV^2$

$$= \frac{1}{2} \times 200 \times 10^{-9} \times (-100)^2$$

$$= 1 \text{ mJ}$$

→ (2 POINT)

SOL(6)

Each resistor is rated to a maximum of 250 mW. If the circuit allows this value to be exceeded, excessive heating will occur.

The max^m current the 100Ω resistor can tolerate is

$$\sqrt{\frac{P_{\max}}{R}} = \sqrt{\frac{0.250}{100}} = 50 \text{ mA}$$


The max^m current the 64Ω resistor can tolerate is

$$\sqrt{\frac{P_{\max}}{R}} = \sqrt{\frac{0.250}{64}} = 62.5 \text{ mA}$$


Using Superposition,

Consider only 6V source -
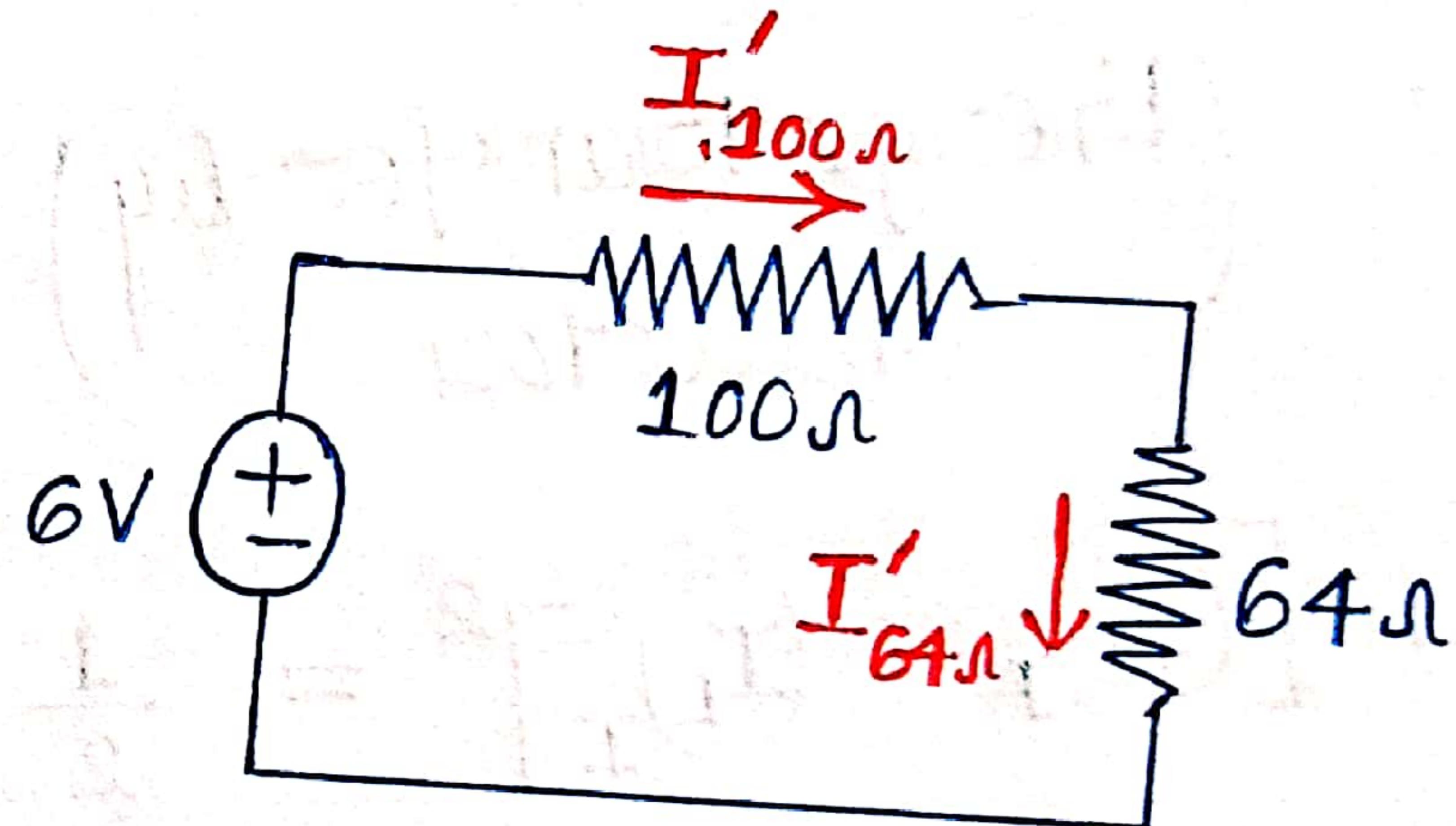
$$I'_{100\Omega} = I'_{64\Omega} = \frac{6}{100+64} = 36.59 \text{ mA}$$



Consider only I_x source -

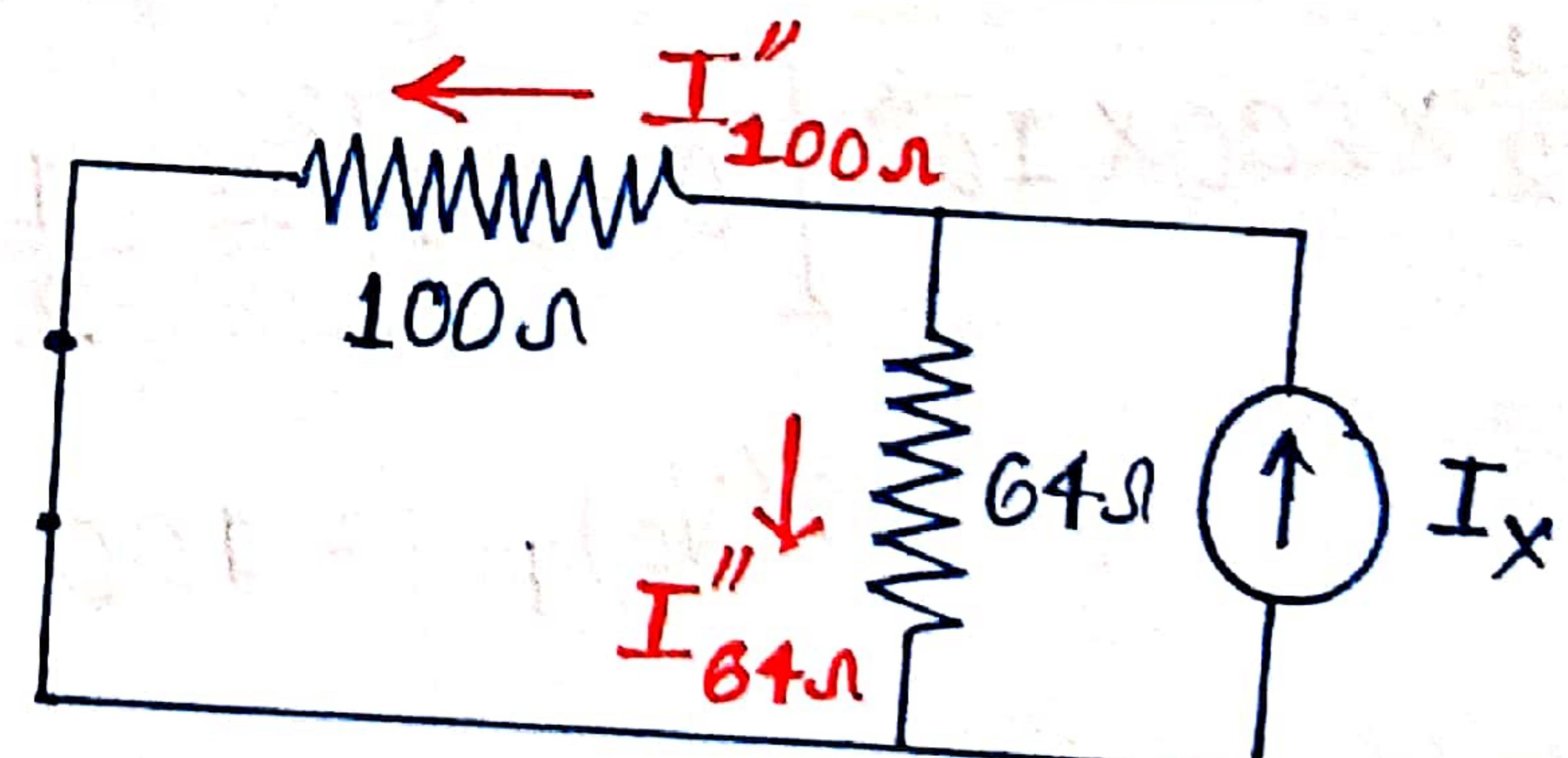

We note that -

Current through 100Ω resistor = ($I'_{100\Omega} \sim I''_{100\Omega}$)

Current through 64Ω resistor = ($I'_{64\Omega} + I''_{64\Omega}$)

Therefore, I_x can safely contribute $(62.5 - 36.59)$ mA
 $= 25.91$ mA to the 64Ω resistor, and $(50 + 36.59)$ mA

= 86.59 mA equivalent to the 100 Ω resistor.

∴ Constraint of I_x by 100 Ω resistor,

$$I_x < (86.59 \times 10^{-3}) \left(\frac{100+64}{64} \right)$$

$$I_x < 221.88 \text{ mA}$$


∴ Constraint of I_x by 64 Ω resistor,

$$I_x < 42.49 \text{ mA}$$

∴ Overall constraint on I_x will be —

$$I_x < 42.49 \text{ mA} \rightarrow (6 \text{ POINT})$$

SOL(7)

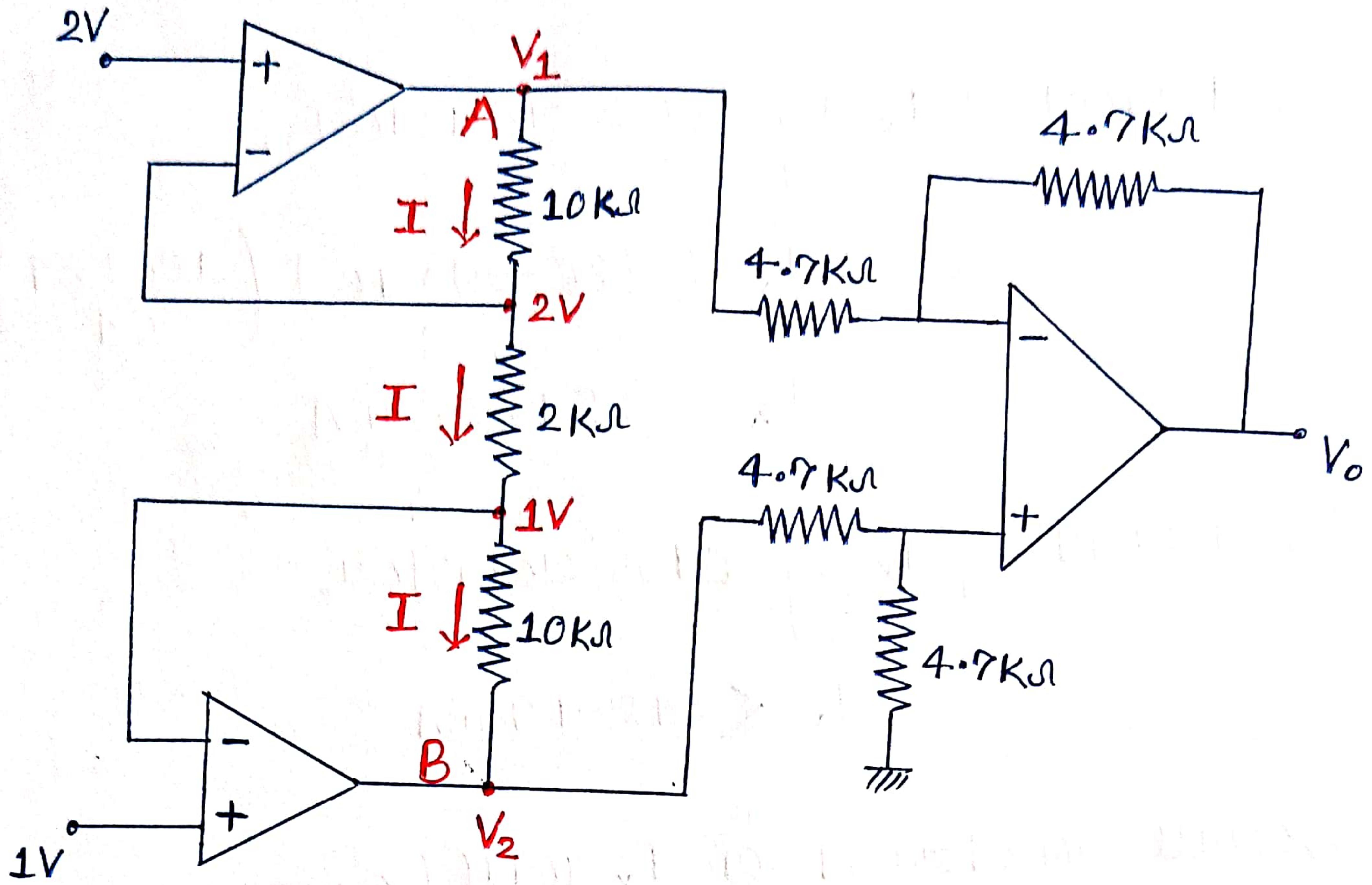

$$V_o = \left(-\frac{4.7}{4.7}\right)V_1 + \left(1 + \frac{4.7}{4.7}\right)\left(\frac{4.7}{4.7+4.7}\right)V_2$$

$$V_o = -V_1 + 2 \times 0.5 V_2$$

$$V_o = -V_1 + V_2 \quad \text{--- (1)}$$

By given circuit — $I = \left(\frac{2-1}{2 \times 10^3}\right) = 0.5 \text{ mA}$

$$\frac{V_1 - 2}{10 \times 10^3} = I$$

$$\therefore V_1 = 2 + 10^4 \times 0.5 \times 10^{-3} = 7 \text{ Volt} \rightarrow (2 \text{ POINT})$$


$$\frac{1 - V_2}{10 \times 10^3} = I$$

$$\therefore V_2 = 1 - 10^4 \times 0.5 \times 10^{-3} = -4 \text{ Volt} \rightarrow (2 \text{ POINT})$$

By eqⁿ(1), $V_o = -7 - 4 = -11 \text{ Volt} \rightarrow (2 \text{ POINT})$

SOL(B):

Circuit analysis at $t < 0$

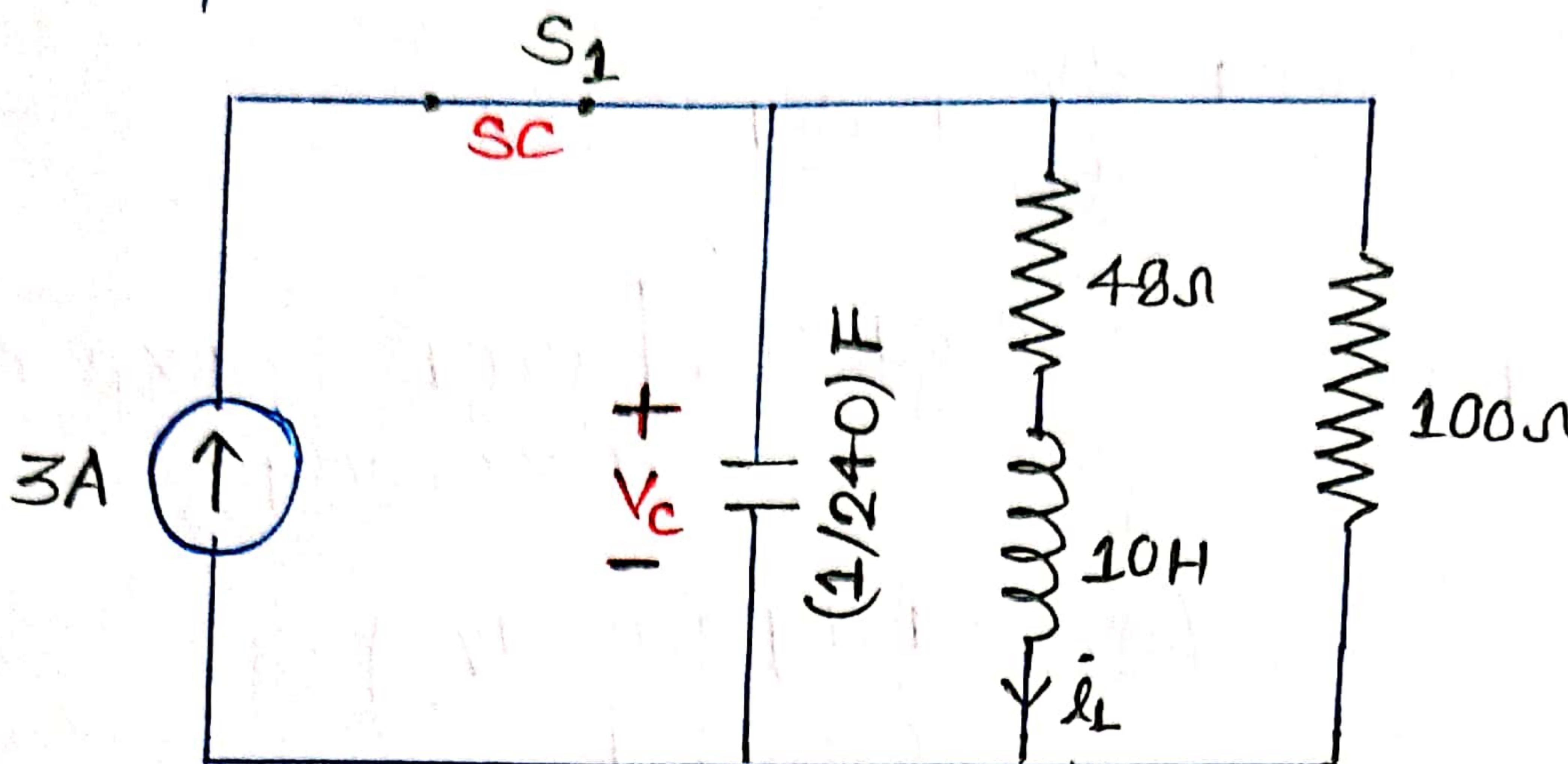


at steady state — $i_L(0^-) = \left(\frac{100}{100+48}\right) 3 = 2.02 \text{ A}$

→ (0.5 POINT)

$$v_c(0^-) = 97.29 \text{ V}$$

Circuit analysis at $t > 0$

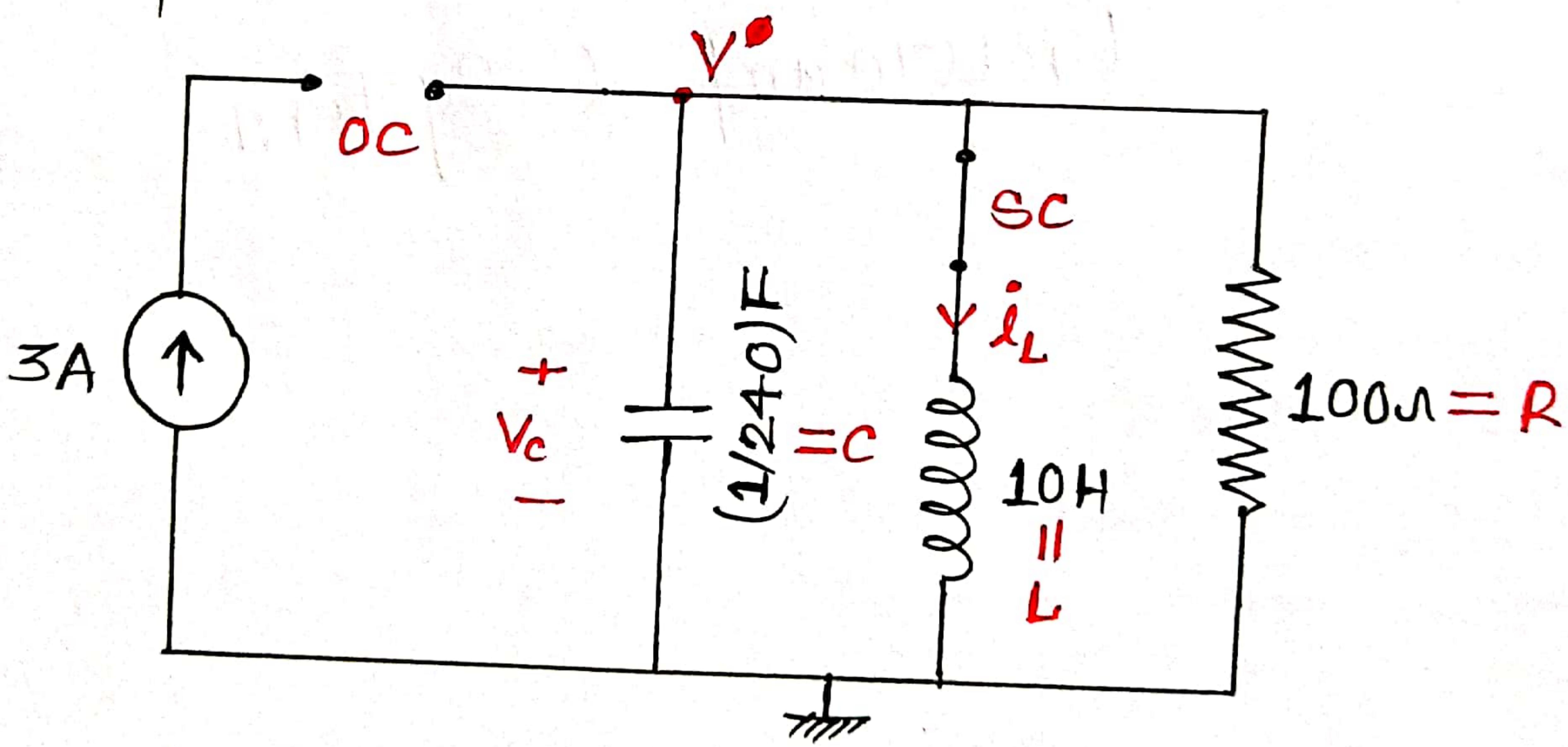

By nodal analysis, we can write —

$$\frac{V}{R} + \frac{1}{L} \int_0^t V dt - i_L(0) + C \frac{dV}{dt} = 0 \quad (1)$$

Here, $V = v_L = L \frac{di_L}{dt}$ — (2)

By eqn(1) & eqn(2), we can write —

$$\frac{L}{R} \frac{d\dot{i}_L}{dt} + \frac{1}{L} \times L \dot{i}_L - i_L(0) + LC \frac{d^2 \dot{i}_L}{dt^2} = 0$$

$$LC \frac{d^2 \dot{i}_L}{dt^2} + \frac{L}{R} \frac{d\dot{i}_L}{dt} + i_L = i_L(0)$$

$$0.042 \frac{d^2 \dot{i}_L}{dt^2} + 0.1 \frac{d\dot{i}_L}{dt} + i_L = 2.02 \quad \rightarrow (4 \text{ POINT})$$

$$\text{Roots, } S_{1,2} = \frac{-0.1 \pm \sqrt{0.1^2 - 4 \times 0.042 \times 1}}{2 \times 0.042}$$

$$= \frac{-0.1 \pm j0.40}{0.084}$$

$$= (-1.19 \pm j4.76)$$



Roots are purely imaginary }



Underdamped System

→ (1.5 POINT)

(b)

case

Set(A):

$$V_o = \left(1 + \frac{R_F}{R_1}\right) V_{in}$$

$$= \left(1 + \frac{2}{1}\right) 2 = 6V$$

Hence, current flowing through resistor 'a' will be
 $= \frac{(6-2)}{2} = 2mA$ → (2 POINT)

Set(B):

$$V_o = \left(1 + \frac{R_F}{R_1}\right) V_{in}$$

$$= \left(1 + \frac{2}{1}\right) 3 = 9V$$

Hence, current flowing through resistor 'a' will be -

$$= \frac{(9-3)}{2} = 3mA$$

→ (2 POINT)

SOL(2)


According to given characteristic of diode,

Forward voltage drop across diode / cut-in voltage,

$$V_x = 1 \text{ Volt}$$

Forward resistance, $R_f = 0$


Case(I): When input voltage = +10V

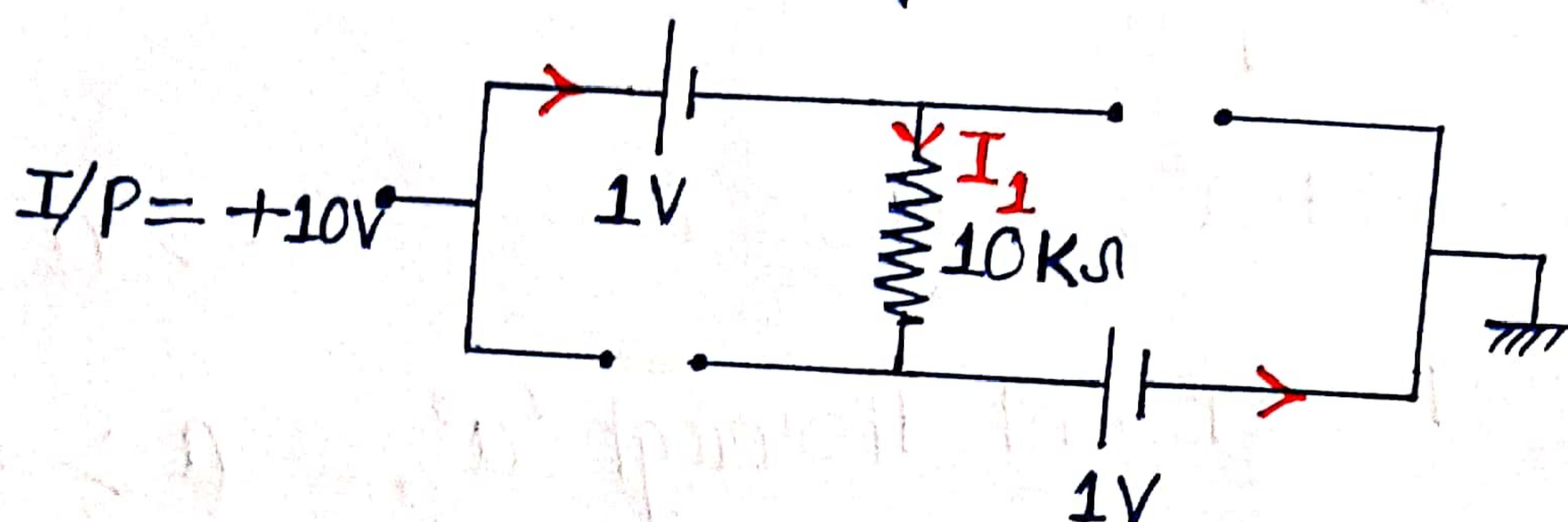

$$\therefore \text{Current, } I_1 = \left(\frac{10 - 1 - 1}{10 \times 10^3} \right) = 0.8 \text{ mA} \rightarrow (1 \text{ POINT})$$

$$\begin{aligned} \therefore \text{Power used by diodes} &= \text{voltage drop} \times \text{Current} \\ &= (1+1) \times 0.8 = 1.6 \text{ mW} \rightarrow (1.5 \text{ POINT}) \end{aligned}$$

Case(II): When input Voltage = -10V

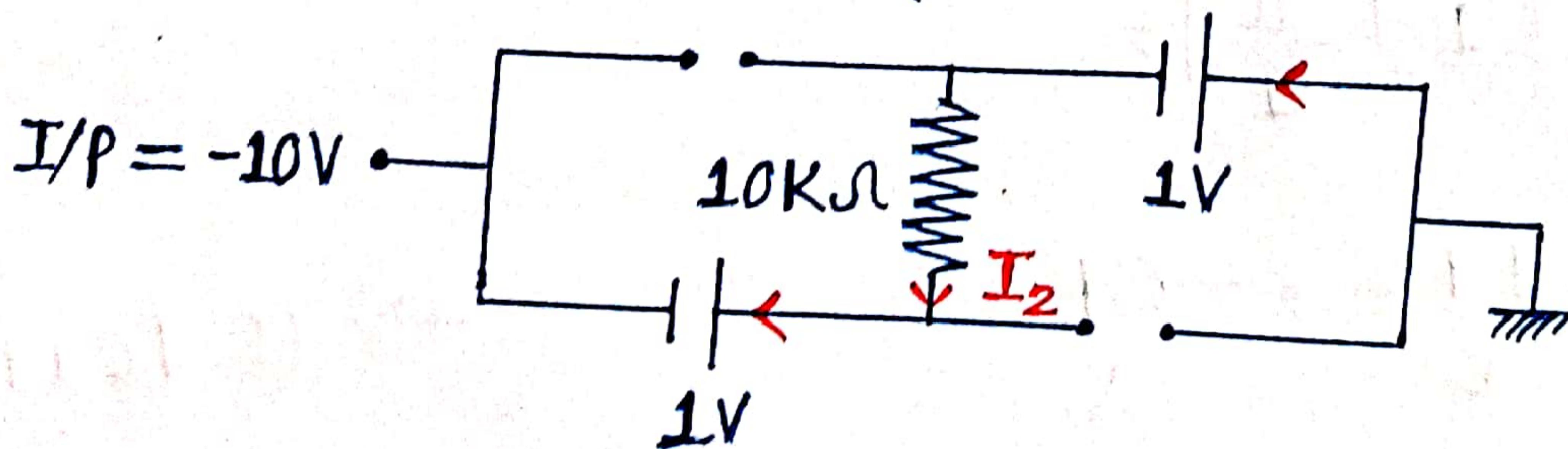

$$\therefore \text{Current, } I_2 = \left(\frac{10 - 1 - 1}{10 \times 10^3} \right) = 0.8 \text{ mA} \rightarrow (1 \text{ POINT})$$

$$\begin{aligned} \therefore \text{Power used by diodes} &= \text{voltage drop} \times \text{Current} \\ &= (1+1) \times 0.8 = 1.6 \text{ mW} \rightarrow (1.5 \text{ POINT}) \end{aligned}$$

Conclusion: We can see that power used over one time period is constant & it will remain same for all time period.

$$\therefore \text{Amount of energy used in one second} = P \times t$$


$$= 1.6 \times 1$$

$$= 1.6 \text{ mJ}$$

$$\rightarrow (1 \text{ POINT})$$

Set(B):


Case(I): When input voltage = +12V

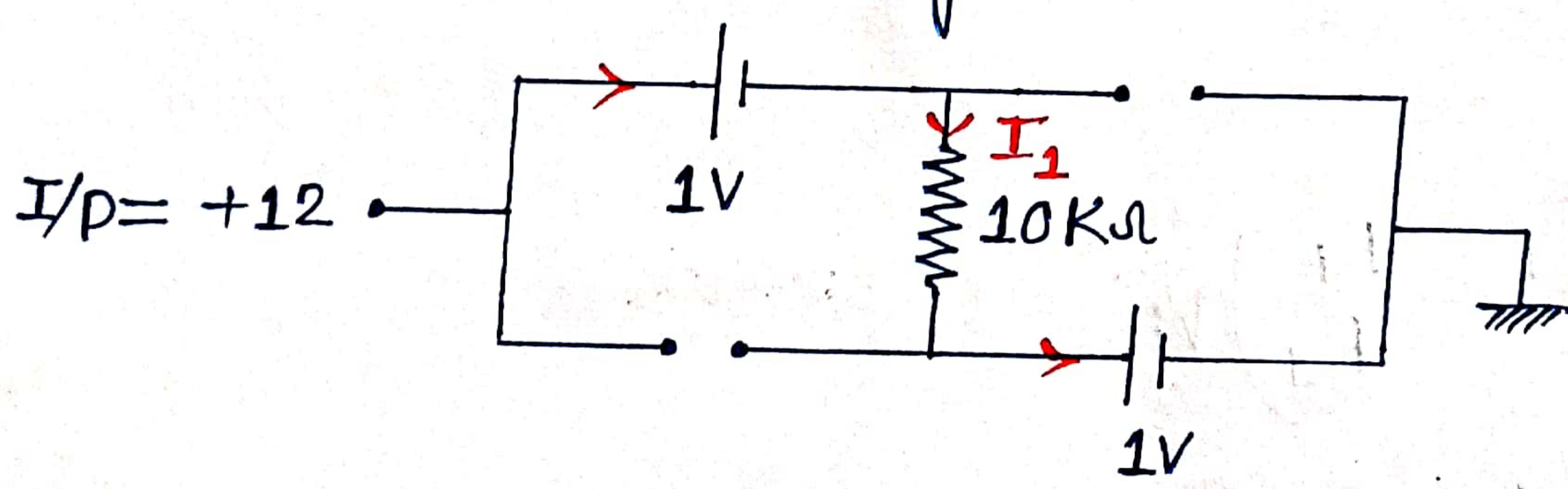

$$\therefore \text{Current, } I_1 = \left(\frac{12 - 1 - 1}{10 \times 10^3} \right) = 1 \text{ mA} \rightarrow (1 \text{ POINT})$$

$$\begin{aligned} \therefore \text{Power used by diodes} &= \text{voltage drop} \times \text{current} \\ &= (1+1) \times 1 = 2 \text{ mW} \rightarrow (1.5 \text{ POINT}) \end{aligned}$$

Case(II): When input voltage = -12V

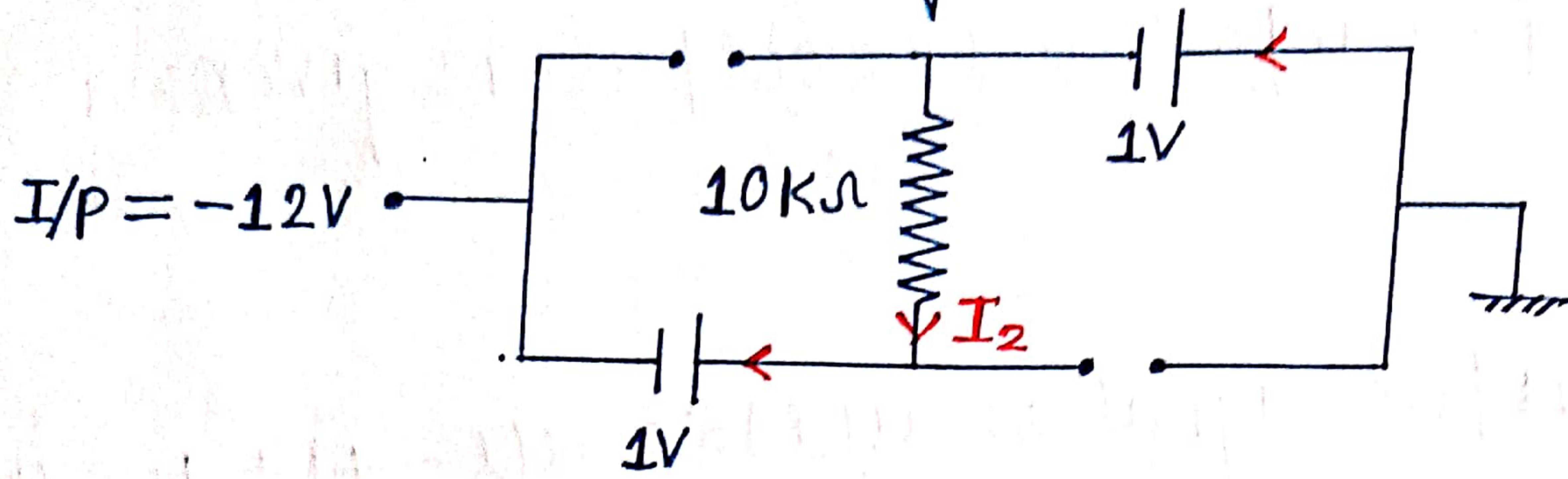

$$\therefore \text{Current, } I_2 = \left(\frac{12 - 1 - 1}{10 \times 10^3} \right) = 1 \text{ mA} \rightarrow (1 \text{ POINT})$$

$$\begin{aligned} \therefore \text{Power used by diodes} &= \text{Voltage drop} \times \text{Current} \\ &= (1 + 1) \times 1 = 2 \text{ mW} \rightarrow (1.5 \text{ POINT}) \end{aligned}$$

Conclusion: We can see that power used over one time period is constant & it will remain same for all time period.

$$\begin{aligned} \therefore \text{Amount of energy used in one second} &= P \times t = 2 \times 1 \\ &= 2 \text{ mJ} \rightarrow (1 \text{ POINT}) \end{aligned}$$


SOL(3)

By question, for input $u(t)$, output is given.

Set(A)


New applied input signal = $u(t) - 2u(t-4) + 1.0u(t-5)$

Output signal for input $u(t)$,

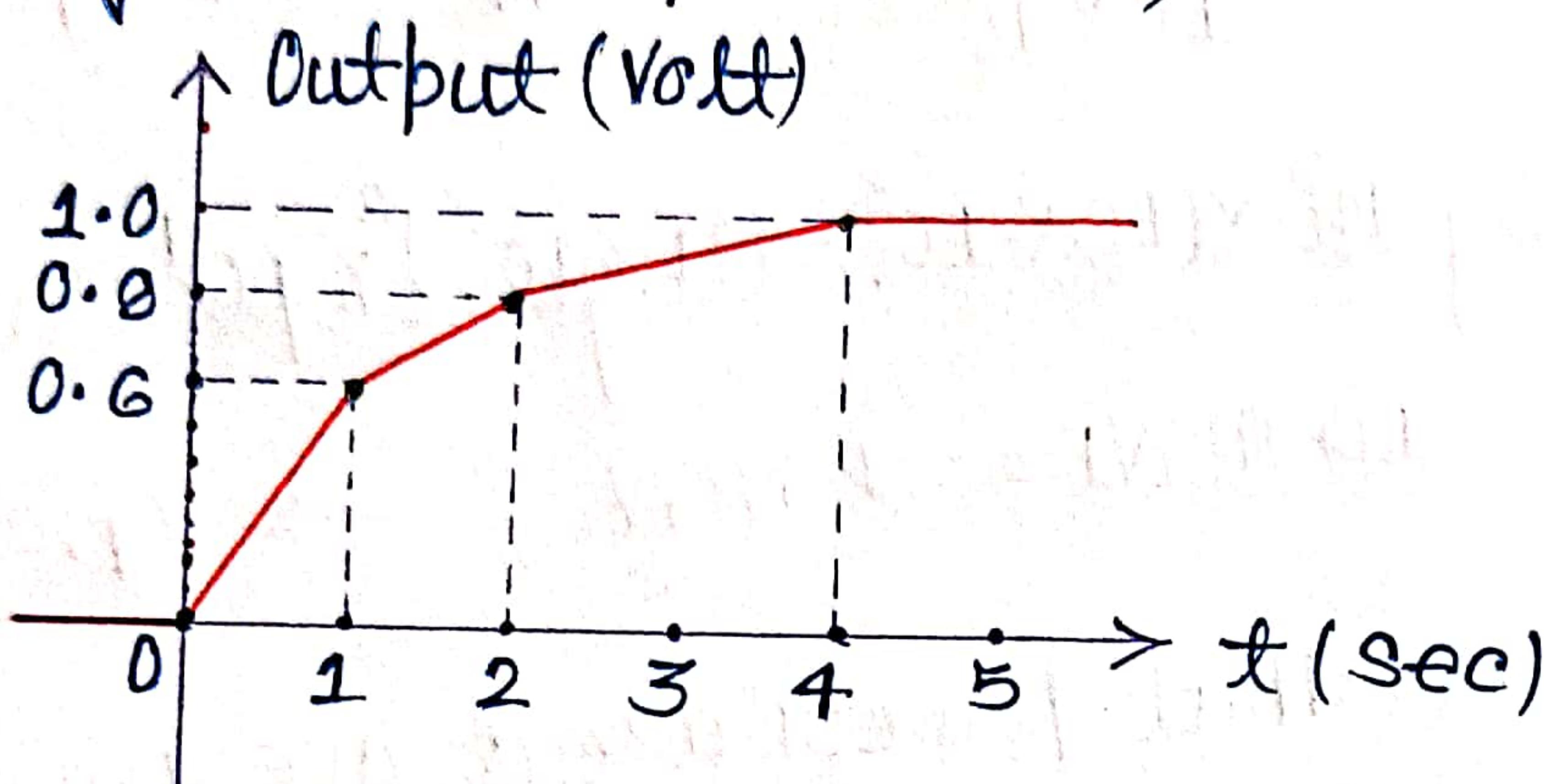


Case(II)-

Output signal for input $-2u(t-4)$,

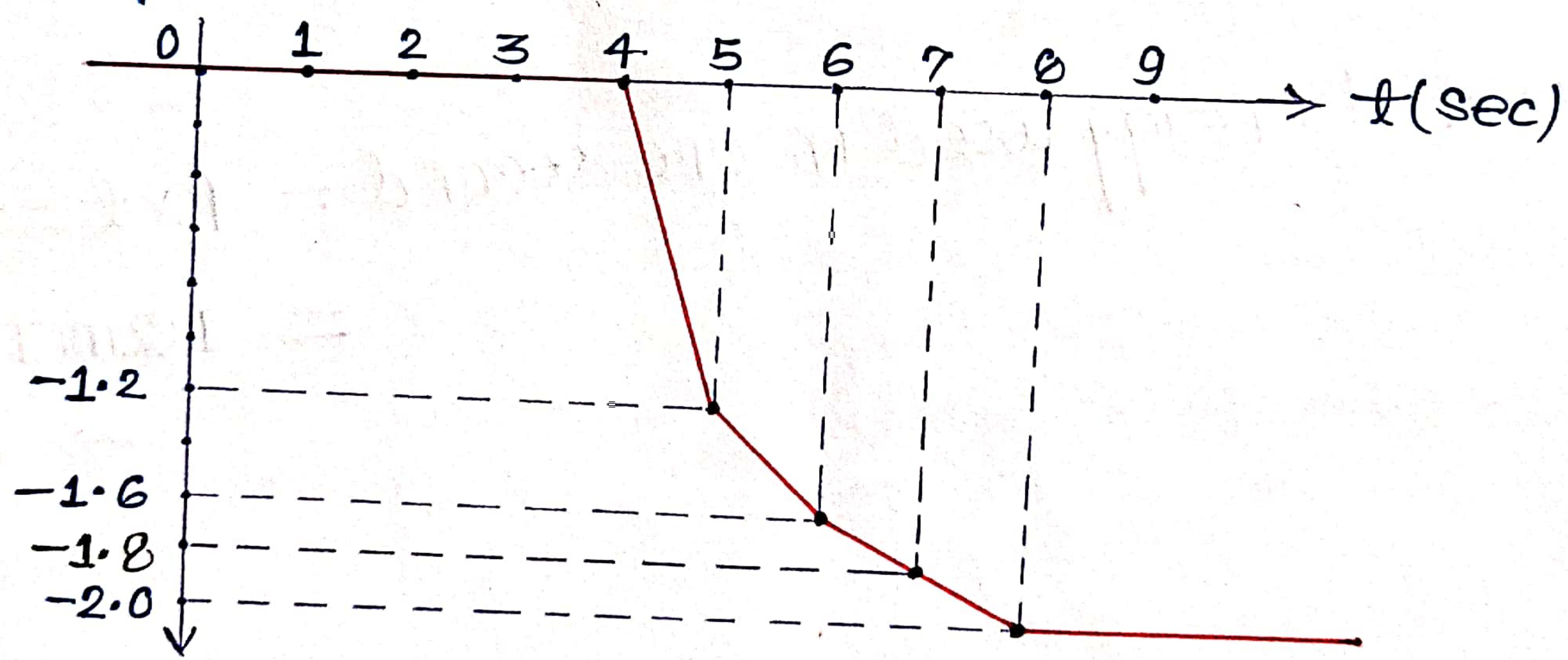


Case(III)-

Output signal for input $1.0u(t-5)$,

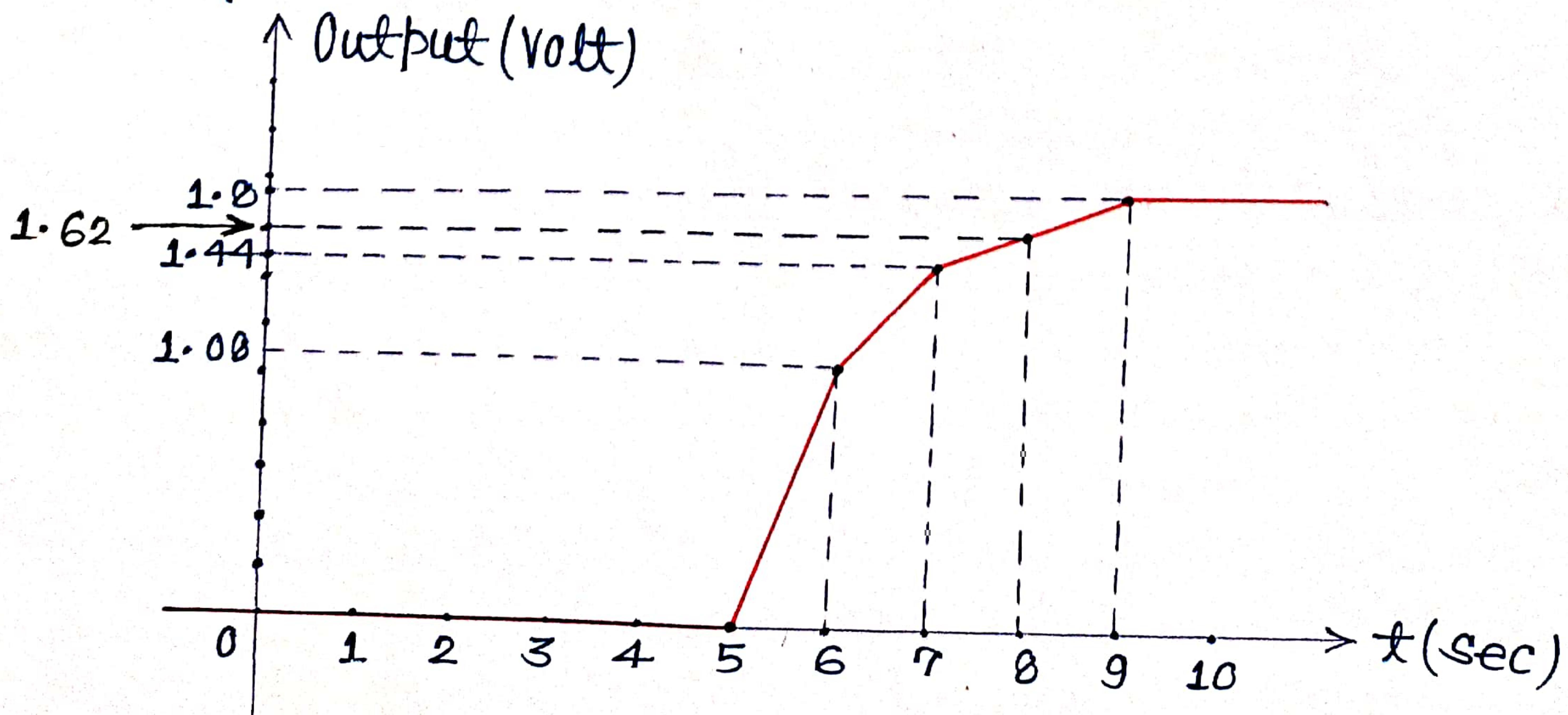

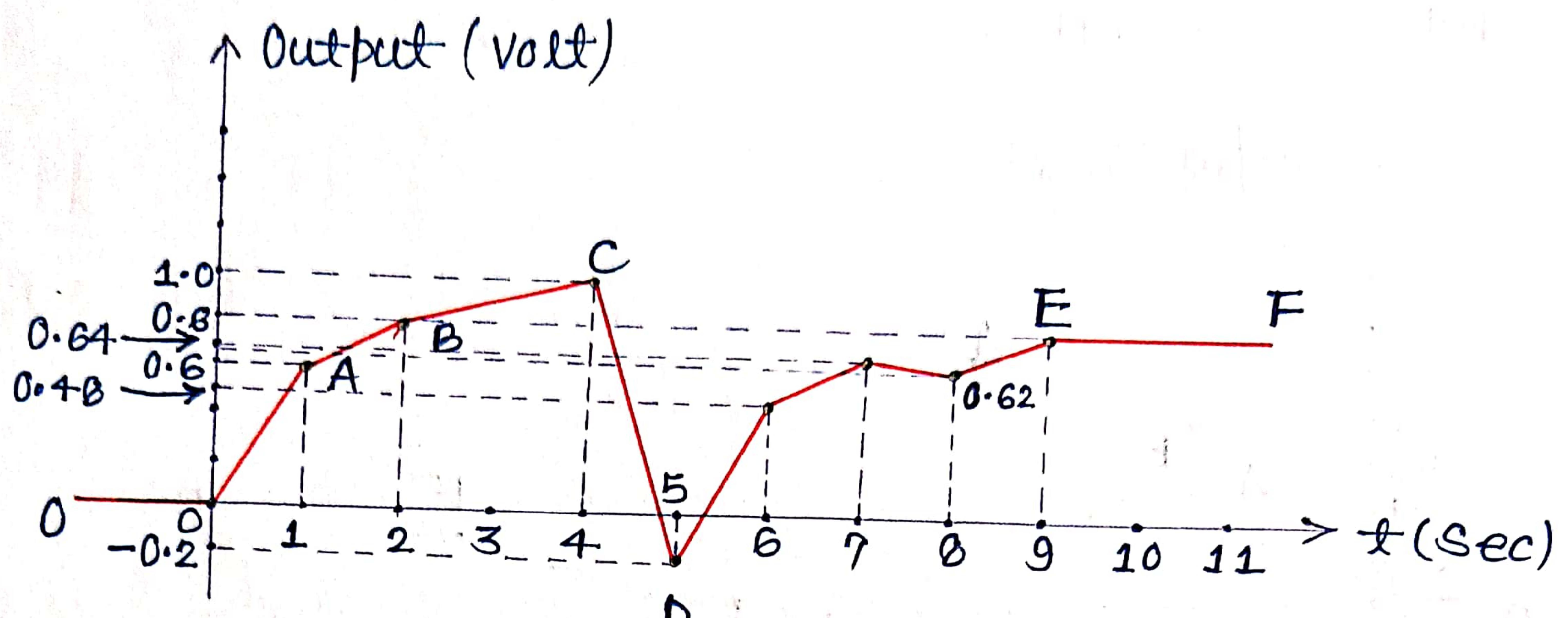By using the property of linearity, resultant signal for the input signal $u(t) - 2u(t-4) + 1.8u(t-5)$ will be-




$(OA, AB, BC, CD, DE, EF) \times 1 \text{ POINT} \rightarrow (6 \text{ POINT})$

Set (B):


New applied input signal = $u(t) - 2u(t-4) + 1.4u(t-6)$

Case(I) & Case(II) will be same as Set(A).

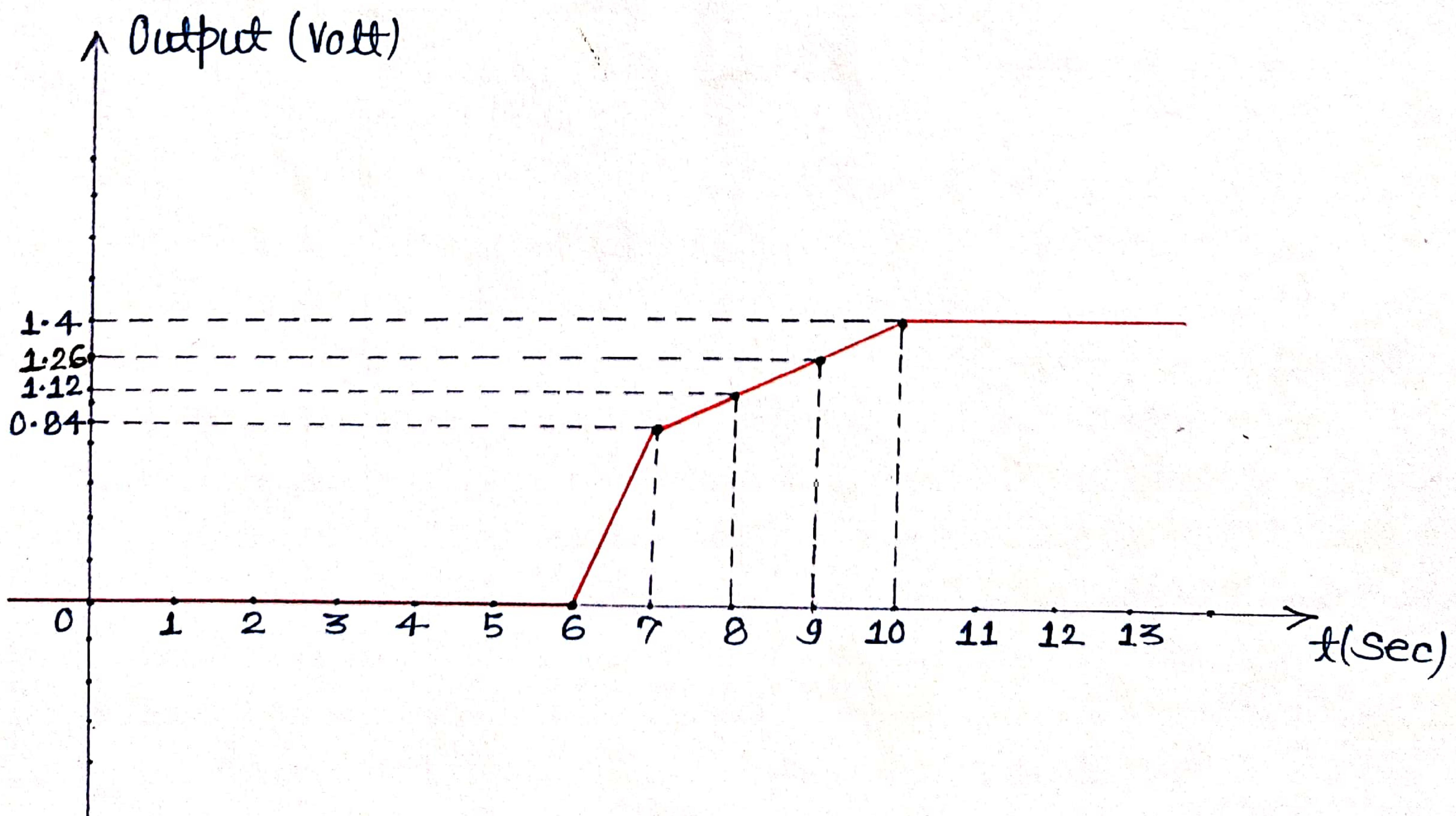Case(III) — Output signal for input $1.4u(t-6)$,



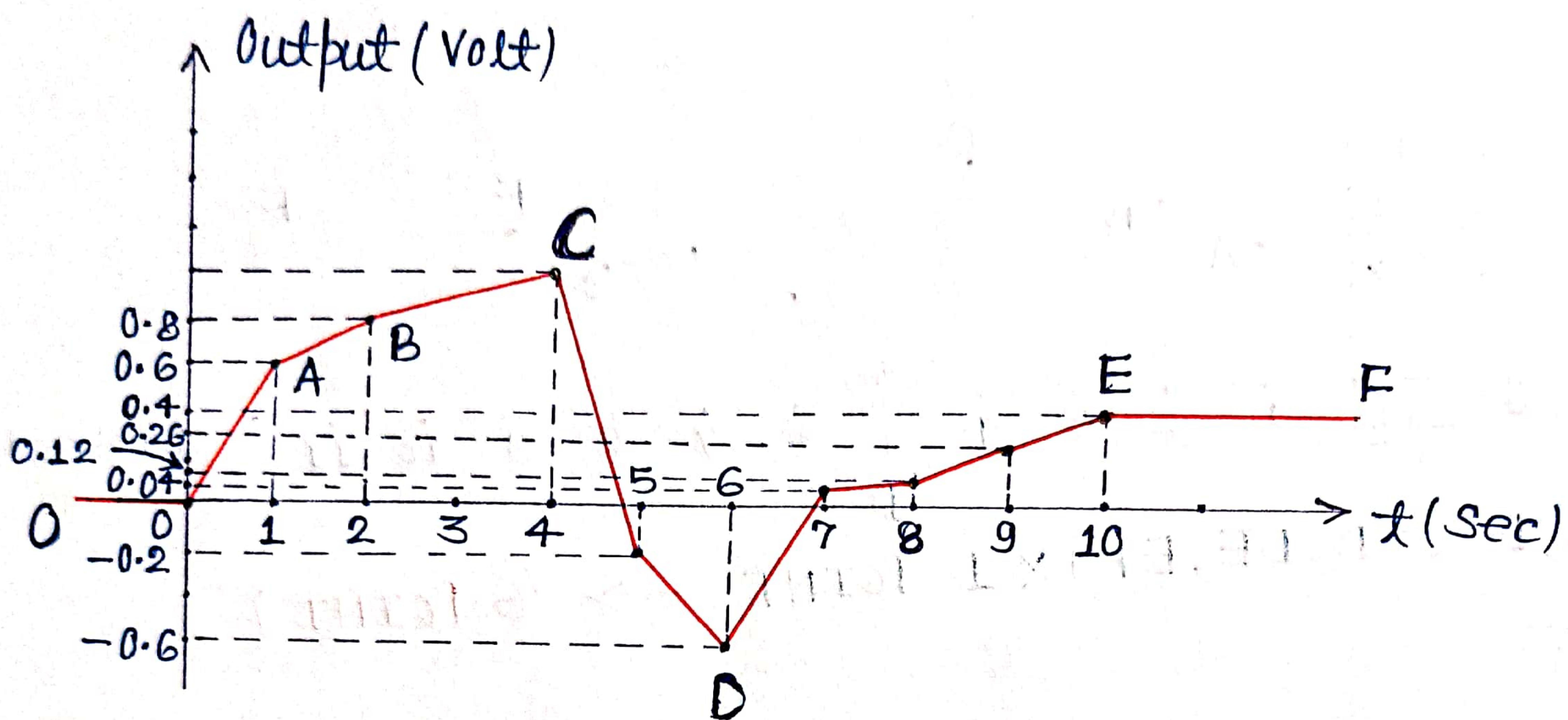By using the property of linearity, resultant output signal for the given input signal, $u(t) = 2u(t-4) + 1.4u(t-6)$ will be -




$(OA, AB, BC, CD, DE, EF) \times 1 \rightarrow (6 \text{ POINT})$

SOL(4) :-

Set(A) :-

Given V-I characteristic of diode -

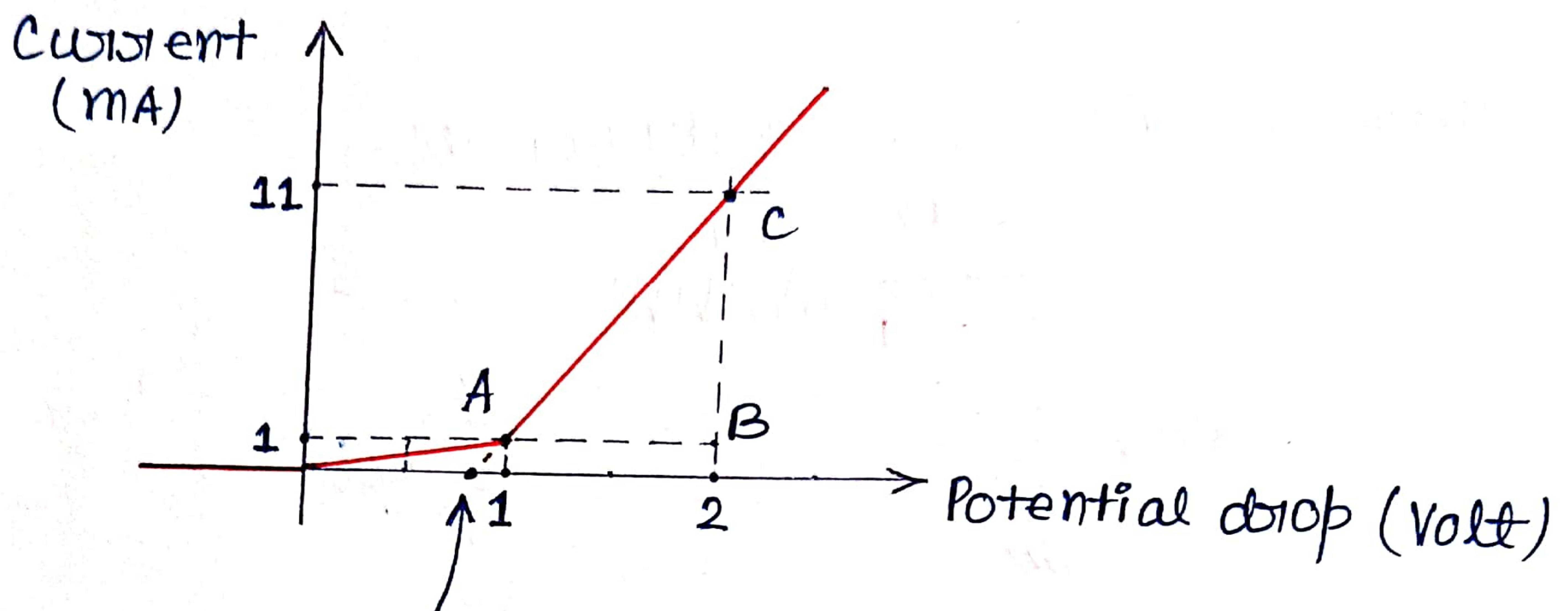


Forward Voltage Drop / Cut-in Voltage (V_f)

$$= 0.9 \text{ Volt} \rightarrow \text{(2 POINT)}$$

Internal Resistance of diode / Forward Resistance

$$(R_f) = \left(\frac{2-1}{11-1}\right) k\Omega = \frac{1}{10} k\Omega = 100\Omega \rightarrow \text{(2 POINT)}$$

Given circuit can be redrawn as -

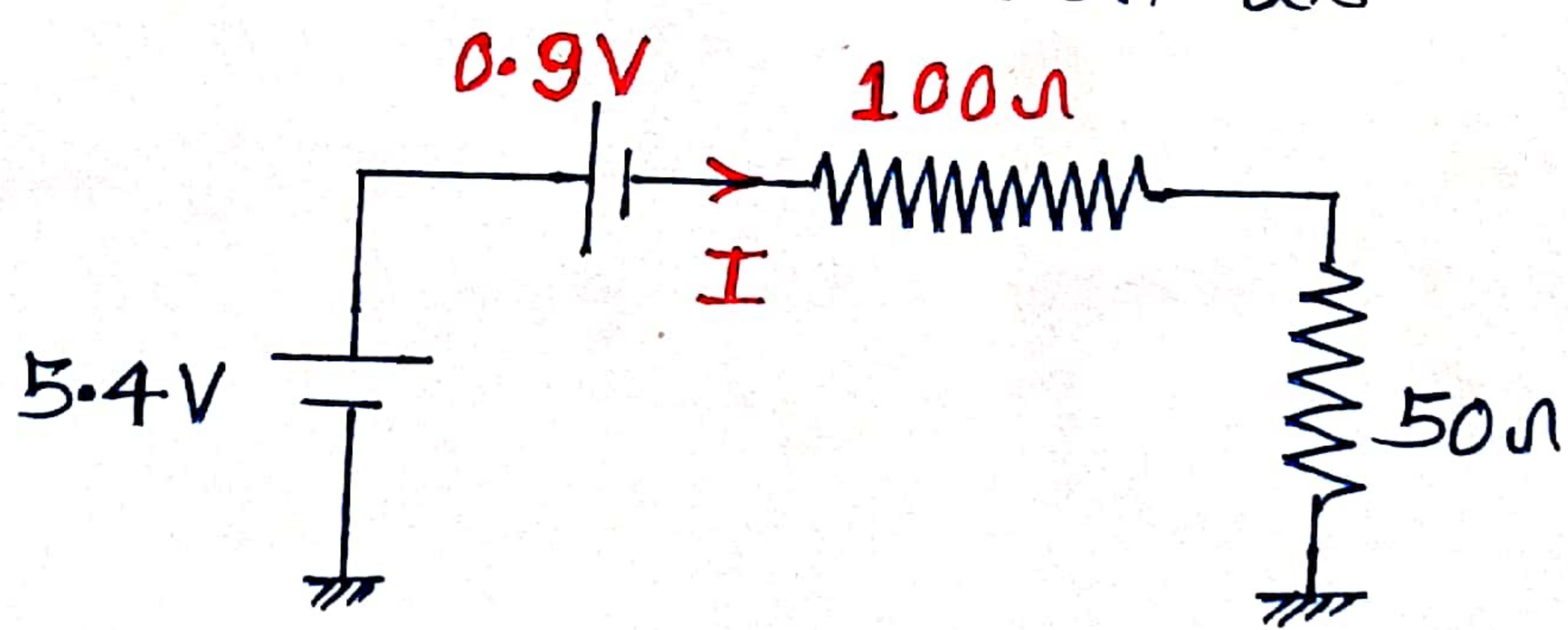

$$\therefore \text{Current, } I = \frac{(5.4 - 0.9)}{(100 + 50)} = 0.03A = 30 \text{ mA} \rightarrow \text{(2 POINT)}$$