

## MID SEM EXAM (SET-A)

### SOLUTION


SOL(1):

For maximum power transfer from 10V source to the  $5\Omega$  load is possible, when the value of resistor  $R_1$  should be minimum & the value of resistor  $R_2$  can take any value ( $R_2 \neq 0$ ).

$\therefore$  Min<sup>m</sup> possible value of  $R_1 = 0\Omega$  (sc)  $\rightarrow$  [1 POINT]

$\therefore$  Value of  $R_2 =$  any value but not short circuit  $\rightarrow$  [1 POINT]

SOL(2):

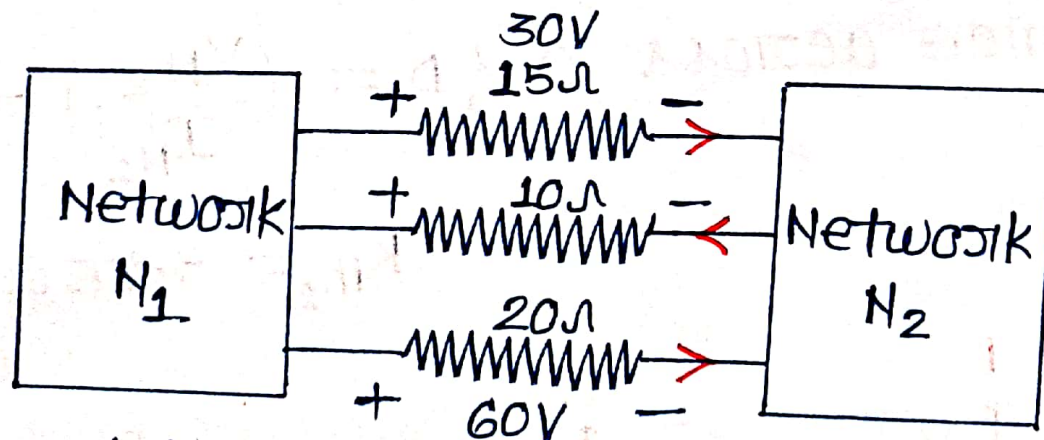

For Network  $N_1$  / Network  $N_2$  —

By using KCL, Total incoming current = Total outgoing current

$$\text{Current through } 15\Omega \text{ resistor} = \frac{30}{15} = 2A$$

$$\text{Current through } 20\Omega \text{ resistor} = \frac{60}{20} = 3A$$

$$\therefore \text{Current through } 10\Omega \text{ resistor} = 2 + 3 = 5A \quad [1 \text{ POINT}]$$

$$\therefore \text{Voltage across } 10\Omega \text{ resistor} = (-5)(10) = -50 \text{ Volt} \quad [1 \text{ POINT}]$$



SOL(3):

by

By Table-1, for Linear Circuit-1 —

∴ OC voltage / Thevenin voltage across A & B = 10 Volt

$$V_{th1} = 10 \text{ Volt}$$

∴ SC current / Norton current across A & B = 5A [0.5 POINT]

$$I_{N1} = 5A$$

∴ Thevenin resistance across A & B =  $\left(\frac{V_{th1}}{I_{N1}}\right) = \left(\frac{10}{5}\right)$

$$R_{th1} = 2\Omega$$

[0.5 POINT]

By Table-2, for Linear Circuit-2 —

∴ OC voltage / Thevenin voltage across C & D = 15 Volt

$$V_{th2} = 15 \text{ Volt}$$


∴ SC current / Norton current across C & D = 4A [0.5 POINT]

$$I_{N2} = 4A$$

∴ Thevenin resistance across C & D =  $\left(\frac{V_{th2}}{I_{N2}}\right) = \left(\frac{15}{4}\right)$

$$R_{th2} = 3.75\Omega$$

[0.5 POINT]

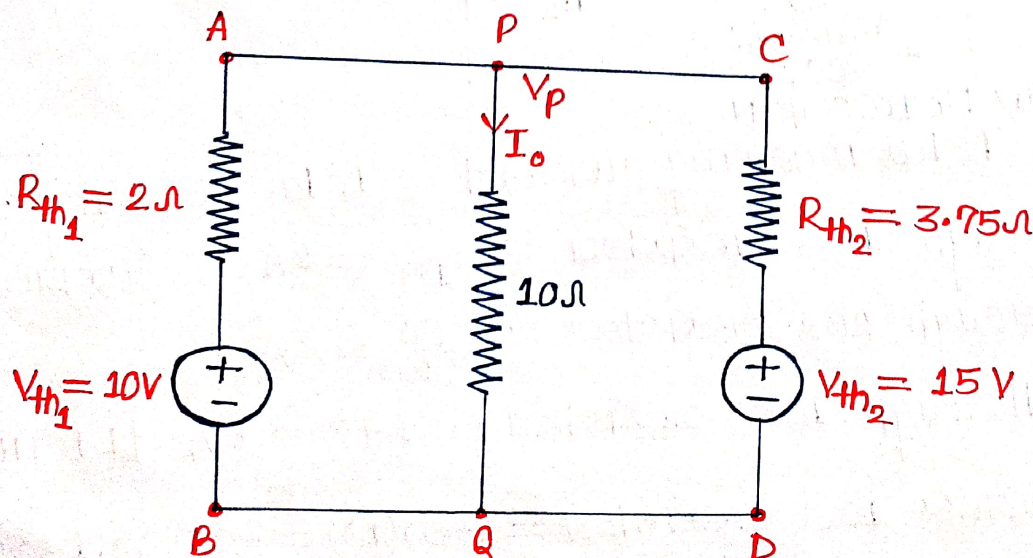

By Nodal analysis at Node-P,

$$\frac{V_p}{10} + \frac{V_p - V_{th1}}{R_{th1}} + \frac{V_p - V_{th2}}{R_{th2}} = 0$$

$$\frac{V_p}{10} + \frac{V_p - 10}{2} + \frac{V_p - 15}{3.75} = 0$$


$$\frac{13}{15} V_p = 9$$

$$\therefore V_p = \frac{135}{13} = 10.38 \text{ Volt}$$

$$\therefore I_o = \frac{V_p}{10} = \frac{10.38}{10} = 1.04 \text{ A}$$

[1 POINT]

SOL(4)

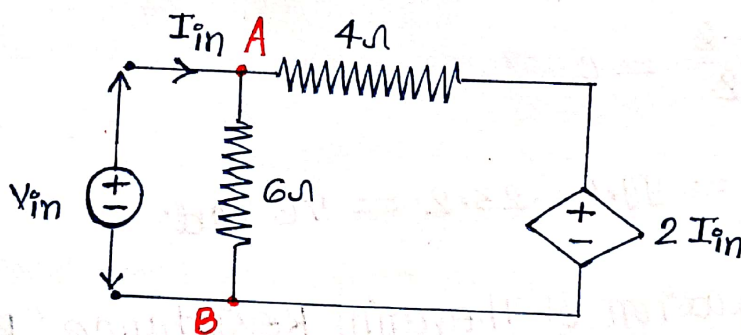

By Nodal analysis at Node-A,

$$\frac{V_{in}}{6} + \frac{V_{in} - 2I_{in}}{4} = I_{in}$$

$$10 V_{in} - 12 I_{in} = 24 I_{in}$$


$$\frac{V_{in}}{I_{in}} = \frac{36}{10} = 3.6 \Omega$$

[3 POINT]

SOL(5):

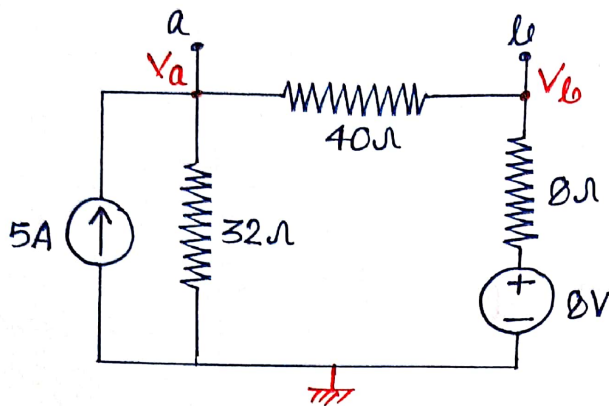(a) Thevenin equivalent circuit as viewed by resistor 'R'

Step(I): Calculation of Thevenin voltage ( $V_{th}$ )



KCL at node - a, we get -

$$5 = \frac{V_a}{32} + \frac{V_a - V_b}{40}$$


KCL at node - b, we get -

$$\frac{V_b - V_a}{40} + \frac{V_b - 8}{8} = 0$$

$$\therefore V_{th} = V_a - V_b = 99.2 - 23.2 = 76 \text{ Volt}$$

[2 POINT]

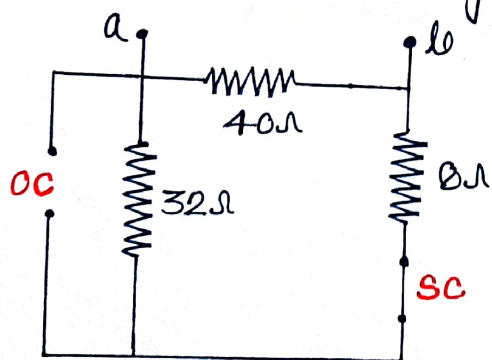Step(II): Calculation of Thevenin Resistance ( $R_{th}$ )



$$\therefore R_{th} = R_{ab} = 40 \parallel (32 + 8) = 40 \parallel 40 = 20\Omega$$

[2 POINT]



Q. (b) By maximum power transfer theorem, the power dissipated by 'R' will be maximum, when value of 'R' across point a & b will be equal to the thevenin resistance across point a & b.

$$\therefore R = R_{th} = 20\Omega$$

[1 POINT]

(c) By maximum power transfer theorem,

The maximum power will be equal to  $\frac{V_{th}^2}{4R_{th}} = \frac{V_{th}^2}{4R_L}$

$$\therefore P_{max} = \frac{V_{th}^2}{4R} = \frac{76^2}{4 \times 20} = 72.2 \text{ Watt}$$

[1 POINT]


SOL (6):

Step (I): Find currents through  $2\Omega$  &  $6\Omega$ , when  $R = 3\Omega$

$$R_{eq}(\text{across } 12V) = 2 + \frac{3 \times 6}{3+6} = 4\Omega$$

$$\therefore I_2 = \frac{12}{4} = 3A$$

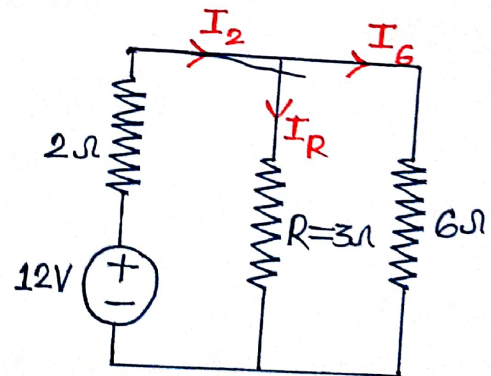
$$\therefore I_6 = 3 \times \left(\frac{3}{3+6}\right) = 1A$$



[2X1 POINT]

Step(II): Find currents through  $2\Omega$  &  $6\Omega$ , when  $R = 6\Omega$
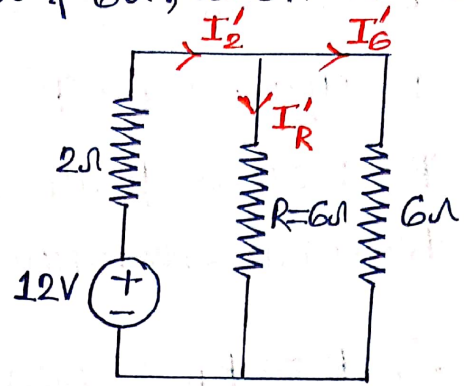
$$R_{eq}(\text{across } 12V) = 2 + \frac{6 \times 6}{6+6} \\ = 5\Omega$$



$$\therefore I_2' = \frac{12}{5} = 2.4 \text{ A}$$

$$\therefore I_6' = 2.4 \times \left(\frac{6}{6+6}\right) = 1.2 \text{ A}$$

[2X1 POINT]

Step(III):

$$\therefore \text{Difference of value of current in } 2\Omega = |I_2 - I_2'| \\ = |3 - 2.4| \\ = 0.6 \text{ A}$$

[1 POINT]

$$\therefore \text{Difference of value of current in } 6\Omega = |I_6 - I_6'| \\ = |1 - 1.2| \\ = 0.2 \text{ A}$$

[1 POINT]


Q. 01(7):

From Figure-7,

Equivalent resistance across A & B,

$$R'_{eq} = \frac{1}{\left(\frac{1}{32} + \frac{1}{16} + \frac{1}{8}\right)} = \frac{32}{7} \Omega$$

[2 POINT]

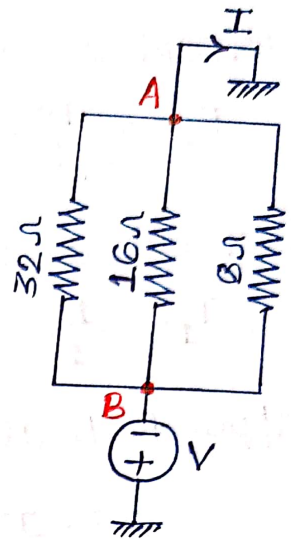


From Figure-8,

Equivalent resistance across P & Q,

$$R''_{eq} = \frac{1}{\left(\frac{1}{4} + \frac{1}{2} + \frac{1}{1}\right)} = \frac{4}{7} \Omega$$

[2 POINT]

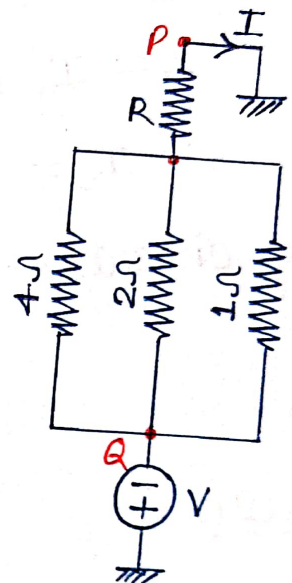

The value of current 'I' remain same (Given), Hence—

$$R'_{eq} = R''_{eq} + R$$

$$\frac{32}{7} = \frac{4}{7} + R$$

$$\therefore R = \frac{28}{7} = 4 \Omega$$

[2 POINT]



SOL(8):

Current across  $2\Omega$  resistance,

$$I_2 = \frac{10}{2} = 5A$$

Current across  $1\Omega$  resistance,

$$\therefore I_1 = \frac{10}{1} = 10A$$

[2 POINT]

Apply KCL at node-A,

$$2 = I_s + I_2 + I_1$$

$$2 = I_s + 5 + 10$$


$$\therefore I_s = -13A$$

[2 POINT]

By circuit —  $-V_s + 2 \times 5 + 10 = 0$

$$\therefore V_s = 20 \text{ Volt}$$

[2 POINT]

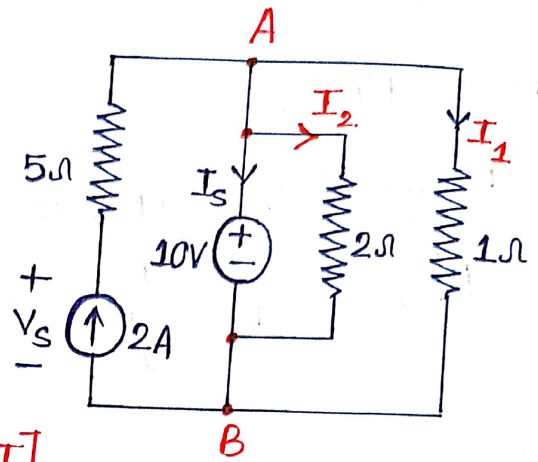

SOL(9):

By using Superposition Theorem,

$$I_o = \pm I_1 \pm I_2$$

where,


$I_1$  = Current across resistor  $R$ , when voltage source  $V$  active alone

$I_2$  = Current across resistor  $R$ , when current source  $I$  active alone

$$\sqrt{\left(\frac{P_o}{R}\right)} = \pm \sqrt{(P_1/R)} \pm \sqrt{(P_2/R)}$$

$$P_o = (\pm \sqrt{P_1} \pm \sqrt{P_2})^2$$

[2 POINT]

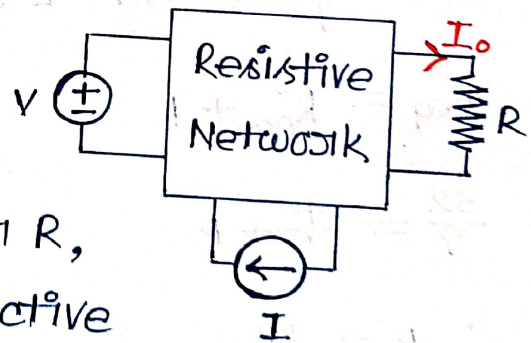

$$P_o = (\sqrt{4} + \sqrt{9})^2 = (2+3)^2 = 25 \text{ W}$$

$$P_o = (\sqrt{4} - \sqrt{9})^2 = (2-3)^2 = 1 \text{ W}$$

$\therefore$  Power dissipated by resistor R, when both sources are active —  $P_o = 25 \text{ W}, 1 \text{ W}$

[4 POINT]