

ECE113: Basic Electronics (BE)

Winter 2024

Quiz-2

Date: 18-April-2024

Duration: 30 Minutes

Total Points: 24 Points

[CO3] **Q1: [6 Points]** In the given following circuit (Figure-1), the initial value of voltage $[V_C(0)]$ across capacitor is **6V**. Find the value of energy absorbed by the resistor in the time interval $0 \leq t < \infty$.

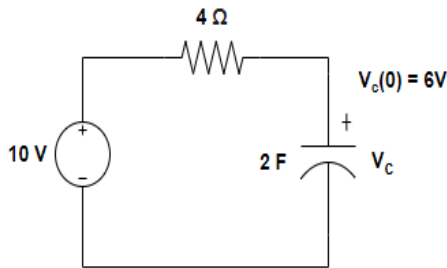


Figure 1

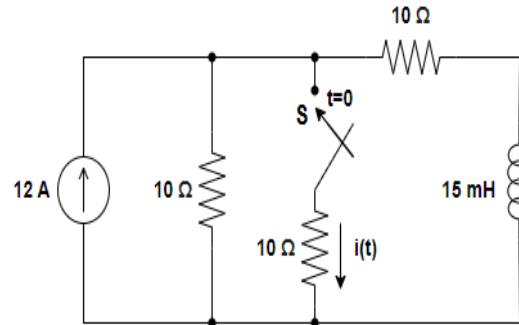


Figure 2

[CO3] **Q2: [4 Points]** In the given following circuit (Figure-2), the switch **S** is open for a long time and is closed at $t=0$. Find the value of current $i(t)$ for $t \geq 0^+$.

[CO3] **Q3: [6 Points]** In the given following circuit (Figure-3), the switch **S** was on position **A** for a long time, and is moved to position **B** at time $t=0$ sec. Find the value of current $i(t)$ for $t > 0$.

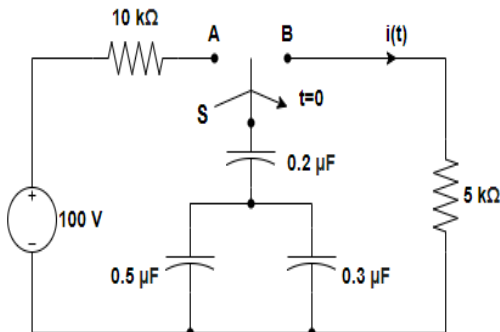


Figure 3

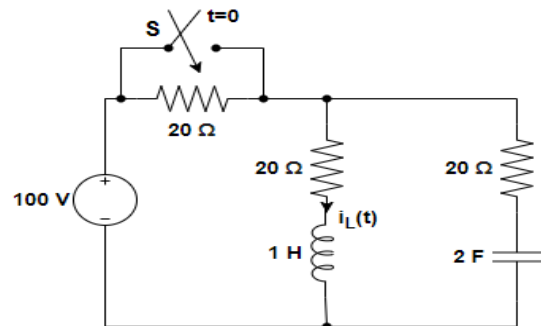


Figure 4

[CO3] **Q4: [4 Points]** In the given circuit (Figure-4), find the rate of change of current across the inductor at time $t=0^+$.

[CO3] **Q5: [4 Points]** Find Time constant (**T**) of the circuit shown in Figure-5.

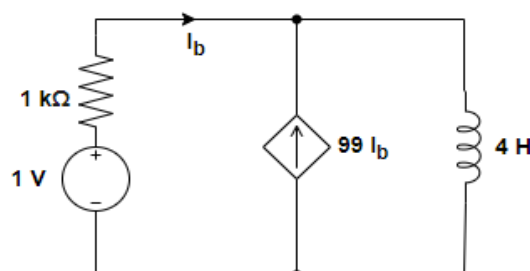


Figure 5