

ECE113: Basic Electronics (BE)

Winter 2024

Mid Semester Exam (Set-A)

Date: 29-Feb-2024

Duration: 1Hours

Total Points: 40 Points

[CO1, CO2] **Q1: [2 Points]** Find the value of resistor R_1 and R_2 , so that maximum power can be delivered from **10 volt** source to **5 Ω** load (Figure-1).

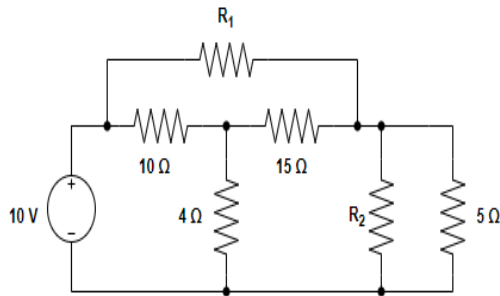


Figure 1

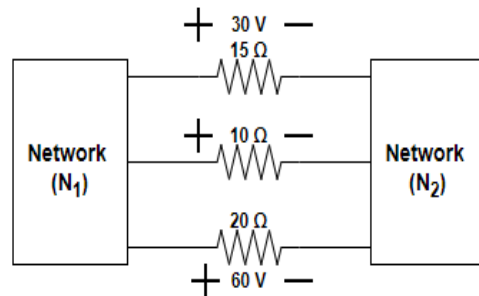


Figure 2

[CO1, CO2] **Q2: [2 Points]** Two electrical networks N_1 and N_2 are connected through three resistors (Figure-2). The voltage across **15 Ω** resistor and **20 Ω** resistor are given to be **30 V** and **60 V** respectively. Find the value of voltage across **10 Ω** resistor.

[CO1, CO2] **Q3: [3 Points]** Find the value of current I_o flowing through resistor **10 Ω** (Figure-3) by using Table-1 (when Circuit-1 work independently) and Table-2 (when Circuit-2 work independently).



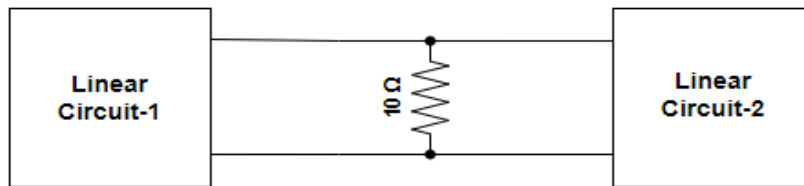


Figure 3

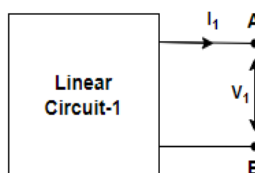

| | | |
|-----------------|----|---|
| V_1 (in Volt) | 10 | 0 |
| I_1 (in Amp) | 0 | 5 |

Table 1

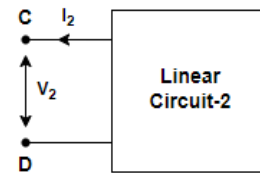

| | | |
|-----------------|---|----|
| V_2 (in Volt) | 0 | 15 |
| I_2 (in Amp) | 4 | 0 |

Table 2

[CO1, CO2] **Q4: [3 Points]** For the active network shown in the Figure-4, find the value of V_{in}/I_{in} .

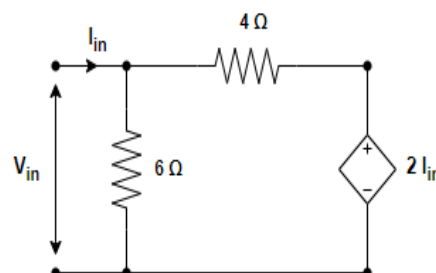


Figure 4

[CO1, CO2] Q5: [6 Points] (a) Determine the Thevenin equivalent circuit as viewed by the resistor R (Figure-5). (b) What value of R is required if the power dissipated by R is to be maximum? (c) What is the value of the said power?

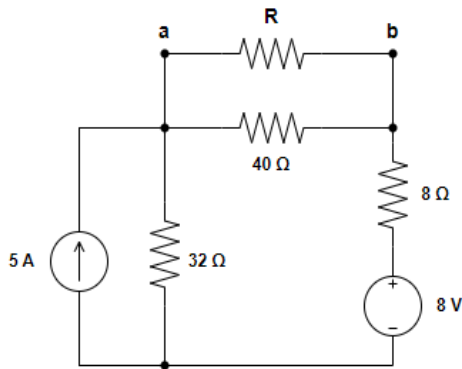


Figure 5

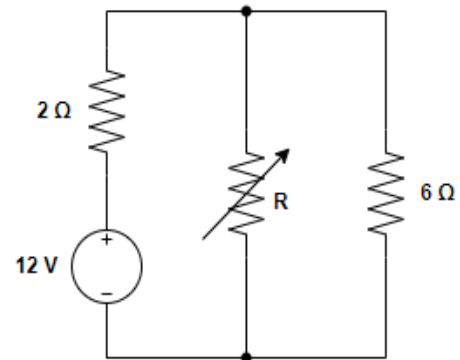


Figure 6

[CO1, CO2] Q6: [6 Points] Find the difference of value of currents in $2\ \Omega$ resistor and $6\ \Omega$ resistor, when the resistance in variable branch is changed from $3\ \Omega$ to $6\ \Omega$ (Figure-6).

[CO1, CO2] Q7: [6 Points] The circuit shown in Figure-7 is replaced by that in Figure-8. If the value of current " I " remain same, then find the value of resistance " R " in Figure-8.

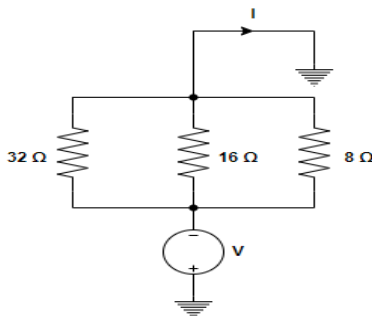


Figure 7

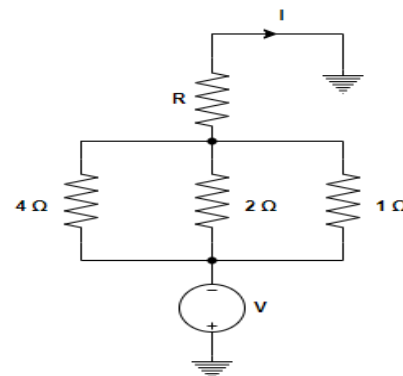


Figure 8

[CO1, CO2] Q8: [6 Points] Find the value of I_s (in Amps), V_s (in Volts) and current in the $1\ \Omega$ resistor (Figure-9).

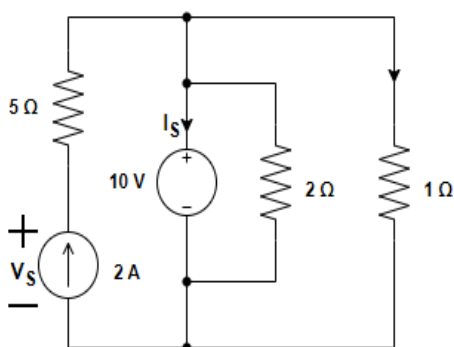


Figure 9

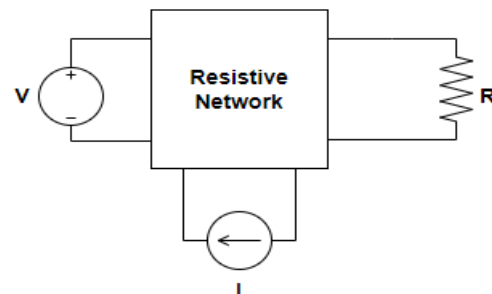


Figure 10

[CO1, CO2] Q9: [6 Points] A DC circuit shown in Figure-10 has a voltage source V , a current source I and several resistors. A particular resistor R dissipates a power of **4 watts**, when voltage source V alone is active. The same resistor R dissipates a power of **9 watts**, when current source I alone is active. Find the value of power dissipated by resistor R , when both sources are active.