

Tutorial-9

Winter 2024

Basic Electronics (ECE113)

Q1: In Figure-1, If $V_i(t) = 4 \sin wt$ volt then draw $V_o(t)$ & transfer characteristic, also define the nature of circuit.
[Ans: Half Wave Rectifiers]

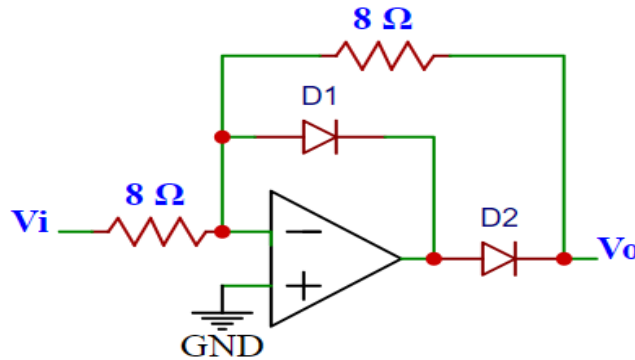


Figure 1

Q2: In Figure-2, If $V_i(t) = 2 \sin wt$ volt then draw $V_o(t)$ & transfer characteristic, also define the nature of circuit.
[Ans: Half Wave Rectifier]

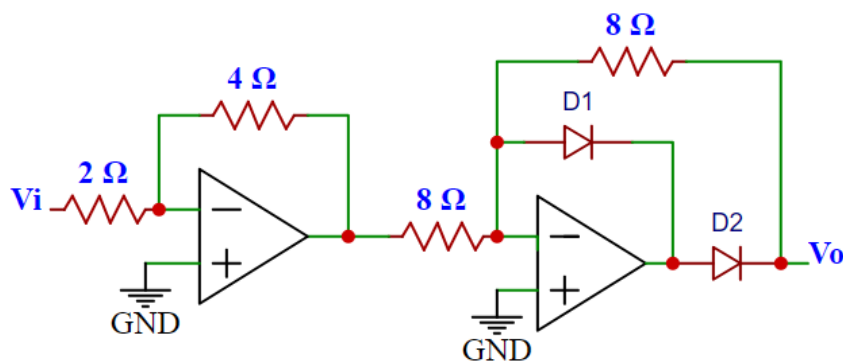


Figure 2

Q3: In Figure-3, if $V_i(t) = 5 \sin wt$ then draw the curve for capacitor voltage $V_c(t)$ & output voltage $V_o(t)$ with explanation. Define the nature of circuit.
[Ans: Clamper Circuit]

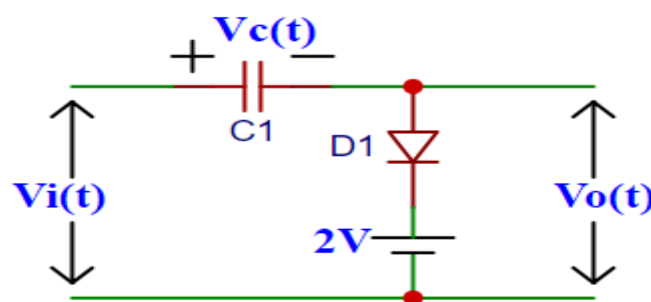



Figure 3

Solution:

5):

Here $V_i(t) = 5 \sin(\omega t)$

$$V_i(t) = V_c(t) + V_d + 2$$

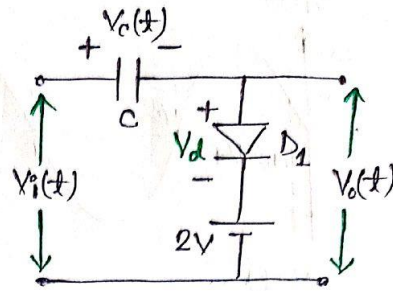


Part (I)

Case (I): For $0 \leq V_i \leq 2$, Diode is OFF.

$$\therefore V_c(t) = 0V$$

$$\therefore V_o(t) = V_d = V_i(t)$$

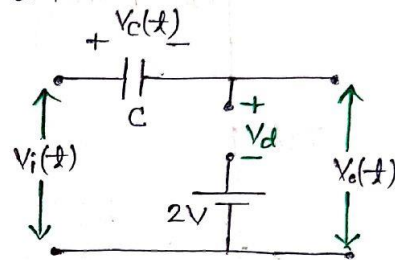

Case (II): For $2 < V_i < 5$, Diode is ON.


$$\therefore V_c(t) = V_i(t) - V_d - 2$$

$$= V_i(t) - 0 - 2$$

$$= [V_i(t) - 2]$$

at $t = (T/4)$, $V_c(t) = (5 - 2) = 3V$


$$\therefore V_o(t) = 2V$$

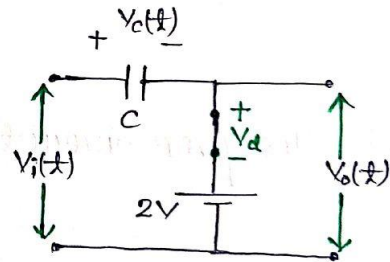


Case (III): For $V_i > 5$, Diode is OFF.

$$V_o(t) = V_d = V_i(t) - V_c(t)$$

$$= [V_i(t) - 3]$$

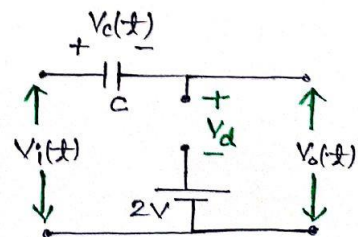

Part (II):

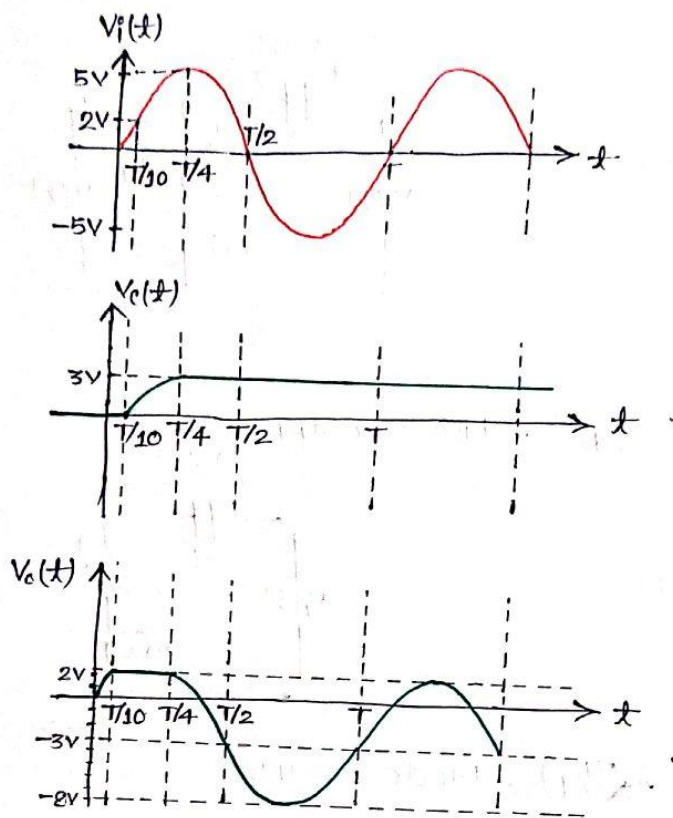

Part (III): The given circuit is working as a clamper circuit.