

ECE113: BASIC ELECTRONICS

QUIZ-1 SOLUTION

SOL(1): The value of coefficients I_2 , I_4 & I_6 are independent of the value of resistors R_1 , R_2 & R_3 respectively.

So, the value of coefficients I_2 , I_4 & I_6 will remain 1A, 2A & 3A respectively.


NOTE: Ideal current source in series with any element is redundant. [4 POINTS]

SOL(2):

By circuit diagram-

$$I = \frac{V_1 - V_2}{2 \times 10^6} = \frac{6 - 4}{2 \times 10^6}$$

$$I = 1 \mu A$$

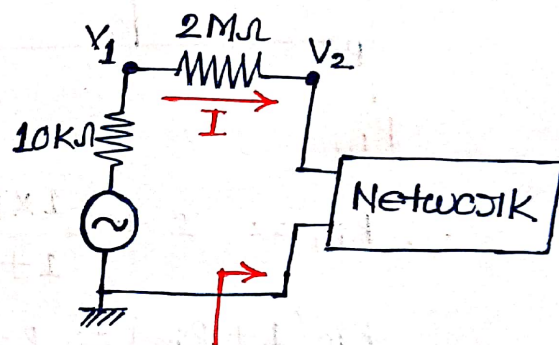

Input Equivalent Resistance $(R_{in})_{eq}$

\therefore Input equivalent Resistance of the Network,

$$(R_{in})_{eq} = \frac{V_2}{I}$$



$$= \frac{4}{1 \times 10^{-6}} = 4 M\Omega$$

$$\therefore (R_{in})_{eq} = 4 M\Omega$$

[4 POINTS]

SOL(3):

Given circuit diagram—

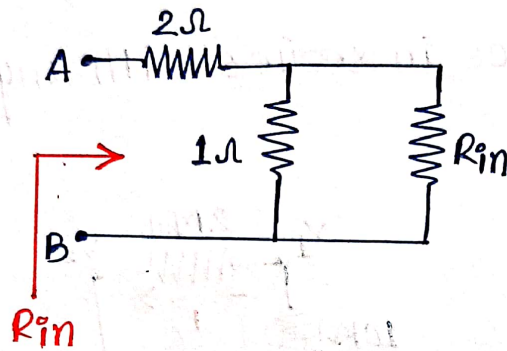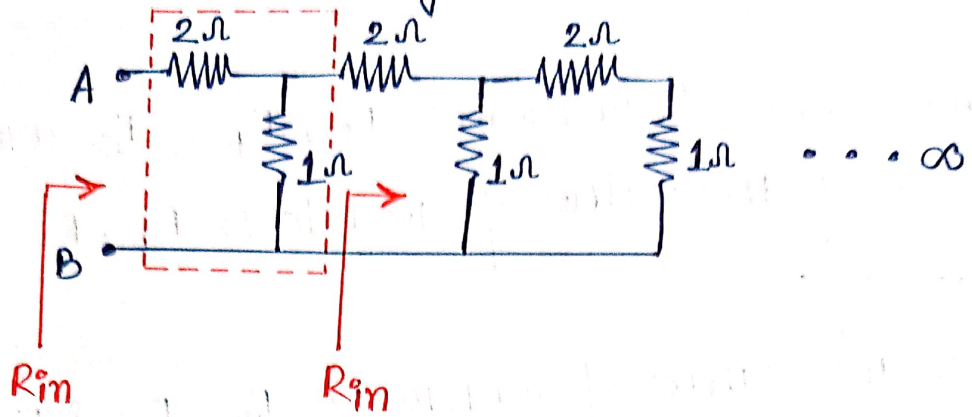

$$\therefore R_{in} = 2 + \frac{1 \times R_{in}}{1 + R_{in}}$$

$$R_{in}(1 + R_{in}) = 2 + 2R_{in} + R_{in}$$

$$R_{in} + R_{in}^2 = 2 + 3R_{in}$$

$$R_{in}^2 - 2R_{in} - 2 = 0$$

$$R_{in} = \frac{2 \pm \sqrt{4 + 8}}{2} = 1 \pm \sqrt{3}$$


$$\therefore R_{in} = (1 + \sqrt{3})\Omega = 2.73\Omega$$

\therefore Equivalent resistance between point A & B,

$$R_{AB} = R_{in} = 2.73\Omega$$

[4 POINTS]


SOL(4):

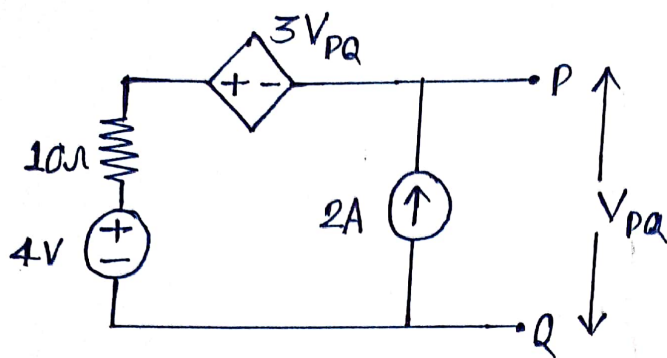

NOTE: In the above network for applying Superposition theorem, dependent source is neither open circuit nor short circuit and it remain same as original network.

Now, By using Superposition Theorem, we can —

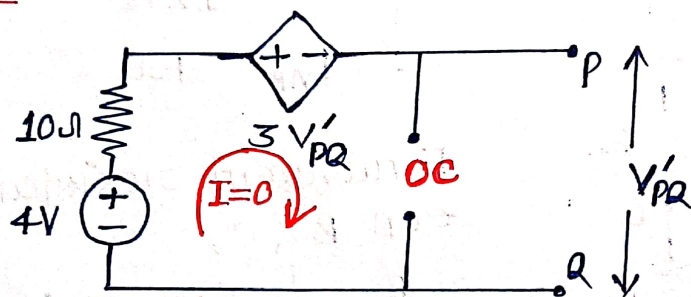Case(I): Consider 4 Volt, ideal voltage source only




$$-4 + 3V'_{PQ} + V'_{PQ} = 0 \quad (\text{apply KVL})$$

$$\therefore V'_{PQ} = 1 \text{ Volt}$$

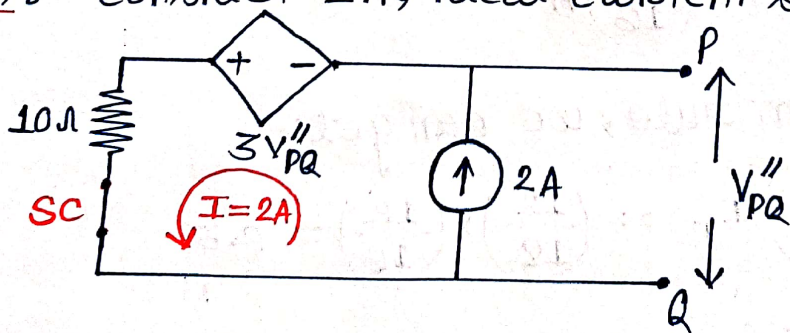[2.75 POINTS]

Case(II): Consider 2 A, ideal current source only



$$-V''_{PQ} - 3V''_{PQ} + 10 \times 2 = 0 \quad (\text{apply KVL})$$

$$\therefore V''_{PQ} = 5 \text{ Volt}$$


[2.75 POINTS]

$$\therefore V_{PQ} = V'_{PQ} + V''_{PQ} = 1 + 5 = 6 \text{ Volt} \quad (\text{Superposition Theorem})$$

[0.5 POINT]

SOL(5) :-

Given circuit diagram—

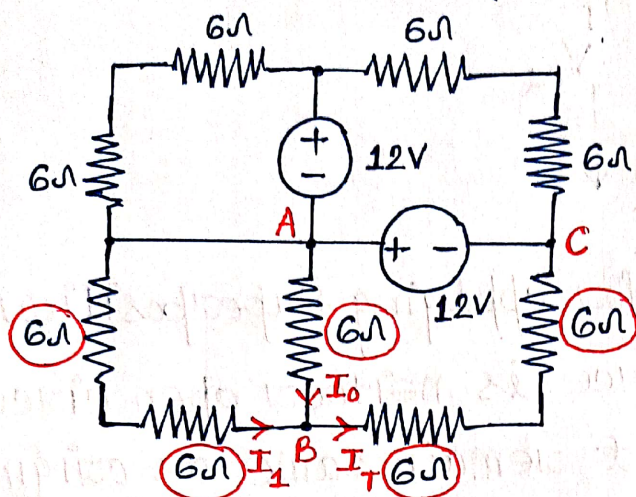

Equivalent resistance between point A & B,


$$R_{AB} = 6 \parallel (6+6) \\ = \frac{6 \times 12}{12+6} = 4$$

$$\therefore R_{AB} = 4\Omega$$

Equivalent resistance between B & C,

$$R_{BC} = 6+6 = 12\Omega$$

$$\therefore R_{BC} = 12\Omega$$

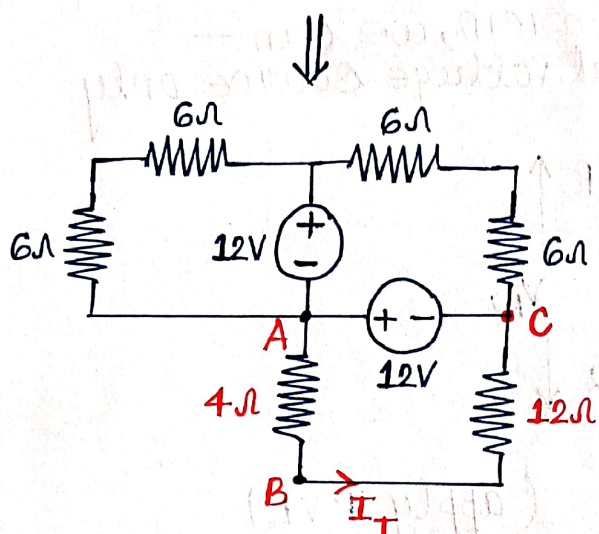

By KVL (between points A, B & C) —

$$I_T = \frac{12}{4+12} = \left(\frac{12}{16}\right) A$$


By current division rule, we can get —

$$I_0 = \left(\frac{12}{12+6}\right) I_T = \left(\frac{12}{18}\right) \times \left(\frac{12}{16}\right) = 0.5$$


$$\therefore I_0 = 0.5 A$$

[6 POINTS]

SOL(6): By given network—

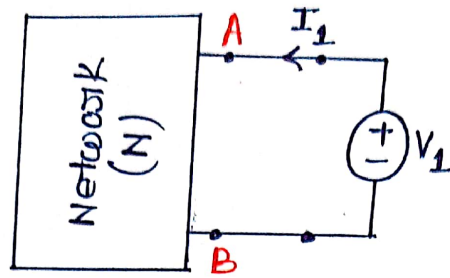

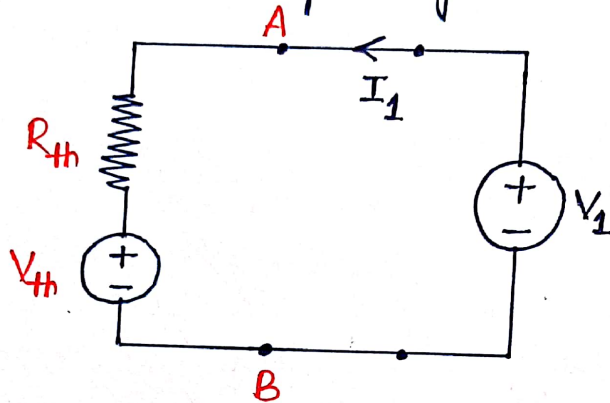Thevenin equivalent of the given circuit can be drawn as—



Applying KVL,

$$-V_1 + I_1 \times R_{th} + V_{th} = 0$$

$$I_1 = \frac{V_1}{R_{th}} - \frac{V_{th}}{R_{th}} \quad \text{--- (1)}$$

Given that— $I_1 = 0.2 V_1 - 2$ --- (2)

Comparing equation (1) & (2), we have—

$$\frac{1}{R_{th}} = 0.2$$

$$\therefore R_{th} = 5 \Omega$$

[3 POINTS]

$$\frac{V_{th}}{R_{th}} = 2$$

$$\therefore V_{th} = 10 \text{ Volt}$$

[3 POINTS]