

## MID SEM EXAM (SET-B)

### SOLUTION

SOL(1):

For maximum power transfer from 20V source to the  $15\Omega$  load is possible, when the value of resistor  $R_1$  should be minimum & the value of resistor  $R_2$  can take any value ( $R_2 \neq 0$ ).

$\therefore$  Min<sup>m</sup> possible value of  $R_1 = 0\Omega$  (SC)  $\rightarrow$  [1 POINT]

$\therefore$  Value of  $R_2 =$  any value but not short circuit  $\rightarrow$  [1 POINT]

SOL(2): For Network  $N_1$  / Network  $N_2$  —


By using KCL (Figure-2),  $\text{Total incoming current} = \text{Total outgoing current}$

$$\text{Current through } 15\Omega \text{ resistor} = \frac{90}{15} = 6A$$

$$\text{Current through } 20\Omega \text{ resistor} = \frac{80}{20} = 4A$$

$$\therefore \text{Current through } 10\Omega \text{ resistor} = 6 + 4 = 10A \quad [1 \text{ POINT}]$$
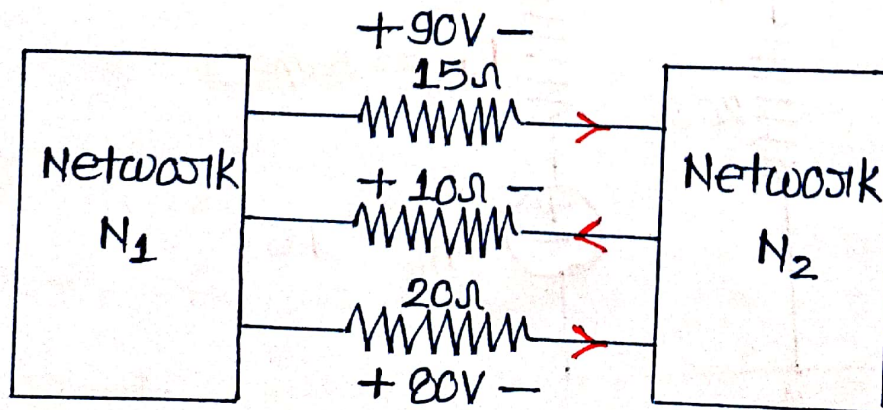
$$\therefore \text{Voltage across } 10\Omega \text{ resistor} = (-10)(10) = -100V \quad [1 \text{ POINT}]$$



SOL(3):

By Table-1, for Linear Circuit-1 -

OC voltage / Thevenin voltage across A & B = 10 Volt

$$V_{th1} = 10 \text{ Volt} \quad [0.5 \text{ POINT}]$$

SC current / Norton current across A & B = 5 A

$$I_{N1} = 5 \text{ A}$$

Thevenin resistance across A & B =  $\frac{V_{th1}}{I_{N1}} = \frac{10}{5}$

$$R_{th1} = 2 \Omega \quad [0.5 \text{ POINT}]$$

By Table-2, for Linear Circuit-2 -

OC voltage / Thevenin voltage across C & D = 15 Volt


$$V_{th2} = 15 \text{ Volt} \quad [0.5 \text{ POINT}]$$

SC current / Norton current across C & D = 4 A

$$I_{N2} = 4 \text{ A}$$

Thevenin resistance across C & D =  $\frac{V_{th2}}{I_{N2}} = \frac{15}{4}$
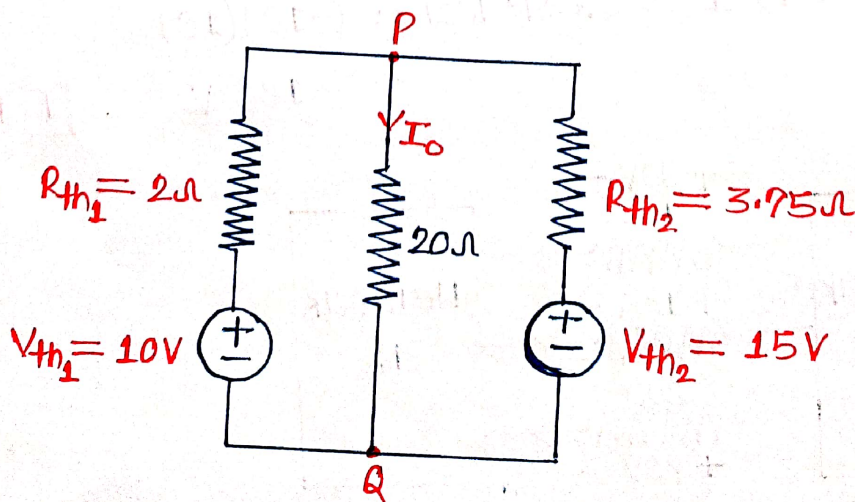
$$R_{th2} = 3.75 \Omega \quad [0.5 \text{ POINT}]$$





By Nodal analysis at Node-P,

$$\frac{V_P}{20} + \frac{V_P - 10}{2} + \frac{V_P - 15}{3.75} = 0$$

$$\frac{49}{60} V_P = 9$$

$$\therefore V_P = 11.02 \text{ Volt}$$

$$\therefore I_o = \frac{V_P}{20} = \frac{11.02}{20} = 0.55 \text{ A}$$

[1 POINT]

SOL(4):

By Nodal analysis at Node-A,


$$\frac{V_{in}}{8} + \frac{V_{in} - 2I_{in}}{4} = I_{in}$$

$$V_{in} + 2V_{in} - 4I_{in} = 8I_{in}$$

$$3V_{in} = 12I_{in}$$

$$\frac{V_{in}}{I_{in}} = 4 \Omega$$

[3 POINT]

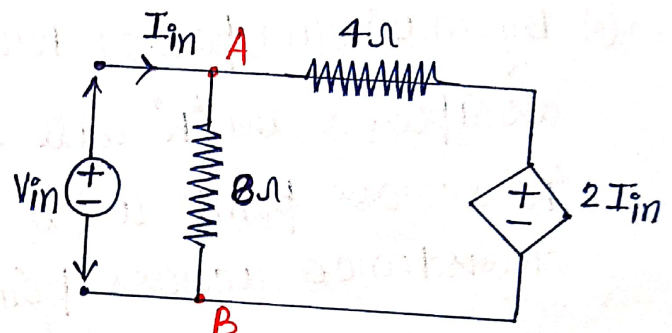

SOL(5):

(a) Thevenin equivalent circuit as viewed by resistor 'R'


Step(I): Calculation of Thevenin Voltage ( $V_{th}$ )

KCL at node-a, we get-

$$3 = \frac{V_a}{8} + \frac{V_a - V_b}{10}$$

KCL at node-b, we get-
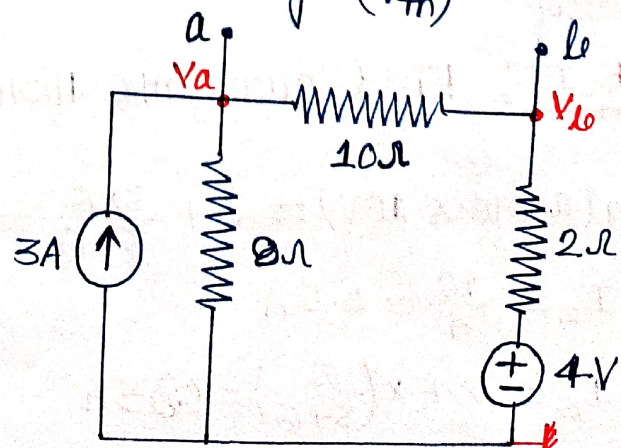
$$\frac{V_b - V_a}{10} + \frac{V_b - 4}{2} = 0$$



$$\therefore V_{th} = V_a - V_b = 16 - 6 = 10 \text{ Volt}$$

[2 POINT]


Step(II) ÷ Calculation of Thevenin Resistance ( $R_{th}$ )

$$\therefore R_{th} = R_{ab}$$

$$= 10 \parallel (8+2)$$

$$= 5 \Omega$$

[2 POINT]

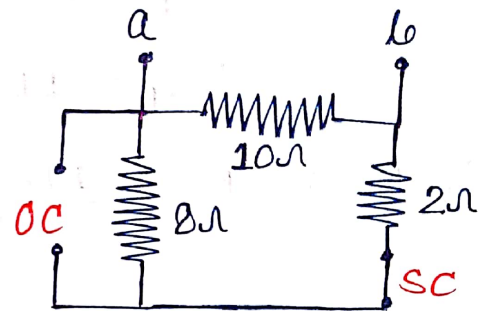

(b) By maximum power transfer theorem, the power dissipated by 'R' will be maximum, when value of 'R' across point a & b will be equal to the thevenin resistance across point a & b.

$$\therefore R = R_{th} = 5 \Omega$$

[1 POINT]

(c) By maximum power transfer theorem,

$$\text{The maximum power will be equal to } \frac{V_{th}^2}{4R_L} = \frac{V_{th}^2}{4R_{th}}$$

$$\therefore P_{max} = \frac{V_{th}^2}{4R} = \frac{10^2}{4 \times 5} = 5 \text{ W}$$

[1 POINT]

SOL(6) ÷


step(I) ÷ Find currents through  $2 \Omega$  &  $6 \Omega$ , when  $R = 3 \Omega$

$$R_{eq}(\text{across } 10V) = 2 + \frac{3 \times 6}{3+6} = 4 \Omega$$

$$\therefore I_2 = \frac{10}{4} = 2.5 \text{ A}$$

$$\therefore I_6 = 2.5 \times \left( \frac{3}{3+6} \right) = 0.83 \text{ A}$$

[2X1 POINT]

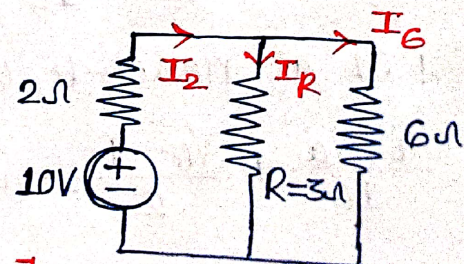




Step(II): Find currents through  $2\Omega$  &  $6\Omega$ , when  $R=6\Omega$ .

$R_{eq}$  (across  $10V$ )

$$= 2 + \frac{6 \times 6}{6+6} = 5\Omega$$

$$\therefore I_2' = \frac{10}{5} = 2A$$
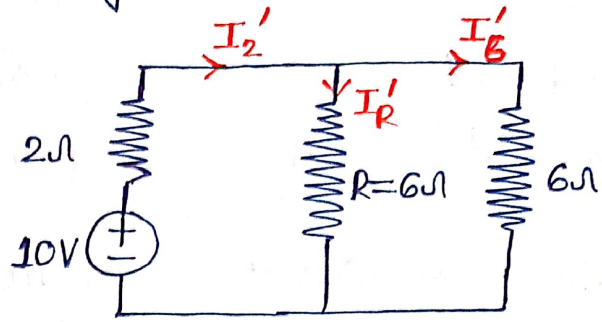
$$\therefore I_6' = 2 \times \left( \frac{6}{6+6} \right) = 1A$$



[2X1 POINT]

Step(III):

$$\begin{aligned} \therefore \text{Difference of value of current in } 2\Omega &= |I_2 - I_2'| \\ &= |2.5 - 2| \\ &= 0.5A \end{aligned}$$

[1 POINT]

$$\begin{aligned} \therefore \text{Difference of value of current in } 6\Omega &= |I_6 - I_6'| \\ &= |1.5 - 1| \\ &= 0.5A \end{aligned}$$

[1 POINT]

SOL(7):

Same as Set-A.

SOL(8):

Current across  $2\Omega$  resistance,

$$\therefore I_2 = \frac{10}{2} = 5A \quad [2 \text{ POINT}]$$

Current across  $4\Omega$  resistance,


$$I_4 = \frac{10}{4} = 2.5A$$

Apply KCL at node-A,

$$2 = I_5 + I_4 + I_2$$

$$2 = I_5 + 2.5 + 5$$
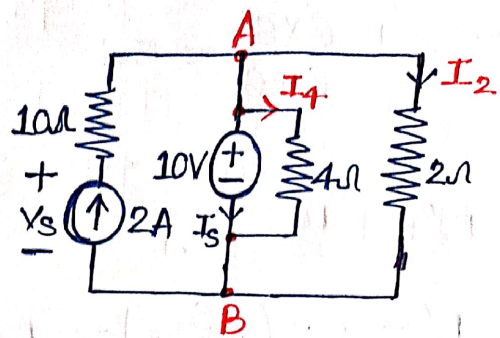
$$\therefore I_5 = -5.5A \quad [2 \text{ POINT}]$$



By circuit —  $-V_s + 2 \times 10 = -2 \times 5$

$$\therefore V_s = +30 \text{ Volt} \quad [2 \text{ POINT}]$$

SOL(9):

By using superposition theorem,

$$I_0 = \pm I_1 \pm I_2$$

where,


$I_1$  = current across resistor  $R$ , when voltage source  $V$  active alone

$I_2$  = current across resistor  $R$ , when current source  $I$  active alone

$$\sqrt{\left(\frac{P_0}{R}\right)} = \pm \sqrt{\left(\frac{P_1}{R}\right)} \pm \sqrt{\left(\frac{P_2}{R}\right)}$$

$$P_0 = (\pm \sqrt{P_1} \pm \sqrt{P_2})^2$$

[2 POINT]

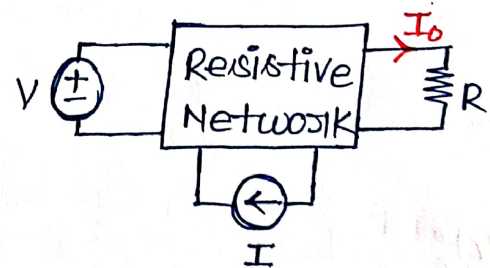



$$P_o = (\sqrt{9} + \sqrt{16})^2 = (3 + 4)^2 = 49W$$

$$P_o = (\sqrt{9} - \sqrt{16})^2 = (3 - 4)^2 = 1W$$

∴ Power dissipated by resistor R, when both sources are active —  $P_o = 49W, 1W$  [4 POINT]