

Tutorial-5 & 6

Winter 2024

Basic Electronics (ECE113)

Q1: In the given following circuit (Figure-1), the switch was initially closed to Position-1 for long time. At time $t=0$ sec, the switch was transferred to Position-2, now find the value of voltage across capacitor at time $t=0$ sec and $t=160 \mu\text{sec}$.

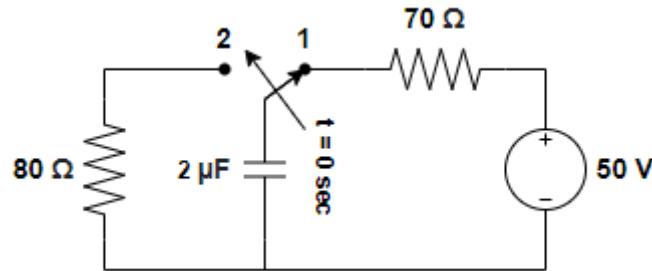


Figure 1

Q2: In the given following circuit (Figure-2), the switch was initially opened for a long time. The switch was closed at time $t=0$ sec. Do-

- (a) Choose R_1 , so that the response after $t=0$ sec will be critically damped.
- (b) Choose R_2 , so that $V_C(0)=100$ Volt
- (c) Find $V_C(t)$ at time $t=1$ msec.

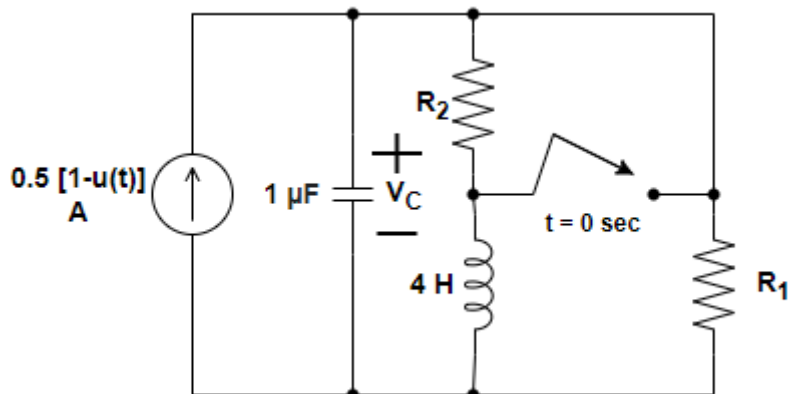


Figure 2

Q3: Find the value of I_C and I in the given following circuit (Figure-3).

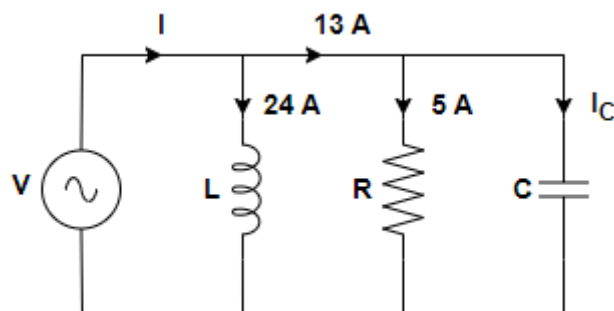


Figure 3

Q4: Find the value of current I_1 and I_L in the circuit shown in Figure-4 for $t > 0$ sec.

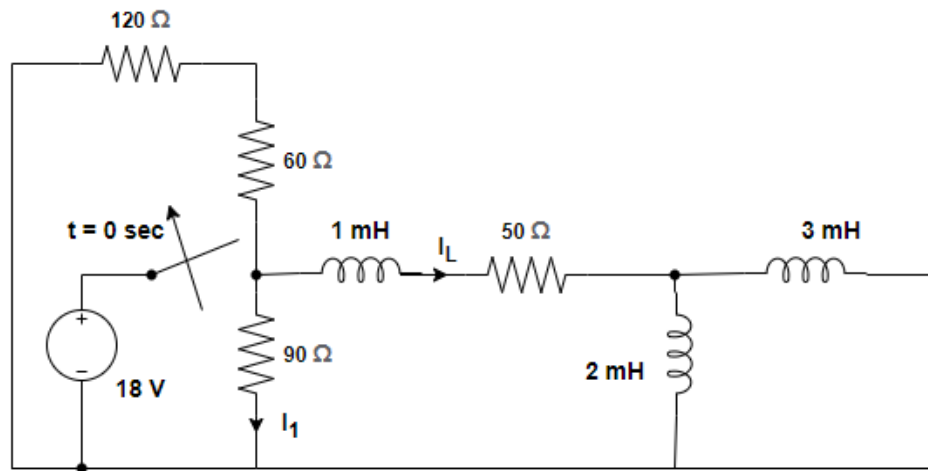


Figure 4

Q5: In the given following circuit (Figure-5), the switch was initially opened for a long time. The switch is closed at $t = 0$ sec then find out the value of-

- (a) $I_L(0^-)$
- (b) $V_C(0^-)$
- (c) $I_R(0^+)$
- (d) $I_C(0^+)$
- (e) $V_C(0.2)$

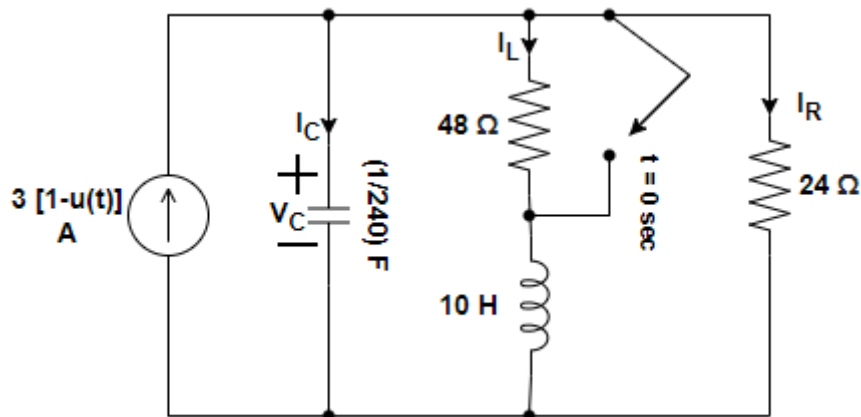


Figure 5

Q6: For the circuit of Figure-6, find the value of $i(t)$ for $t = \infty$, 0^- , 0^+ and $100 \mu\text{sec}$.

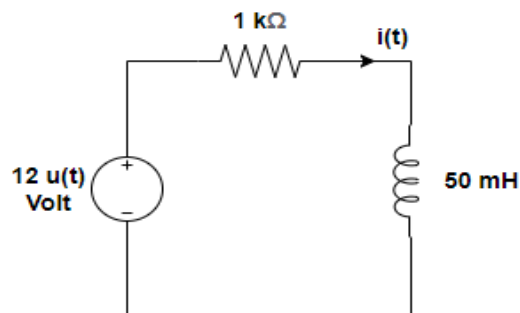


Figure 6

Q7: Determine the value and draw the curve of $i(t)$ for all value of time in the circuit of Figure-7.

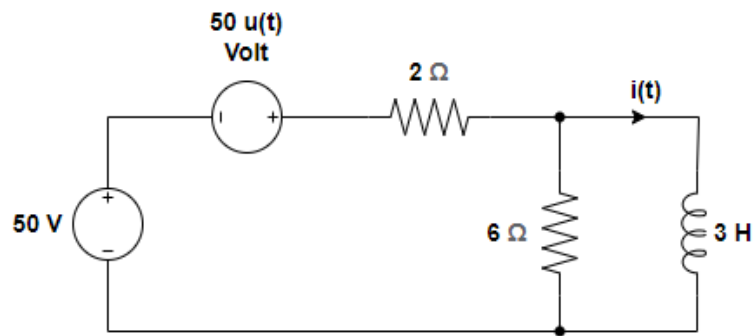


Figure 7

Q8: Find the capacitor voltage $V_C(t)$ and the current $i(t)$ in the $200\ \Omega$ resistor of Figure-8 for all time. (The switch transfer from position **a** to **b** at time $t=0$ sec).

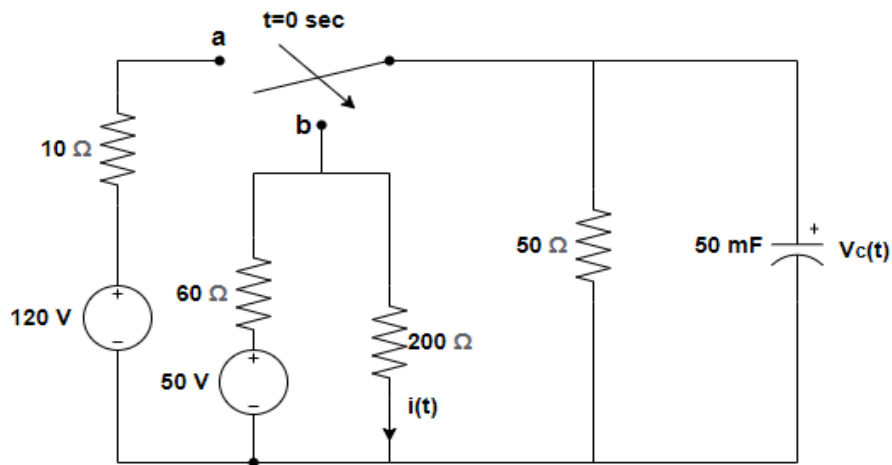


Figure 8