

Tutorial-3

Winter 2024

Basic Electronics (ECE113)

Q1: In the given following circuit (Figure-1), find the value of voltage across 100 ohm (V_p) by using nodal analysis.

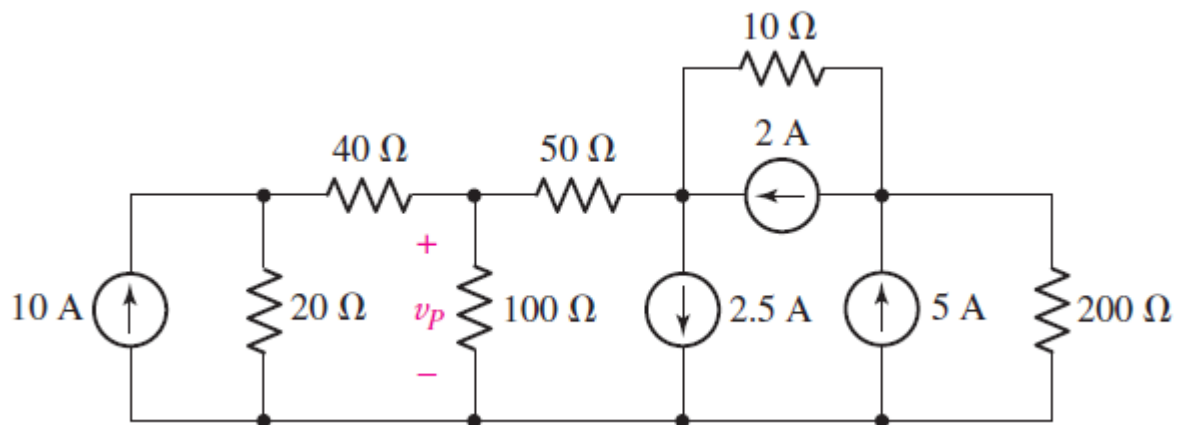


Figure 1

Q2: By bottom node as reference node (Figure-2), find the all node voltages and current through 7 Ω resistance by using nodal analysis.

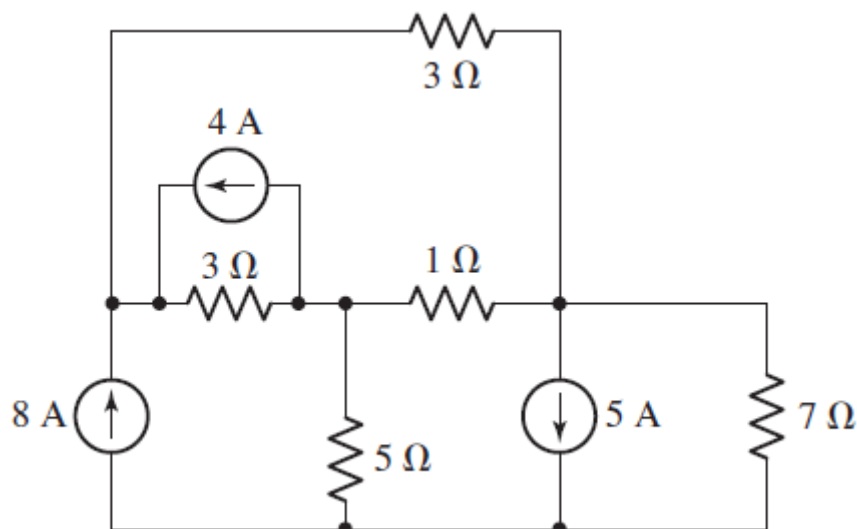


Figure 2

Q3: Find all node voltages with the help of nodal analysis in the given following circuit (Figure-3).

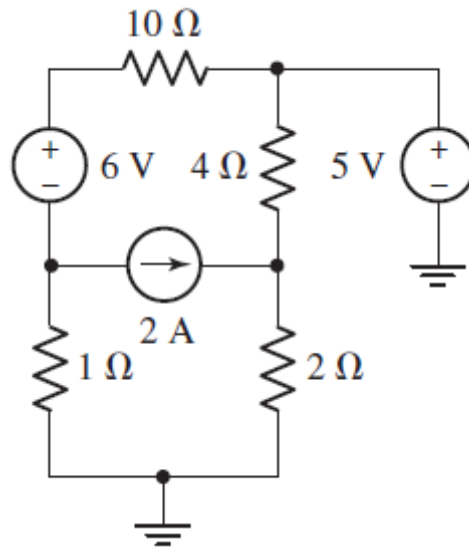


Figure 3

Q4: In the given following circuit (Figure-4), find all node voltages and power dissipation in $1\ \Omega$ resistance.

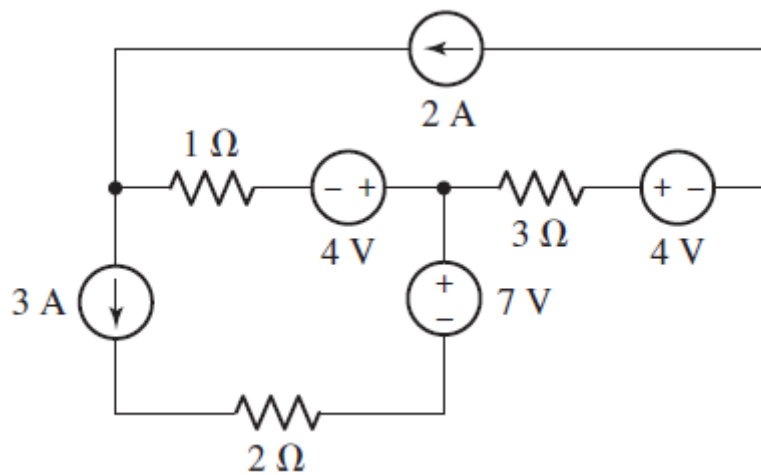


Figure 4

Q5: In the given following circuit (Figure-5), find all node voltages and power delivered by 1V ideal voltages source.

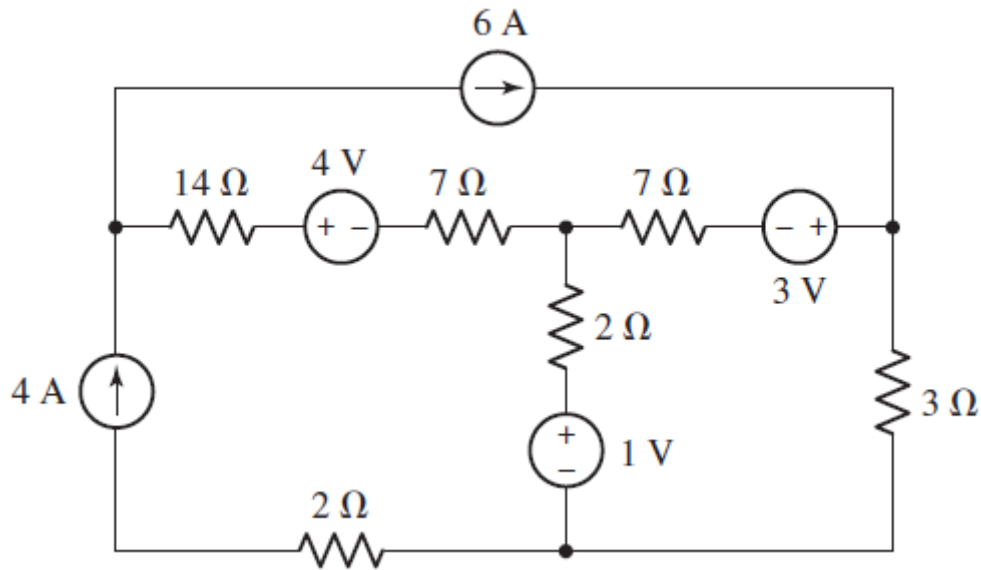


Figure 5

Q6: In the given following circuit (Figure-6), find the value of voltage across $3\ \Omega$ resistance by using nodal analysis.

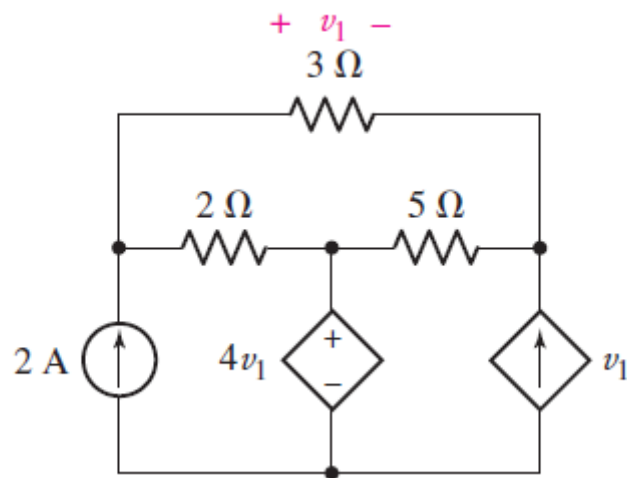


Figure 6

Q7: In the given circuit (Figure-7), set of two **5 volt**, practical voltage source are connected in across the load ($4\ \Omega$). Both sources are represented by their actual voltage and internal resistance. Do the following analysis-

- (a) Find out the current across the load ($4\ \Omega$).

- (b) Is there any internal current in between the two practical sources? If yes then what is the value?
- (c) What will happen, when both practical sources are replaced by ideal voltage source?

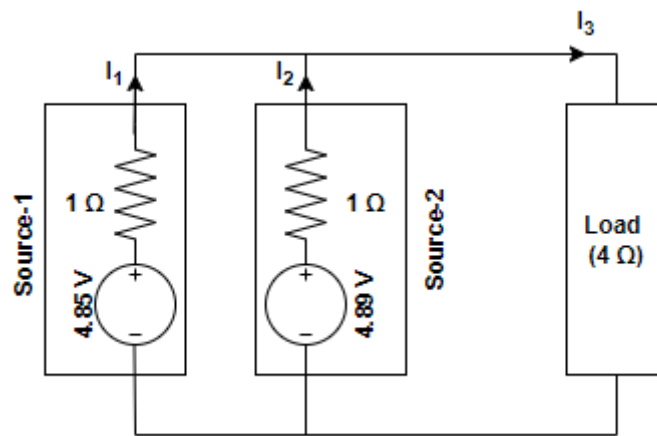


Figure 7