

2022530 → Syed


BE-Ass-2

Ques 1

As initially the current across inductor = 0 & presuming $C_V = 0$.

so, when the S_1 is connected to B_1 & S_2 connected to B_2 .

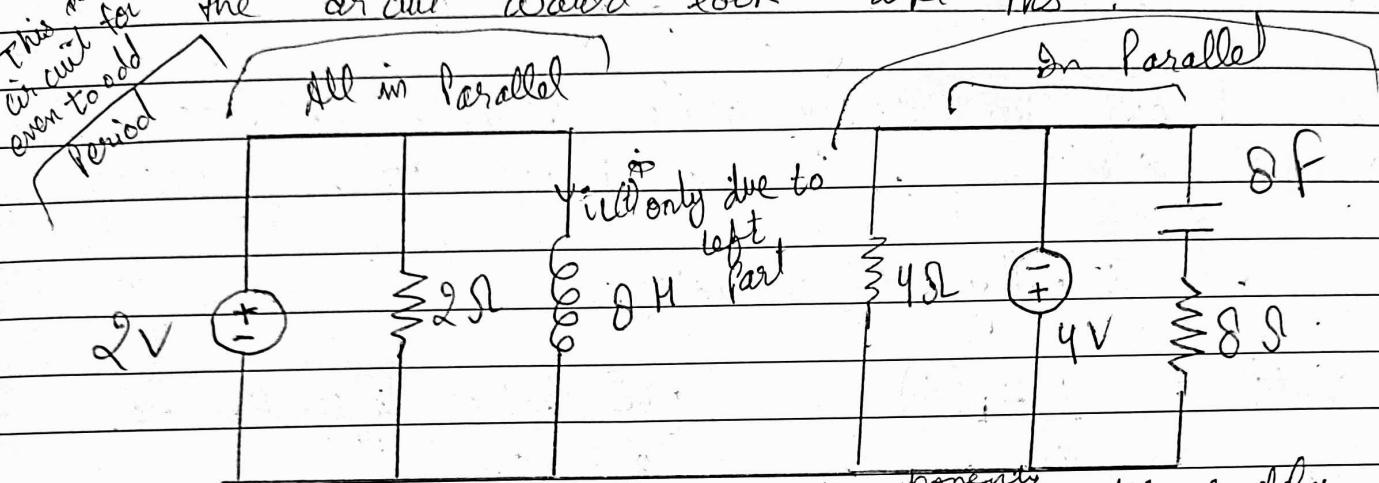This for the circuit would look like this.



(Here both circuits components work independently)

as Both have no input current

The time interval given:

$$2nT \leq t < (2n+1)T, \quad n = 0, 1, 2, \dots$$

$$(2n+1)T \leq t < (2n+2)T, \quad n = 0, 1, 2, \dots$$

By observing above,

$$0T - T \quad 2T - 3T$$

$$T - 2T$$

$$3T - 4T$$

$$\begin{aligned} 4T - ST &\quad \left. \begin{aligned} S_1 &\leftrightarrow B_1 \\ S_2 &\leftrightarrow B_2 \end{aligned} \right\} \\ 3T - 4T &\quad \left. \begin{aligned} S_1 &\leftrightarrow A_1 \\ S_2 &\leftrightarrow B_2 \end{aligned} \right\} \end{aligned}$$

thus we can say there is alternate switching at each time interval T .

~~at $t = 0$~~

In the interval

$$0 \leq t \leq T$$

$$\text{or } i_L(0^-) = i_L(0^+) = 0.$$

~~We know in the steady state~~

But as time passes, current will start to pass through inductor as, ~~in the steady state by short circuit.~~

\because we know in steady state inductor behaves as a short circuit. & we know, $V_L = \frac{L di}{dt}$

As, $\mathfrak{I} V$ directly to inductor.

$$V_L(t) = \frac{L di_L(t)}{dt}$$

~~This is a differential eq. of type~~

$$\int \mathfrak{I} V = 8 \int \frac{di_L(t)}{dt}$$



By integrating, $\Rightarrow \int (t) dt$




$$\int 2dt = \int 8 di_L(t) \Rightarrow (2t)_0^T = 8[i_L].$$

$$i_L(t) = \frac{t}{4}, \quad 0 \leq t \leq T$$

$$\therefore i_L(0^+) = i_L(0^+)$$

As, \mathfrak{I} we can $i_L(t)$ through inductor is linear in time interval $0 \leq t \leq T$

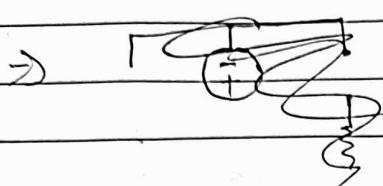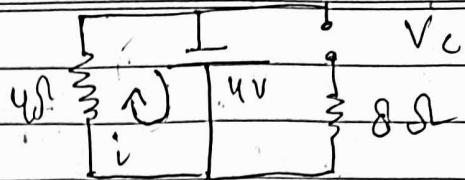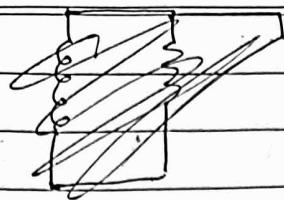Now, in the same interval component 2 = ~~zero~~



$$Req = 8\Omega$$

By KVL, $4 - 4i = 0$, $i = 1$
 $i = 4/4 = 1 \text{ Amp.}$


So, $V_c = 4V$ in the steady state.

~~We can~~

~~go in the Time interval, 0 - T, we will find~~


~~Now None, to interval 0 to~~

~~T, 2T, S₁ to A₁ & S₂ to A₂~~

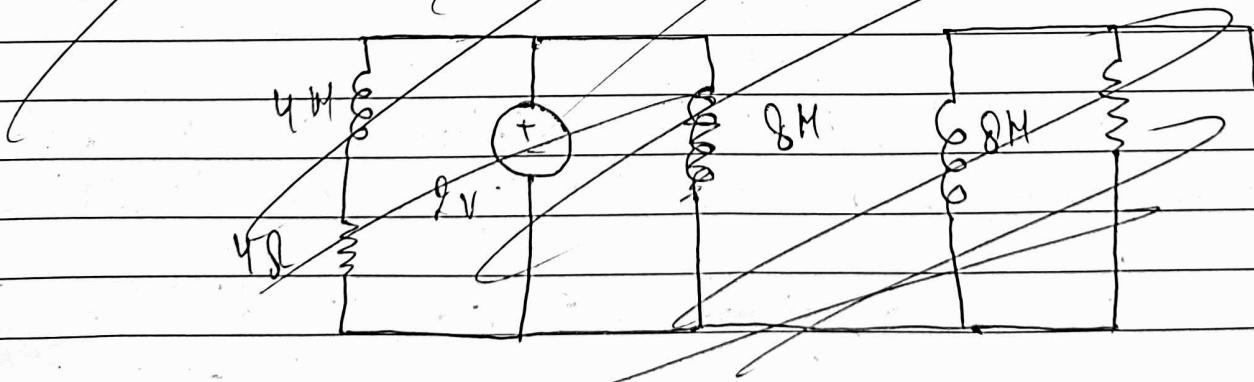

Now, $T \leq t < 2T$

~~(for all odd to even period)~~

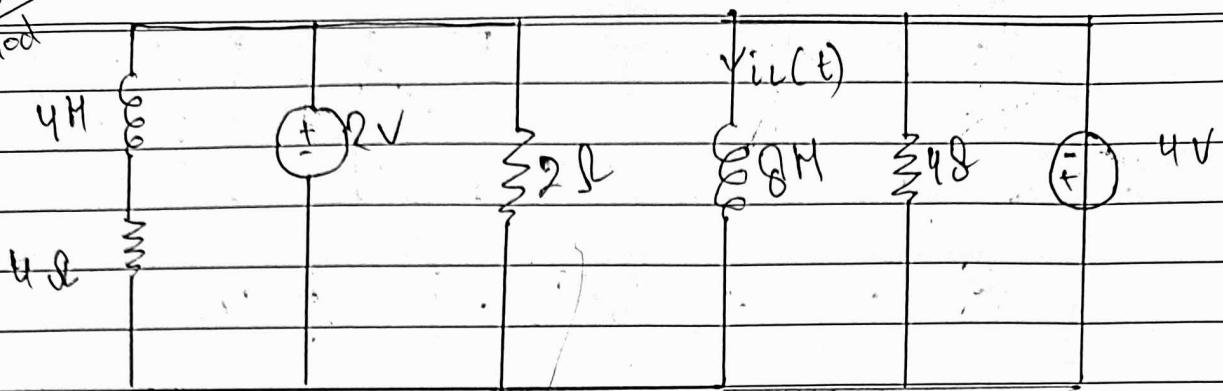

Here $i_L(t)$ only by right component.
Both components work independently

\therefore we know for second.

$$\int 8 \frac{di_L(t)}{dt} = -4 \quad \text{L di/dt} = v$$

$$\Rightarrow -4[t]_T^t = 8 \int_{T/4}^{i_L(t)} di_L(t)$$

$$\Rightarrow T-t = 2i_L(t) - T/2$$

$$i_L(t) = \frac{3T}{4} - \frac{t}{2}, \quad \text{for, } T \leq t < 2T$$

Now, ~~$2T \leq t < 3T$~~ follow the first diagram

Again inductor directly to power source ($2V$)

$$\int 2 = \int 8 \frac{di_L(t)}{dt} \Rightarrow \int 2 dt = 8 \int_{T/4}^{i_L(t)} di_L(t)$$

\therefore Here, the current of.

$$i_L(T^-) = i_L(T^+) \\ i_L(2T^-) = i_L(2T^+)$$

$$= t - 2T = 4(i_L(t) + T/4) \\ i_L(t) = \frac{t}{4} - \frac{3T}{4}$$

So we observe, that $i_L(2T) = i_L(t) = \frac{3T}{4} - \frac{2T}{2}$
 $= -\frac{T}{4}$

so for each end point,

~~start~~ : end current of one interval serves as the starting current for next interval.

Again for $3T \leq t < 4T$.

$$\int_{-4}^t i_L(t) dt = \int_{-4}^{3T} 8 \frac{di_L(t)}{dt} dt = \int_{-4}^{3T} -4 dt = 2 \int_0^t i_L(t) dt$$

~~8T~~ $i_L(t) = \frac{3T}{2} - \frac{t}{2}$

Here similarly, $i_L(3T^-) = i_L(3T^+)$

Again for $4T \leq t < 5T$,

$$2 = \frac{8 \frac{di_L(t)}{dt}}{dt} \Rightarrow \int_{4T}^t dt = 4 \int_{-T/2}^{i_L(t)} di_L(t)$$

$$\Rightarrow t - 4T = -4i$$


$$\Rightarrow t - 4T = 4i_L(t) + 2T$$

$$= i_L(t) = \frac{t}{4} - \frac{6T}{4}$$

$$i_L(t) = \begin{cases} t/4, & 0 \leq t < T \\ 3T/4 - t/2, & T \leq t < 2T \\ t/4 - 3T/4, & 2T \leq t < 3T \\ 3T/2 - t/2, & 3T \leq t < 4T \\ t/4 - \frac{6T}{4}, & 4T \leq t \leq 5T \end{cases}$$

... and so on.

Now, we can also plot a graph.

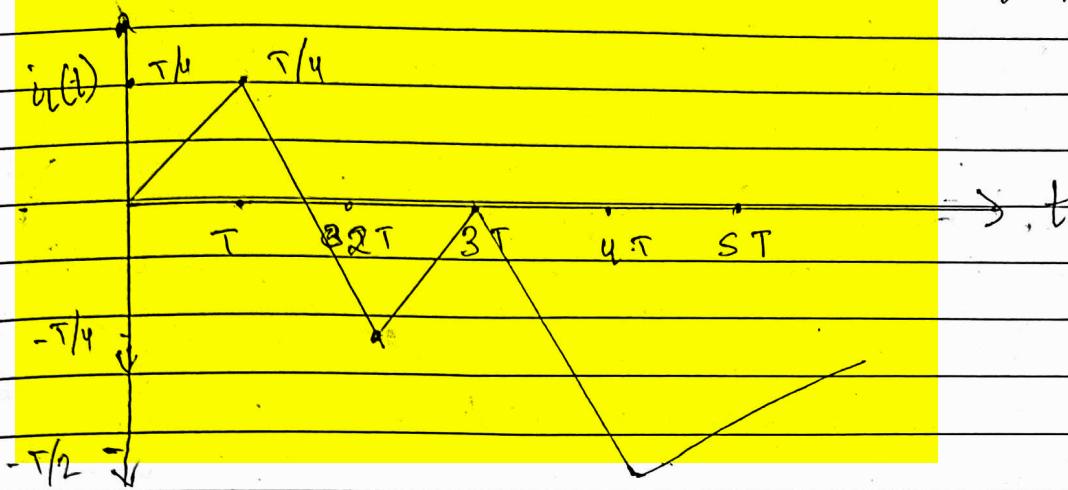

Now, we can use Laplace transform to transform to unit step function.

$$u(t) = \begin{cases} 1, & t \geq 0 \\ 0, & t < 0 \end{cases}$$

$$\begin{aligned} i_u(t) &= \frac{t}{4} u(t) - \frac{t}{4} u(t-T) \\ &\quad + \frac{3T-t}{4} \left(u(t-T) - u(t-2T) \right) \\ &\quad + \frac{t-3T}{4} \left(u(t-2T) - u(t-3T) \right) \end{aligned}$$

and so on

⇒ By solving the above Laplace transform we can change to the standard form


$$\text{or, } i_u(t) = \frac{t}{4} u(t) + 2 \sum_{n=1}^{\infty} (-1)^n (t-nT) (u(t-nT))$$

where u is step functions

$$a \rightarrow 100 \sin(10^4 t) = V_c(t), t \geq 0^+$$

$$b \rightarrow 100 \text{ volt} = V_c$$


Dues - 2

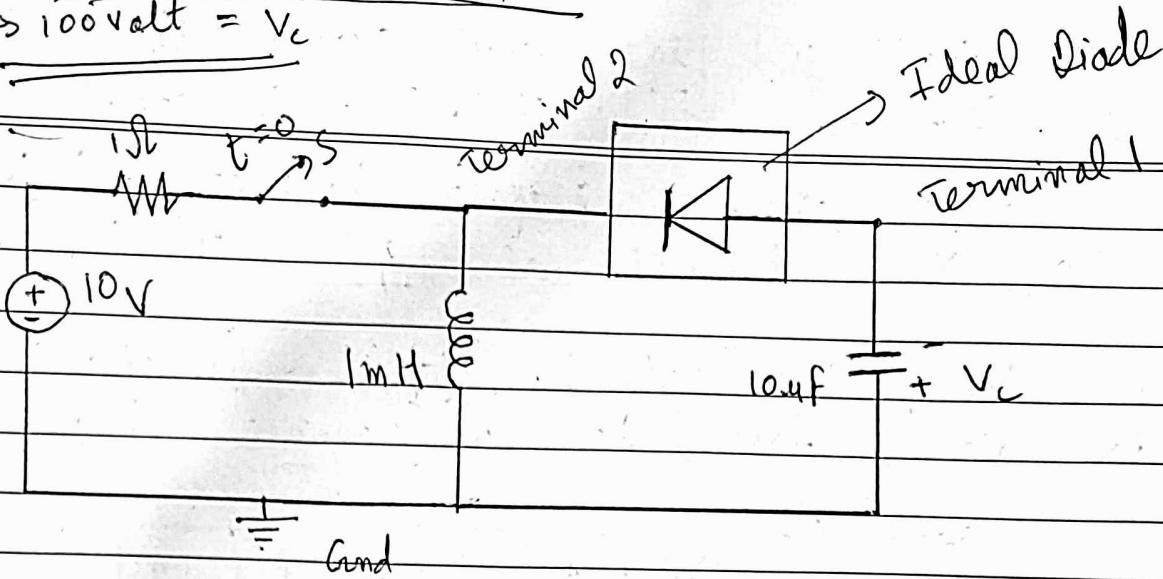

- \because The given electronic device is an ideal diode as it can be inferred from the V-I characteristic curve.
- \because when the diode is in forward bias, $R = 0$ & behaves like a short circuit.
- \because when the diode is in reverse bias, $R = \infty$, like an open circuit.


~~When there is an application of positive voltage, current increases~~

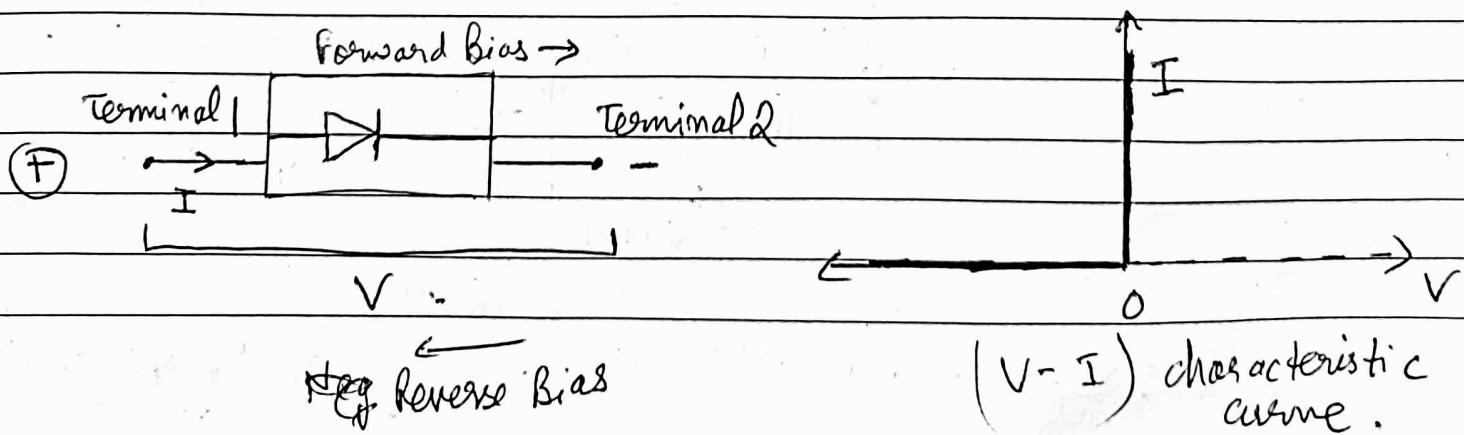- \because when there is an application of positive voltage in the +(+)ve direction (Terminal 1 to Terminal 2) [like open circuit] current increases. [see curve] [like short circuit]
- \because when there is an application of voltage in (-)ve direction (Terminal 2 to terminal 1), current does not increase, & remains 0. [like open circuit]



when the circuit was left with switch closed.
 ie, from ($t \rightarrow -\infty$ to 0) it was in steady state
 " in steady state Inductor behaves as short circuit
 & capacitor behaves as open circuit.

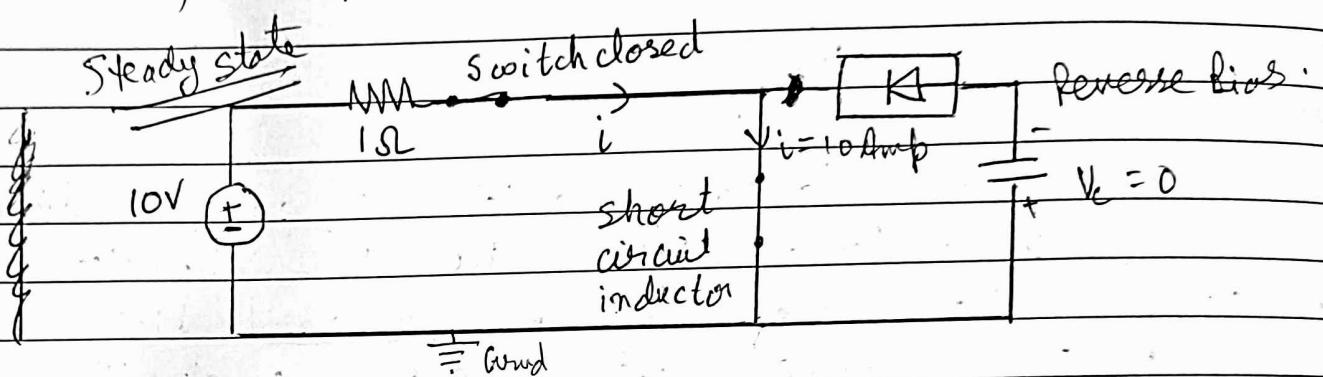When the voltage will be applied, (electronic device)
 (ideal diode) would be in reverse bias




By KVL $10 - iR = 0$
 $i = 10/R = 10/1 = 10 \text{ Amp}$

so, $V_c(0^-) = 0$ so, $i_L(0^-) = 10 \text{ Amp}$

$$V_c(0^-) = V_c(0^+) = 0$$

~~switch open~~

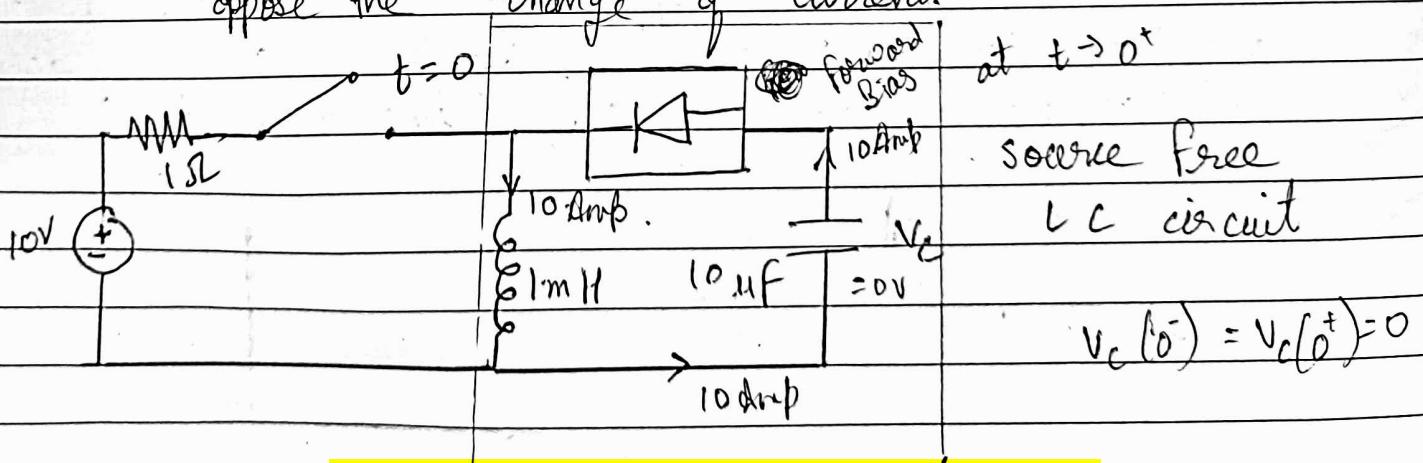Now, in the Transient state, inductor will oppose the change of current.



Q b) $i_L(0^-) = i_L(0^+) = 10 \text{ Amp}$

(Property of
 Transient)

$$i_L(0^-) = i_L(0^+) = 10 \text{ Amp}$$


Property of LC circuit
in transient state

This is like LC oscillation [but only half cycle possible]

\therefore Now inductor will charge the inductor

By KVL - integrator.

$$\Rightarrow -V_L - V_C = 0$$

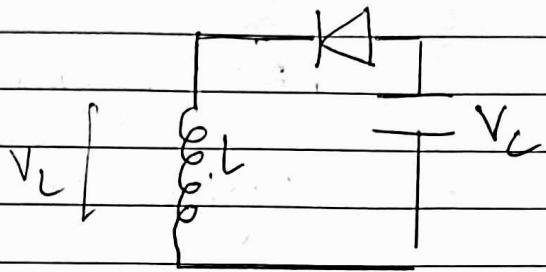

$$\Rightarrow -L \frac{di(t)}{dt} - V_C = 0$$

$$\because V_L = L \frac{di}{dt} \quad \therefore q = CV \Rightarrow dq = C dV$$

$$V_i \left[\begin{array}{c} L \\ \downarrow \\ i(t) \end{array} \right] - \frac{1}{C} V_C$$

$$\Rightarrow \therefore i(t) = \frac{CdV_C}{dt}$$

$$\Rightarrow \frac{Ldi(t)}{dt} + \frac{q(t)}{C} = 0$$

\because As it has two energy storing devices so it is a second order circuit, so it has a differential eq of order 2

$$\Rightarrow \frac{Ldi(t)}{dt} + \frac{1}{C} \int i dt = 0$$

$$\Rightarrow \frac{d^2i(t)}{dt^2} = -\frac{1}{LC} i$$

This is integro differential eq.

$$\Rightarrow \frac{d^2i(t)}{dt^2} = \frac{1}{LC} i$$

Second order differential eq. for the LC series circuit

at time t in the circuit $i(t)$ denotes the current across inductor or across capacitor

$$\therefore \text{Damping factor. } \alpha = \frac{R}{2L} \quad \therefore \text{Natural freq. } = \omega_0 = \frac{1}{\sqrt{LC}}$$

∴ Current $i(t)$ denotes the current through inductor or capacitor or circuit as "L & C are in series"

Now the characteristic eq.

$$D^2 + \frac{1}{LC} i(t) = 0 \Rightarrow \text{so, } D^2 = -\frac{1}{LC}$$

As, Negative here, so, $D = \pm \frac{i}{\sqrt{LC}} \quad] i \rightarrow \text{not current}$

here roots are complex conjugate of each other.

Here i means symbol for complex roots. i.e. imaginary unit no. $\Rightarrow i = \sqrt{-1}$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1 \times 10^{-3} \times 10 \times 10^{-6}}} \Rightarrow \frac{1}{\sqrt{10^{-8}}} = \boxed{10^4 \text{ Hertz}}$$

$$\boxed{\alpha = \frac{R}{2L} = 0 \quad \text{as } R=0} \quad \boxed{\omega_0 = 10^4 \text{ Hertz}}$$

As, $\alpha < \omega_0$ so there is no damping so energy would be conserved & would oscillate.

As, initially after opening switch, $i_L(0^+)$ = 10 A.m.p.

$$\text{so, energy in the inductor} = \frac{1}{2} L i^2 = \frac{1}{2} \times 10^{-3} \times 10 \times 10$$

(Magnetic energy)

$$\text{Initial energy of inductor.} \quad \boxed{0.05 \text{ Joule}} \quad \Leftarrow = \frac{10}{2} = 0.05 \text{ Joule}$$

$L \rightarrow$ stores energy in the form of magnetic field
 $\& C \rightarrow$ stores in the form of Inductor

As, this is LC oscillation, so, after some time all energy would appear across capacitor

$$= \frac{\cancel{q^2}}{2L} - \frac{q^2}{2C}$$

& as energy is conserved $[R = 0]$

$$\frac{1}{2} i^2 = \frac{q^2}{2C}$$

$$0.05 \times 2 \times C = q^2 \Rightarrow q = \sqrt{0.05 \times 2 \times 10 \times 10^{-6}}$$

$q = 0.001$ coulomb. & $q = CV$, so $V = q/C$

$$V_C = \frac{0.001}{10^{-5}} = 100 \text{ volt}$$

$$\text{So, } [V_C = 100 \text{ Volt}]$$

~~Here~~ Now
All energy is at capacitor

This is at when inductor has 0 current & ~~C~~ has Max voltage or $i_L = 0$ & $V_C \rightarrow \text{Max}$

Also By the characteristic eq.

$$i(t) = e^{-\alpha t} [C_1 \cos \omega_d t]$$

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$$

& as $\alpha = 0$

$$= e^{-\alpha t} [C_1 \cos(\omega_d t)]$$

$$\omega_d = \omega_0$$

$$= C_1 \cos \omega_0 t$$

$$\alpha = 0 \text{ so, } e^0 = 1$$

$$\text{Replace } C_1 \text{ by } A = A \cos(\omega_0 t)$$

where "A" is Amplitude of oscillation

~~at~~

Amplitude

ω_0 Angular frequency of oscillation

or replace C_1 by A

$$\text{As, } i(0^+) = \cancel{i(0)} \cancel{\approx} 10 \text{ Amp}$$

$$\text{As } i_L(0^+) = i(0^+) = 10 \text{ Amp.}$$

$$i(t) = A \cos(\omega_0 t)$$

$$10 = A \cos(\omega_0 \times 0)$$



$$10 = A$$

so $\boxed{A = 10 \text{ metres}} \text{Wattes}$

$$\text{so, } i(t) = i_L(t) = 10 \cos(\omega_0 t) = \boxed{10 \cos(10^4 t)}$$

As current would not flow from inductor as then ideal diode would be in reverse bias,

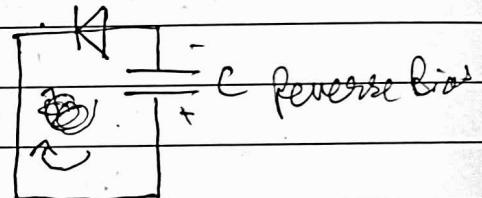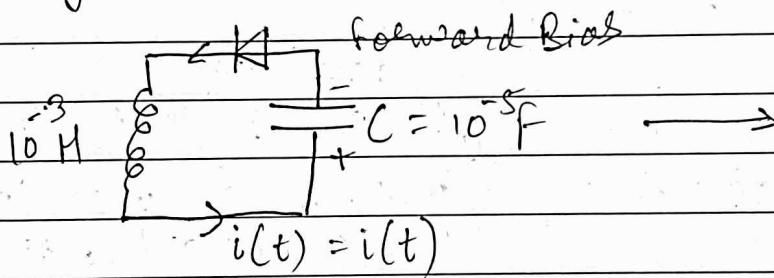so there would be only one cycle half cycle or oscillation, ie, from L to C



$$i_L = 0 \text{ Amp}$$


$$Q_0 = 0 \text{ coulombs} \quad V_C = 0 \text{ volt}$$

$$Q = 0.001 \text{ coulombs}$$


$$V_C = 100 \text{ volt}$$

$$\text{so, when } 10^4 t = \pi/2, \quad t = \frac{\pi}{2} \times 10^{-4} \text{ seconds.}$$

$$\text{or } 0.157 \text{ msec}$$

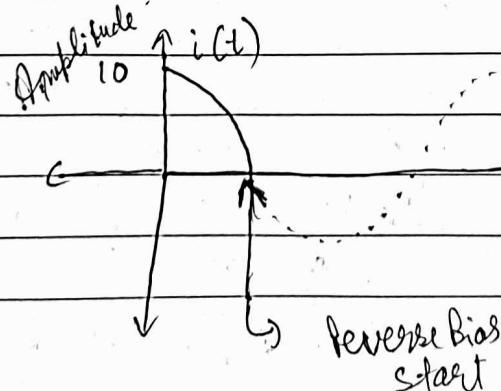

only Half cycle possible

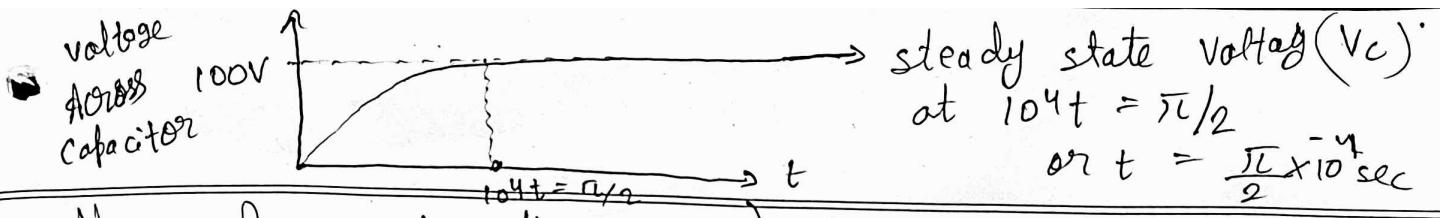

Now By integrating $i(t)$

$$V_c(t) = \cancel{\int i(t) dt}, V_c = \frac{1}{C} \int i(t) dt$$

$$\text{so } V_c(t) = \frac{1}{C} \int i(t) dt$$

$$= \frac{1}{C} \int 10 \cos(10^4 t) dt$$

$$= 10^5 \times 10 \int \cos(10^4 t) dt$$

$$= 10^6 \int \sin(10^4 t) dt$$

~~KO⁵~~

$$= \frac{1}{10 \times 10^{-6}} \times 10 \frac{\sin(10^4 t)}{10^4} dt$$

$$\left(\because \int \cos(at) dt \right)$$

$$= \frac{\sin(at)}{a}$$

$$V_c(t) = 100 \sin(10^4 t), t \geq 0^+$$

Answer (a)

Or say when $10^4 t = \pi/2$

And, at $t = 0.187\text{ms}$, there is steady state

As, Here, LC oscillation would stop due to the presence of diode which will become reverse bias when capacitor will try to loose its charge, hence this half cycle can be said as steady state of capacitor as now voltage would not change so, when $10^4 t = \pi/2$

$$V_c(t) = 100 \sin(10^4 t) = 100 \sin(\pi/2) = 100 \text{ Volt} = V_c$$