

Tutorial-4

Winter 2024

Basic Electronics (ECE113)

Q1: (a) Employ superposition to determine the individual contribution from each independent source to the voltage v as labelled in the circuit shown in Figure-1. (b) Compute the power absorbed by the $2\ \Omega$ resistor.

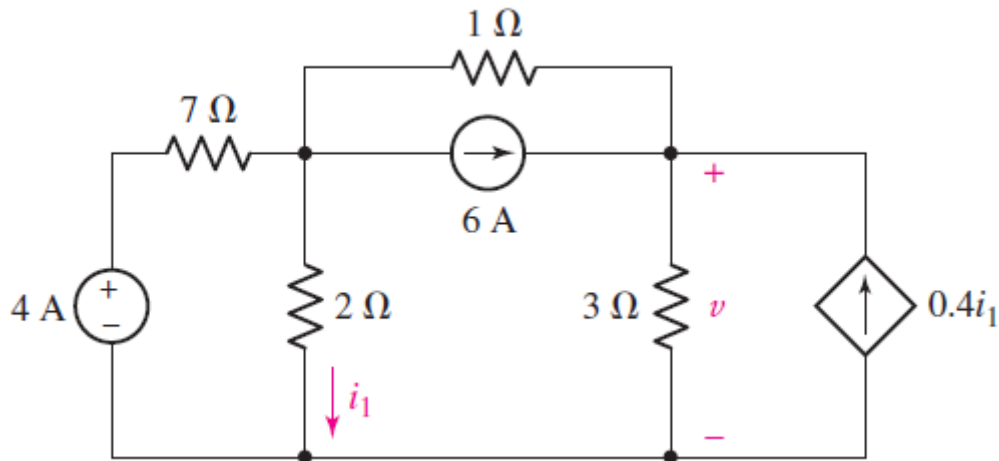


Figure 1

Q2: For the circuit of Figure-2, plot i_L versus v_L corresponding to the range of $0 \leq R \leq \infty$.

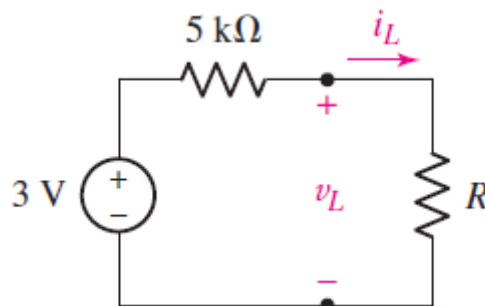


Figure 2

Q3: With regard to the circuit represented in Figure-3, first transform both voltage sources to current sources, reduce the number of elements as much as possible, and determine the voltage V_3 .

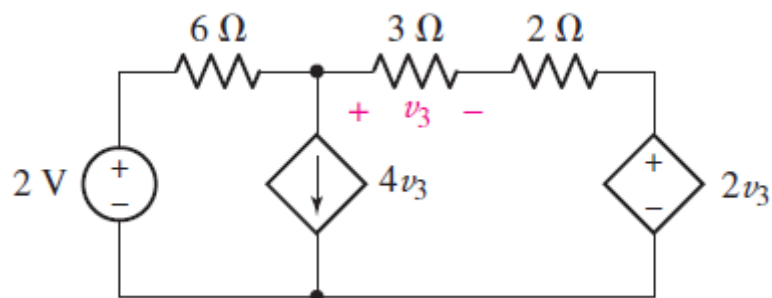


Figure 3

Q4: Determine the Thevenin equivalent of the network shown in Figure-4, as seen looking into the two open terminals.

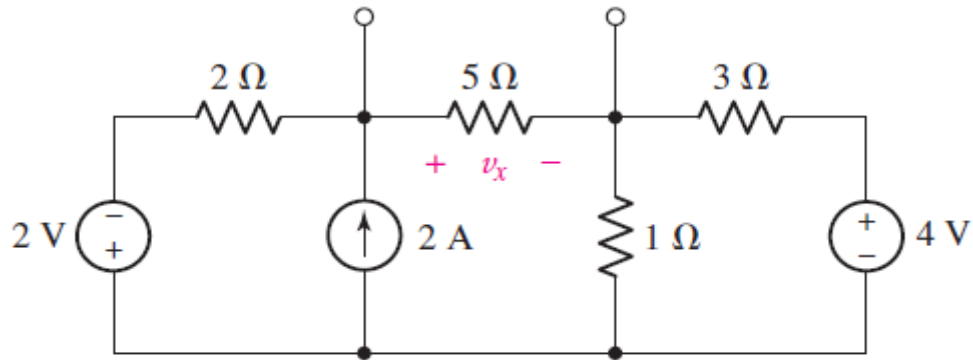


Figure 4

Q5: For the circuit of Figure-5, **(a)** Employ Norton's theorem to reduce the network connected to R_L to only two components. **(b)** Calculate the downward directed current flowing through R_L if it is a $3.3\text{ k}\Omega$ resistor.

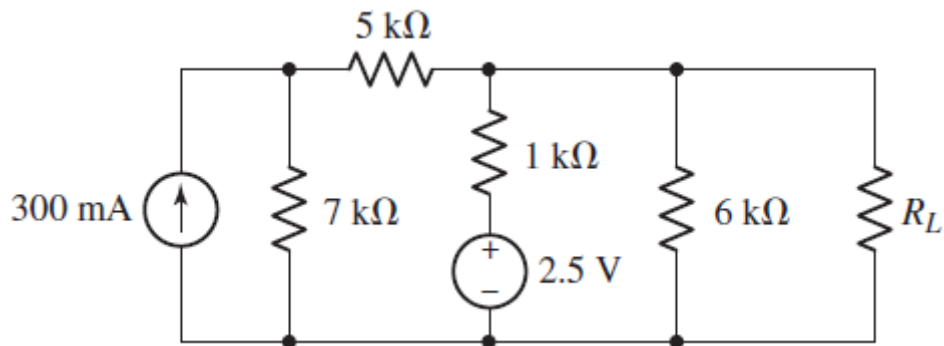


Figure 5

Q6: With regard to the network depicted in Figure-6, determine the Thevenin equivalent as seen by an element connected to terminals **(i) a and b** (ii) **a and c** (iii) **b and c**.

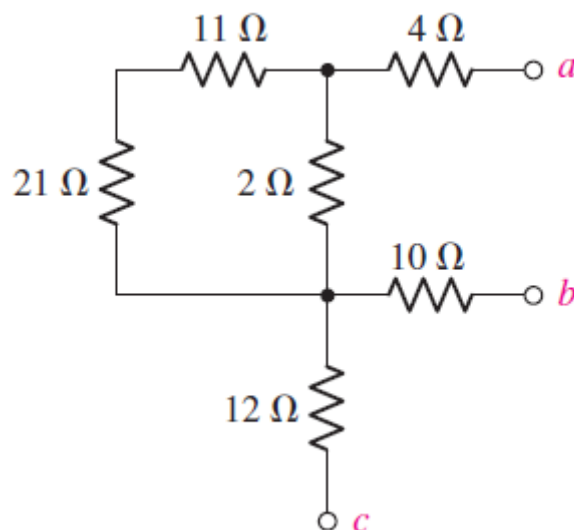


Figure 6

Q7: Employ Thevenin's theorem to obtain a two-component equivalent for the network shown in Figure-7 & Determine the power supplied to a $1\text{ M}\Omega$ resistor connected to the network if current $I_1 = 19\text{ }\mu\text{A}$, $R_1 = R_2 = 1.6\text{ M}\Omega$, $R_3 = 3\text{ M}\Omega$, and $R_4 = R_5 = 1.2\text{ M}\Omega$.

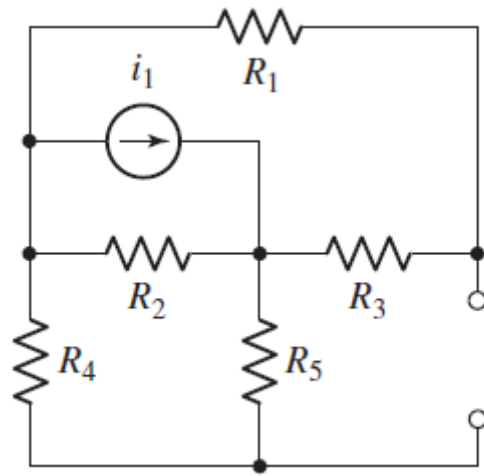


Figure 7